

Quiz #10 EE 220 Fall 2018 Name: _____

Open book and closed notes.

Show your work for credit!

1. Find the op-amp's output voltage in the following circuit. (5 points)

