

Quiz #14 EE 220 Fall 2018 Name: \_\_\_\_\_

Closed book and notes.

Show your work for credit!

1. Plot  $V_r$  for the following simulation **on the same plot** as  $V_{in}$  below. Then write equations (for each transition) that describes  $V_r$ . Do not derive the equations, simply write them. (5 points)

