

Quiz #15 EE 220 Fall 2018 Name: _____

Closed book and notes.

Show your work for credit!

1. Plot V_r for the following simulation **on the same plot** as V_{in} below. Then write equations (for each transition) that describes V_r . Do not derive the equations, simply write them. (5 points)

