

Quiz #16 EE 220 Fall 2018 Name: \_\_\_\_\_

Closed book and notes.

Show your work for credit!

1. Plot the output of the following circuit from a time 0 to 5 ms. Assume the capacitor is initially discharged (both sides are at ground). Show your hand calculations for credit. (5 points)

