

Quiz #17 EE 220 Fall 2018 Name: _____

Closed book and notes.

Show your work for credit!

1. Using phasors determine V_{out} in the following circuit and plot, along with V_{in} , on the same plot. (5 points)

