

Open book and closed notes.

Show your work for credit and **put a box around each of your answers.**

1. Find the current that flows in each of the following circuits in the indicated directions. (5 points)

