


Quiz #4 EE 220 Fall 2018

Name: _____

Open book and closed notes.

Show your work for credit and **place a box around each of your answers.**

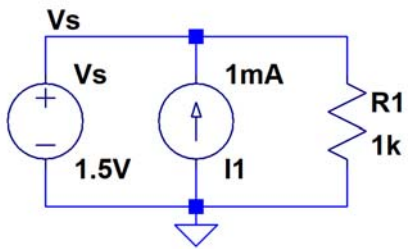1. Determine the current through V_s . Again, show your work for credit. (2 points)



2. Find V_x in the following circuit. (5 points)

