

Quiz #5 EE 220 Fall 2018 Name: \_\_\_\_\_

Open book and closed notes.

Show your work for credit! **Put boxes around your answers.**

1. Find the voltages,  $V_s$ ,  $V_x$ , and  $V_y$  in the following circuit. (5 point)

