

Quiz #7 EE 220 Fall 2018 Name: \_\_\_\_\_

Open book and closed notes.

Show your work for credit!

1. Find the Thevenin and Norton equivalent circuits, with R2 removed, at the terminals marked by red dots seen below. (5 points)

