

Quiz #8 EE 220 Fall 2018 Name: _____

Open book and closed notes.

Show your work for credit!

1. Find V_{out} in the following circuit. Note that $G1$ is a voltage-dependent voltage source. (5 points)

