

Closed book and notes.

Show your work for credit and place boxes around your answers.

1. What are  $V_1$ ,  $V_2$ ,  $V_3$ , and  $V_4$  in the following circuits? (1 point) Next, determine the currents that flow in the directions indicated. (4 points)

