

Quiz #16 EE 220 Fall 2019 Name: _____

Closed book and notes.

Show your work for credit!

1. Calculate the output voltage of the following circuit. Show your hand calculations for credit. (5 points)

