

Quiz #17 EE 220 Fall 2019 Name: \_\_\_\_\_

Closed book and notes.

Show your work for credit!

1. Determine the voltages across the capacitors after the switch closes (hint:  $CV = Q$ ).  
Again, show your work for credit. (5 points)

