

Quiz #21 EE 220 Fall 2019 Name: _____

Closed book and notes.

Show your work for credit!

1. Determine the current (in the time domain) in the following circuit using phasor analysis and sketch, along with the input voltage showing amplitudes and phase shift. Note the peak input voltage is 5V. (5 points)

