

Quiz #6 EE 220 Fall 2019 Name: _____

Closed book and notes.

Show your work for credit!

1. Determine V_x in the following circuit and the current through R_3 . (5 points)

