

Quiz #7 EE 220 Fall 2019 Name: _____

Closed book and notes.

Show your work for credit!

1. Find the Thevenin and Norton equivalent circuits at the terminals marked by red dots seen below. Note that nothing (e.g. R_2) is being removed from this circuit. (5 points)

