

Quiz #8 EE 220 Fall 2019 Name: \_\_\_\_\_

Closed book and notes.

Show your work for credit!

1. Find  $V_{out}$  in the following circuit. Note that E1 is a voltage-dependent voltage source. (5 points)

