

Quiz #9 EE 220 Fall 2019 Name: _____

Open book and closed notes.

Show your work for credit!

1. Find the voltages across R1 ($V_s - V_{out}$) and R2 (V_{out}). As always, show your work for credit. (5 points)

