
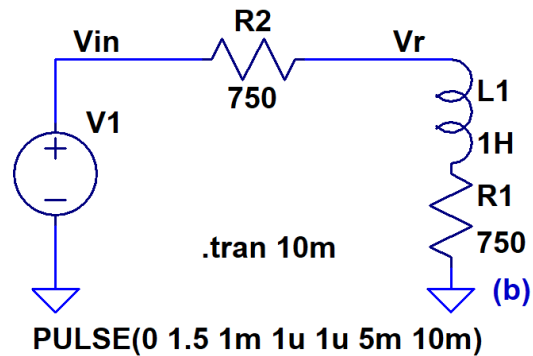


Show your work for credit!

- Design a circuit that creates a triangle waveform that swings between  $-2.5$  and  $+2.5$  V at  $10\text{kHz}$ . Assume the input to the circuit is a square-wave that oscillates at  $10\text{ kHz}$  between  $0$  and  $+1$  V. Show your hand calculations for credit. Verify your design using LTSpice. (4 points)
- Write equations for  $V_r$ , and sketch along with  $V_{in}$ , in the following circuits. Verify your answers with LTSpice. (2 points)

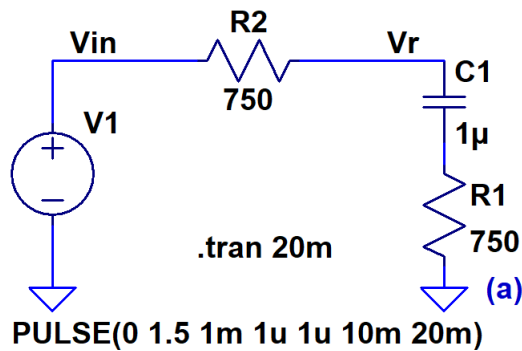

- Determine  $V_{out}$  for each of the following circuits. Sketch  $V_{out}$  and  $V_{in}$  on the same plot. Show your hand calculations for credit. Verify your answers using LTSpice. (8 points)

