

Closed book and notes.

Show your work for credit and place boxes around your answers.

1. What are V1, V2, V3, and V4 in the following circuits? (1 point) Next, determine the currents that flow in the directions indicated. (4 points)

