

Quiz #17 EE 220 Fall 2020 Name: _____

Closed book and notes.

Show your work for credit!

1. Determine the voltages across the capacitors after the switch closes (hint: $CV = Q$).
Again, show your work for credit. (5 points)

