

Quiz #19 EE 220 Fall 2020 Name: _____

Closed book and notes.

Show your work for credit!

1. Determine the output voltage (in the time domain) in the following circuit using phasor analysis and sketch, along with the input voltage showing amplitudes and phase shift. Note the peak input voltage is 5V. (5 points)

