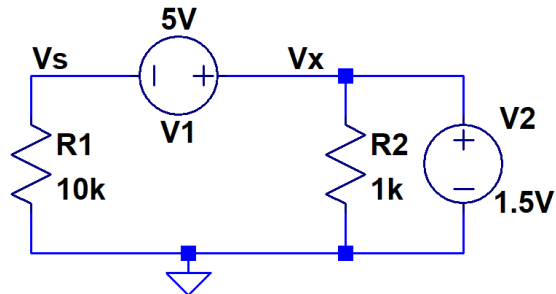


H.W. #2 EE 220 Fall 2021

Show your work for credit and place a box around each of your answers!

1. Determine the voltage and currents in the following circuit. Use simulations to confirm your hand calculations. (3 points)



2. Find the voltages and currents in each of the following circuits. Verify your answers with LTSpice. (9 points)

