

Quiz #12 EE 220 Fall 2021 Name: _____

Closed book and notes.

Show your work for credit!

1. Plot V_c for the following simulation. Then write an equation that describes V_c . Do not derive the equation, simply write it. (5 points)

