

Quiz #14 EE 220 Fall 2021 Name: _____

Closed book and notes.

Show your work for credit!

1. Plot V_r for the following circuit on the plot seen below for both transitions of the input pulse. Write equations for both edges as well. Do not derive the equations, simply write them. (5 points)

