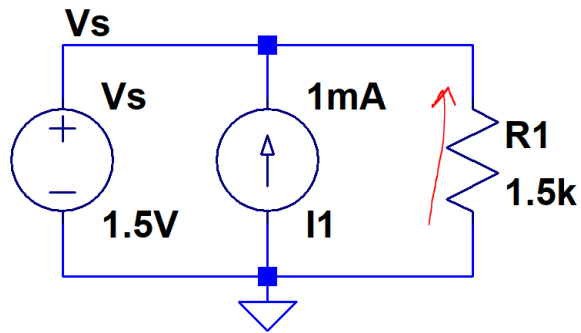


Closed book and notes.

Show your work for credit and **place a box around each of your answers.**

1. Determine the current through R1 in the direction indicated. Again, show your work for credit. (2 points)



2. Find V_x in the following circuit. (5 points)

