

Quiz #7 EE 220 Fall 2021 Name: \_\_\_\_\_

Closed book and notes.

Show your work for credit!

1. Find the Thevenin and Norton equivalent circuits at the terminals marked by red dots seen below. Note that *nothing* (e.g. R2) is removed from this circuit. (5 points)

