

Quiz #9 EE 220 Fall 2021 Name: \_\_\_\_\_

Closed book and closed notes.

Show your work for credit!

1. Find the voltages across R1 ( $V_{out} - V_s$ ) and R2 ( $V_{out}$ ). As always, show your work for credit. (5 points)

