

Quiz #12 EE 220 Fall 2022 Name: \_\_\_\_\_

Closed book and notes.

Show your work for credit!

1. Plot  $V_c$  for the following simulation. Then write an equation that describes  $V_c$ . Do not derive the equation, simply write it. (5 points)

