

Quiz #21 EE 220 Fall 2022 Name: _____

Closed book and notes.

Show your work for credit!

1. Determine V_{out} (in the time domain) in the following circuit using phasor analysis and sketch, along with the input voltage showing amplitudes and phase shift. Note the peak input voltage is 1V. (5 points)

