

Quiz #5 EE 220 Fall 2022 Name: _____

Closed book and notes.

Show your work for credit! **Put boxes around your answers.**

1. Find the voltages, V_s , V_x , and V_y in the following circuit. (5 point)

