

Quiz #8 EE 220 Fall 2022 Name: _____

Closed book and notes.

Show your work for credit!

1. Find V_{out} in the following circuit. Note that E1 is a voltage-dependent voltage source. (5 points)

