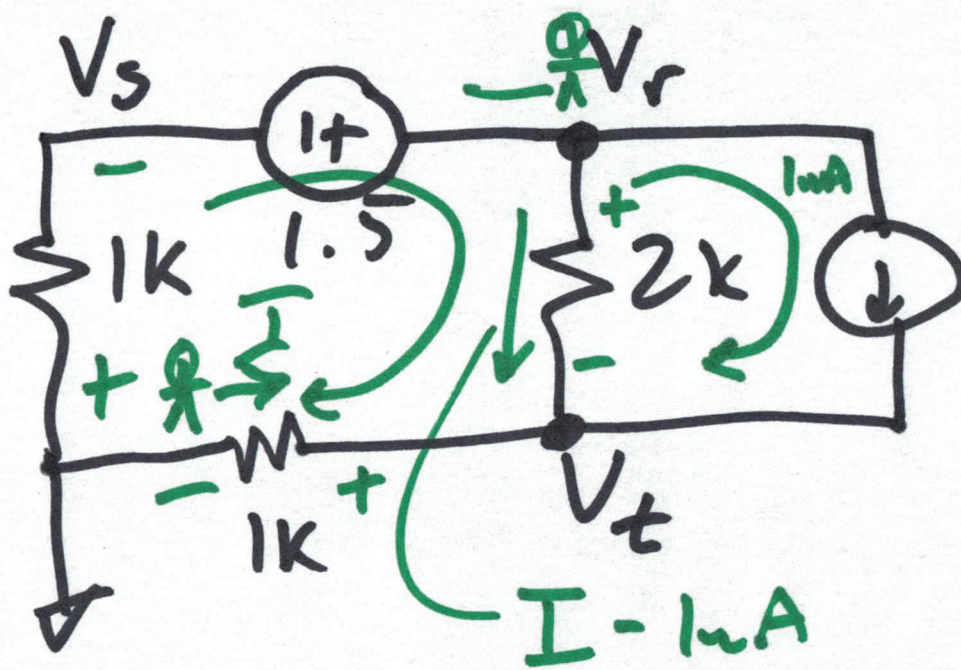


EE 220 Circuits I

Lecture 11

October 4, 2023



$$V_t = +1kI$$

$$V_s = -1kI$$

$$V_r = +1kI + 2k(I - 1\mu A)$$

$$= -1kI + 1.5V$$

$$+1kI + 1k \cdot I + 2k(I - 1\mu A) - 1.5 = 0$$

$$I(1k + 1k + 2k) - 3.5 = 0$$


"4k"

$$V = \frac{3.5}{4} \mu A$$

$$I = \frac{3.5}{4k}$$

Power & Energy

Resistor

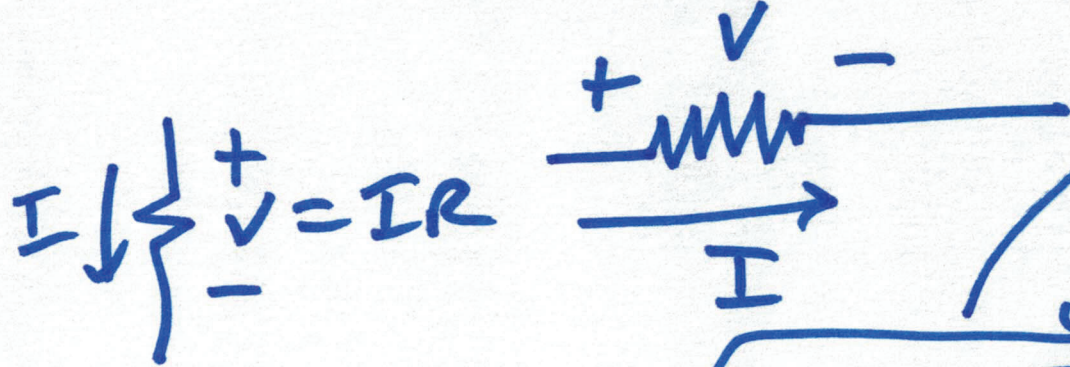

$$V = I \cdot R$$



$$I = \frac{V}{R}$$


$$P = \frac{V^2}{R}$$

(DC power)

$$P = V \cdot I$$

$$P = I^2 R$$

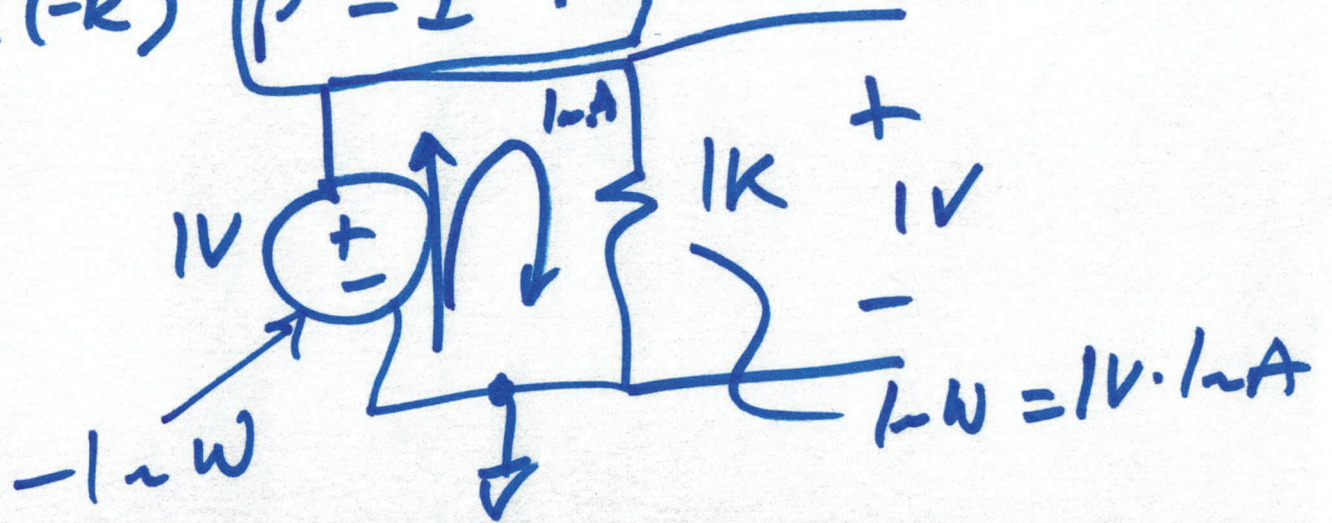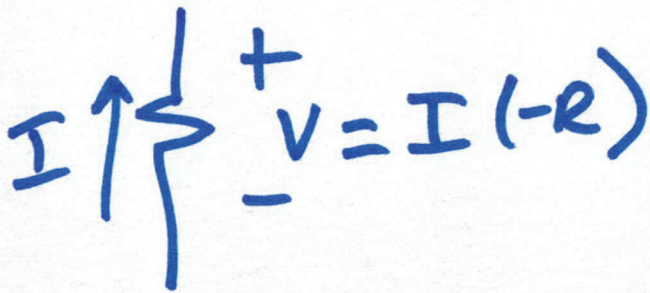

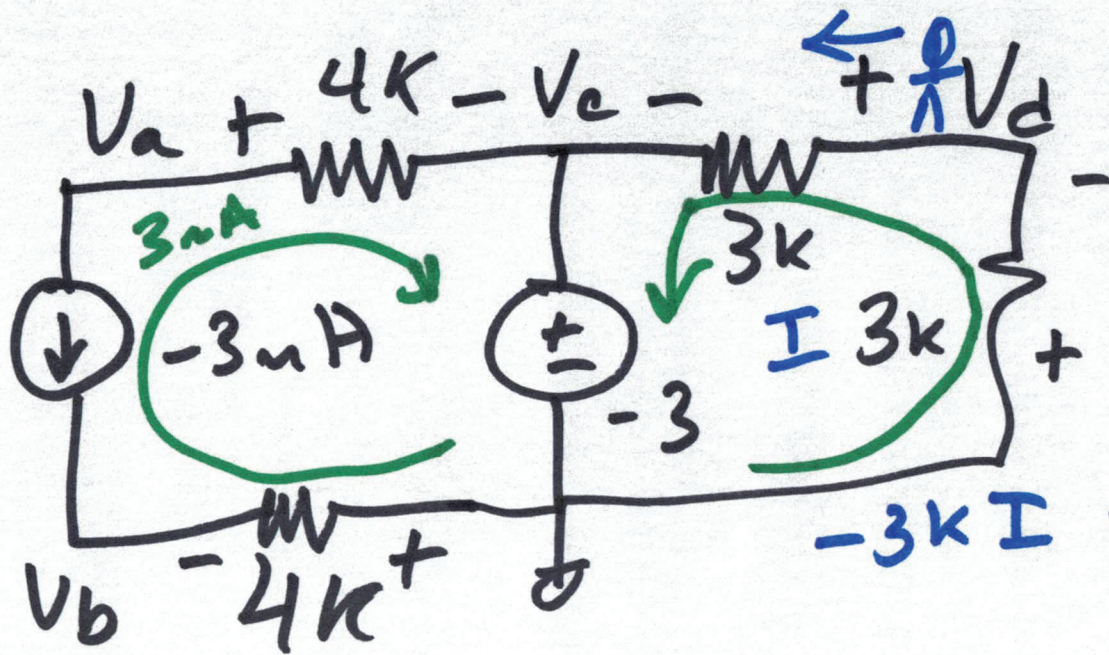

Qc

$$-3kI - (-3) - 3kI = 0$$


$$I = \frac{3}{6k}$$

$$I = \frac{1}{2} mA$$

4k power

$$P = I^2 R$$



$$V = (3nA) 4k = 36mW$$

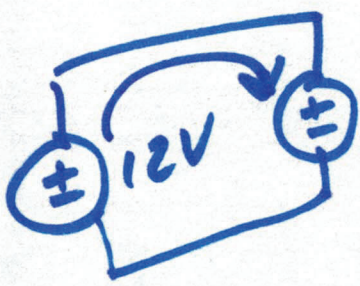

$$3k$$

$$P = I^2 R \rightarrow \left(\frac{1}{2} mA\right)^2 \cdot 3k = \frac{1}{2} \cdot \frac{1}{2} mA \cdot 3k$$

$$= \frac{3}{4} mW$$

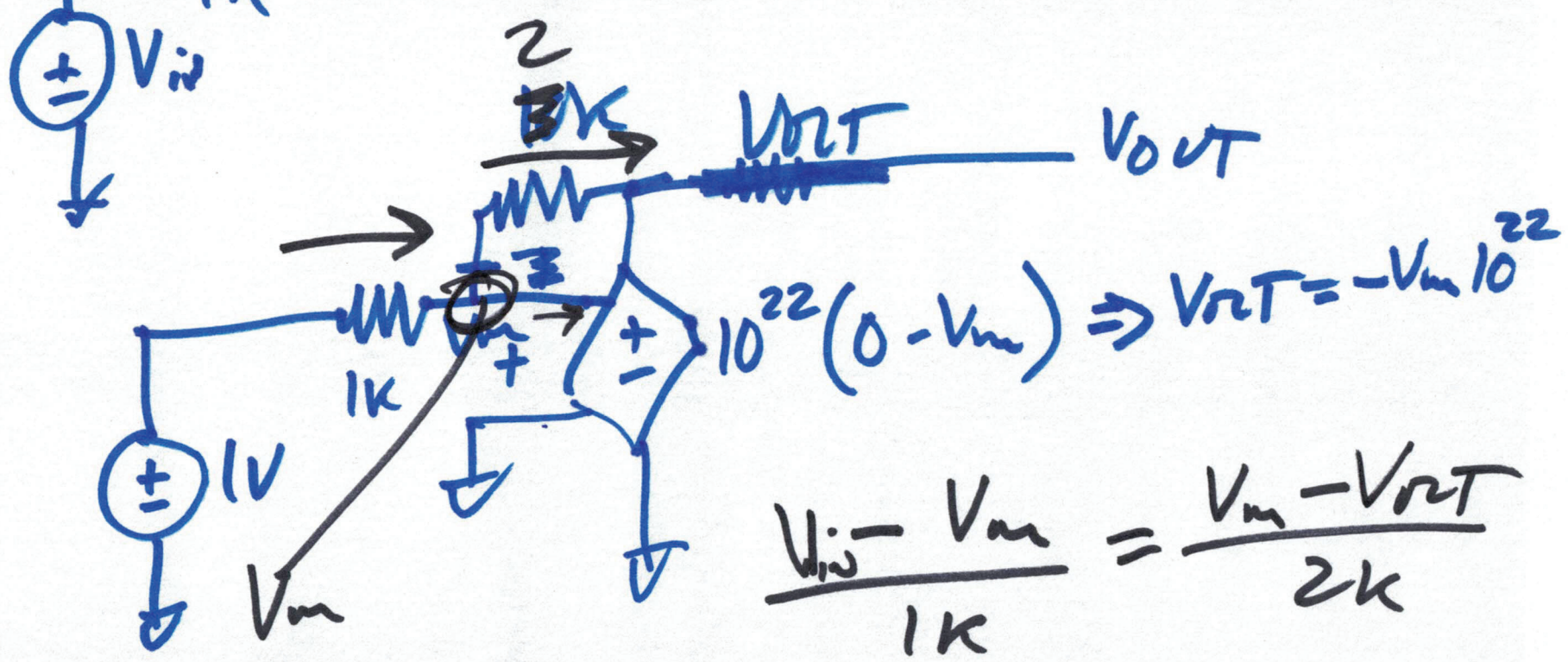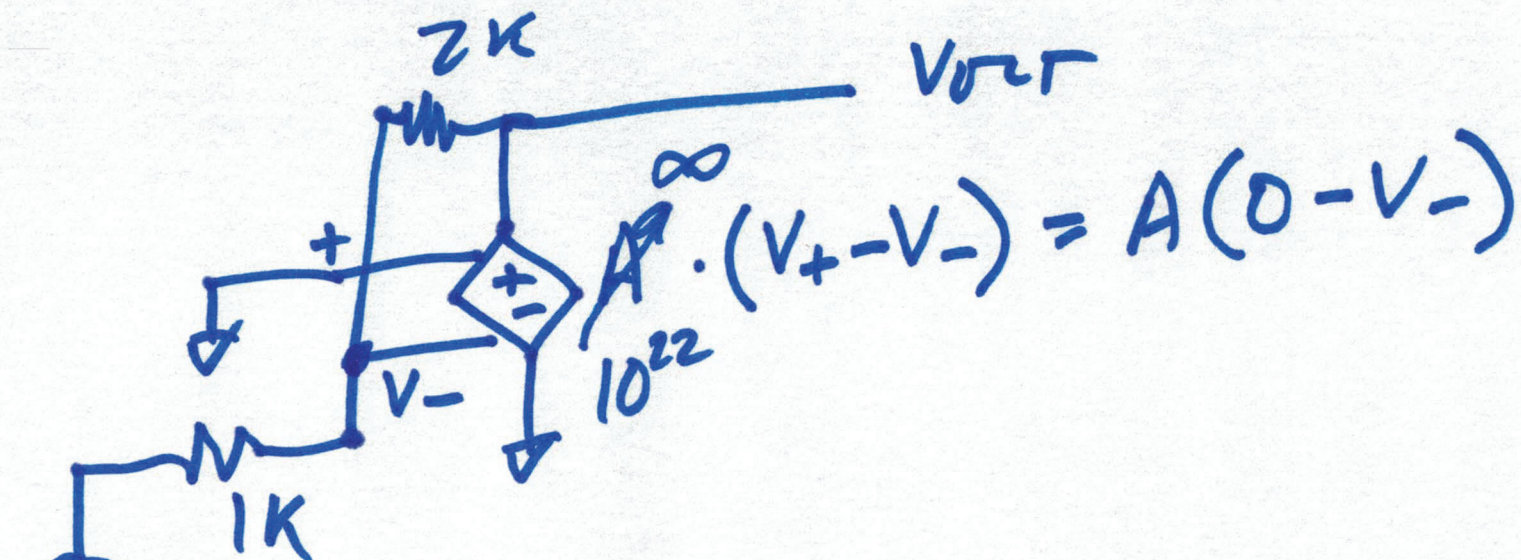

$$\left(\frac{V_{in} - V_m}{1k} \right)^{2k} = \left(\frac{V_m - V_{out}}{2k} \right)^{2k}, \quad V_{out} = -10^{22} \cdot V_m$$

$$2V_m + 2V_{in} - 2V_m = V_m - V_{out} + 2V_m \quad V_m = \frac{V_{out}}{-10^{22}}$$

$$2V_{in} = 3V_m - V_{out}$$

$$V_{out} = \cancel{3} \left(\frac{V_{out}}{-10^{22}} \right) - 2V_{in}$$


$$V_{out} = -2V_{in}$$

Operational - Amplifier

(op-amp)

inverting

V_{in}

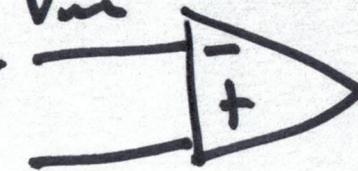

V_{out}

$$= \infty (V_p - V_n)$$

A

non-inverting

V_p