

EE 220 Circuits I

OCT. 9, 2023


Lecture 12

1) determine
NON-INVERTING
INPUT voltage

1) (determine
 V_+)

2) $V_+ = V_-$
 $V_p = V_n$


3) KCL
@ V_-

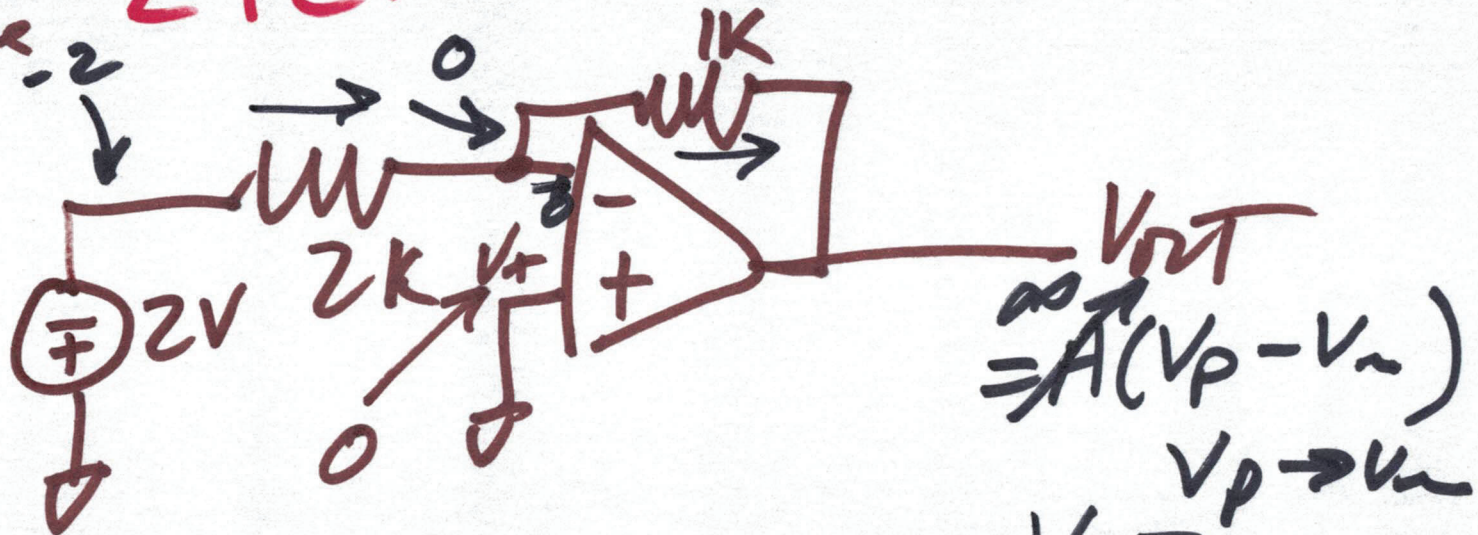

$$\frac{-2 - 0}{2k} = \frac{0 - V_{out}}{1k}$$

$$\frac{1k}{2k} (+2) = +V_{out}$$

$$\boxed{V_{out} = 1V}$$

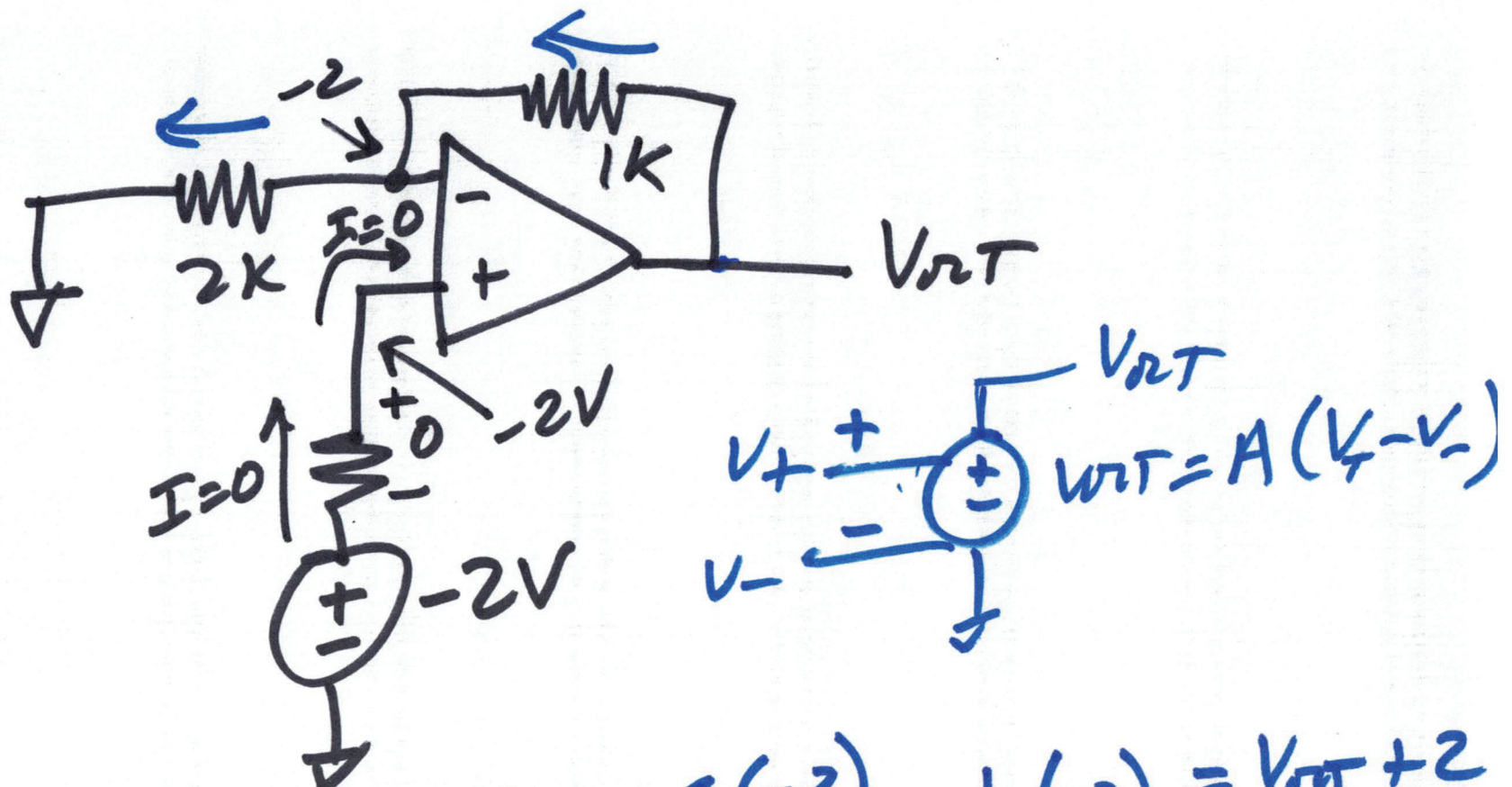


$$\frac{-2 - 0}{2k} = \frac{V_{out} - (-2)}{1k}, \quad \frac{1}{2}(-2) = V_{out} + 2$$

$$-1 = V_{out} + 2$$

$$V_{out} = -3V$$

2)

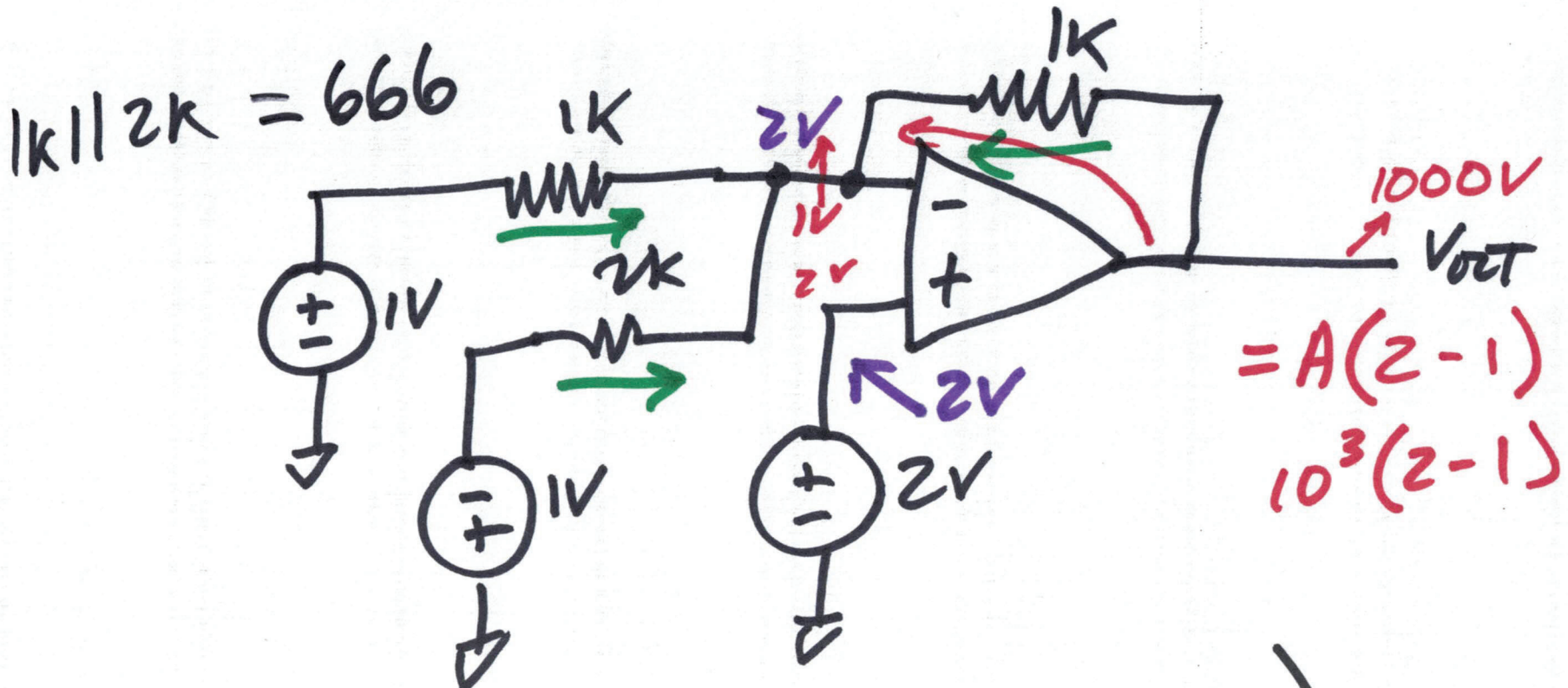


$$2k \left(\frac{1-2}{1k} + \frac{-1-2}{2k} + \frac{V_{out}-2}{1k} \right) = 0$$

$$2(-1) + (-3) + 2V_{out} - 4 = 0$$

$$2V_{out} = 9$$

$$V_{out} = 4.5V$$

Inverting topology

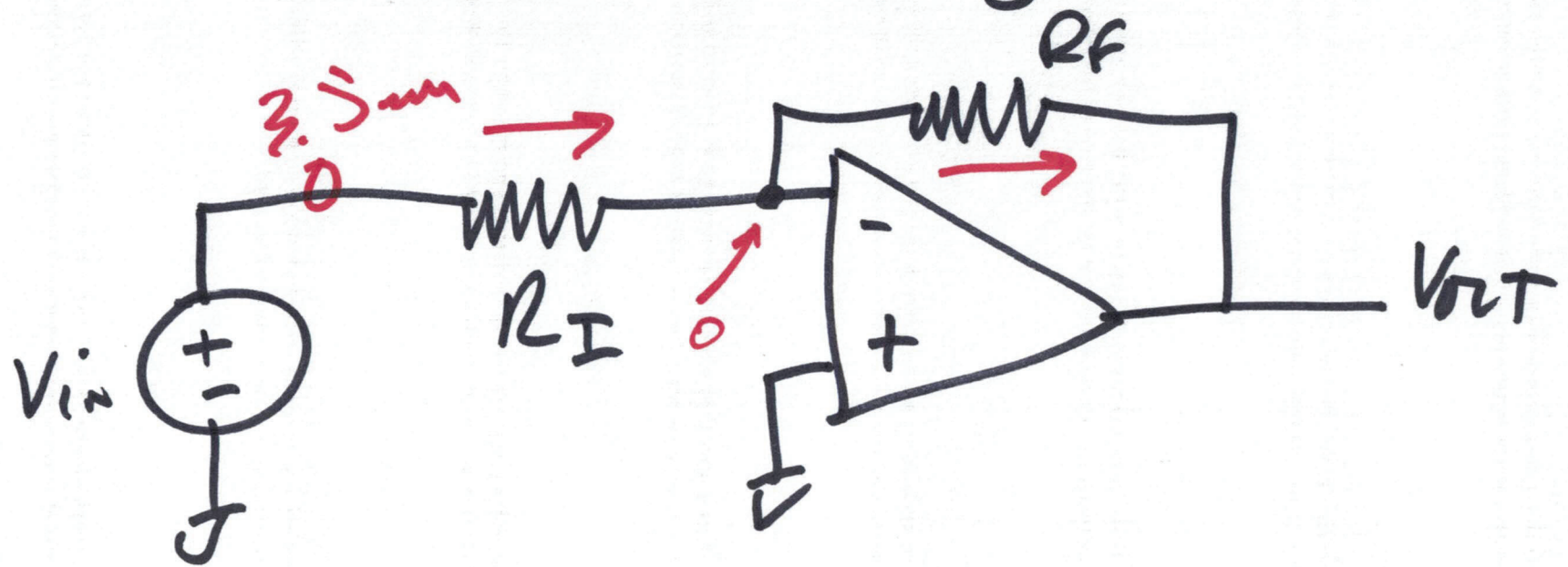


GAIN =

$$\frac{V_{out}}{V_{in}} = -\frac{R_F}{R_I}$$

$$\frac{V_{in} - 0}{R_I} = \frac{0 - V_{out}}{R_F}$$

$$V_{out} = -V_{in} \cdot \frac{R_F}{R_I}$$

NON-INVERTING R_F

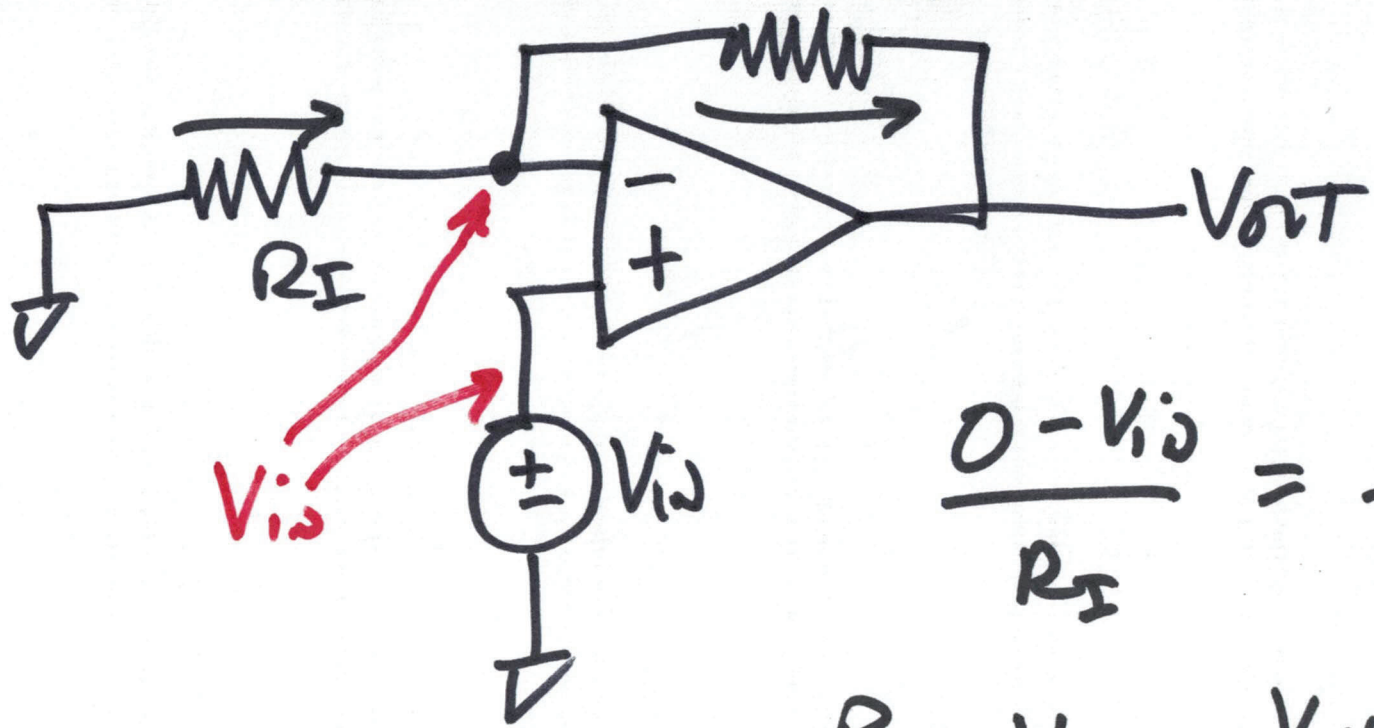


$$\frac{0 - V_{in}}{R_I} = \frac{V_{in} - V_{out}}{R_F}$$

$$-\frac{R_F}{R_I} \cdot V_{in} = V_{in} - V_{out}$$


$$V_{out} = \left(1 + \frac{R_F}{R_I}\right) V_{in}$$
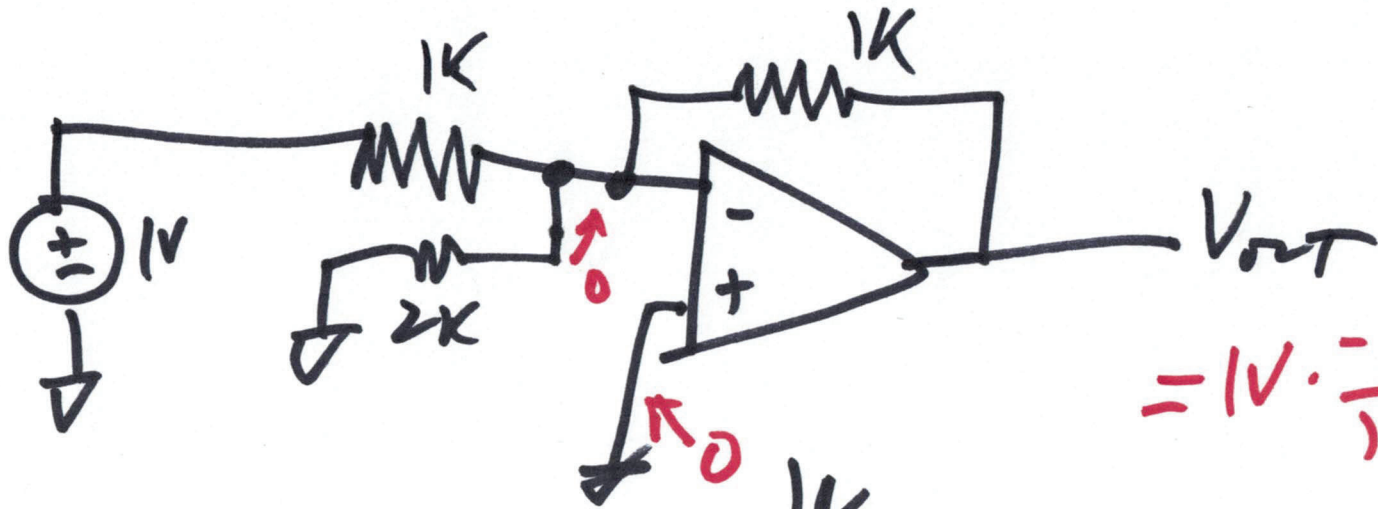
$$\frac{R_I + R_F}{R_I} = \frac{V_{out}}{V_{in}} = \left(1 + \frac{R_F}{R_I}\right)$$




$$= 1V \cdot \frac{-1k}{1k}$$

$$= -1V$$

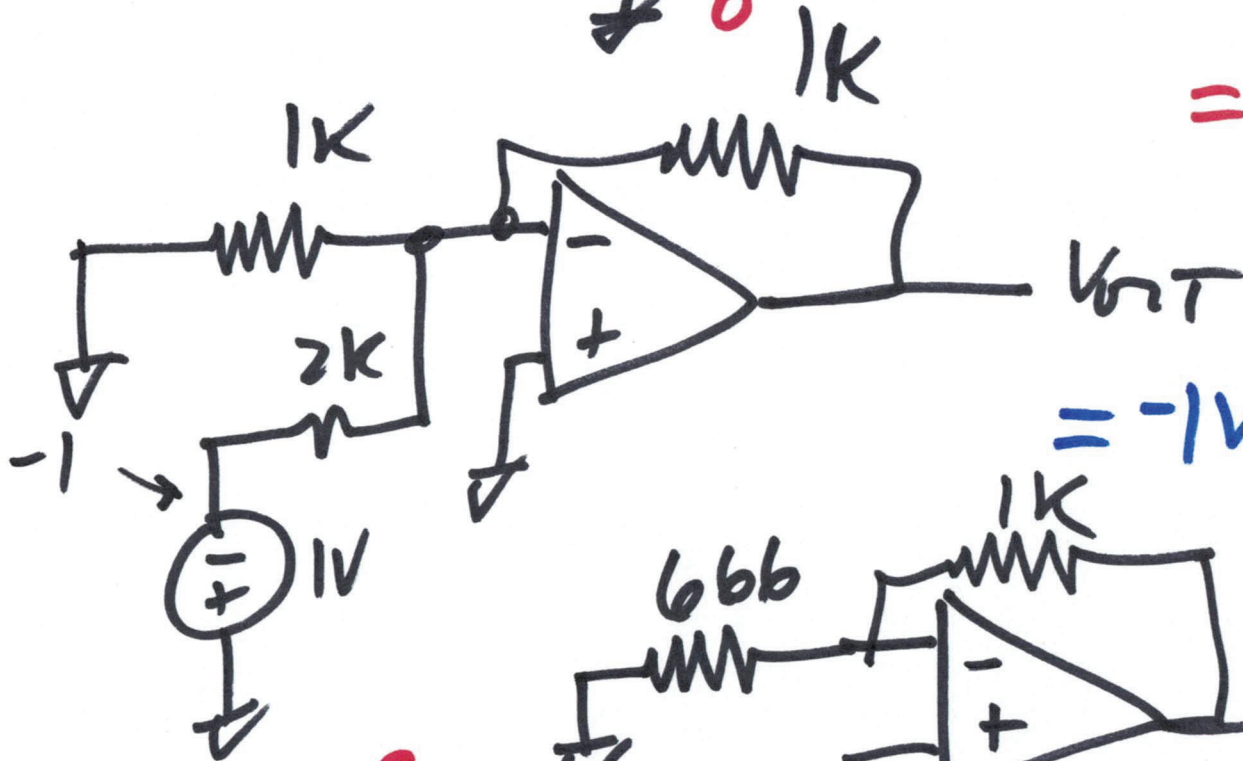
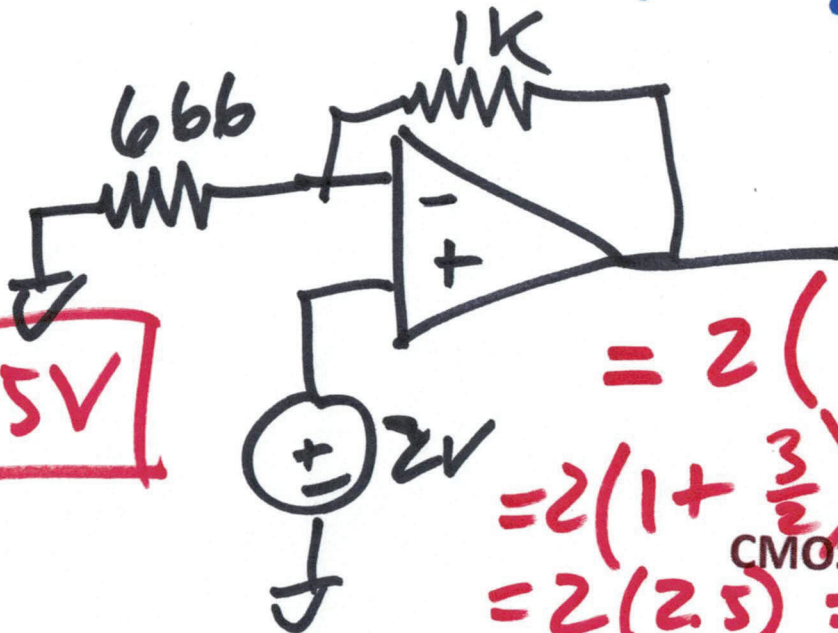
$$= -1V \cdot \frac{-1k}{2k} = +\frac{1}{2}V$$



$$= 2 \left(1 + \frac{1k}{666} \right)$$

$$= 2 \left(1 + \frac{3}{2} \right) \frac{2}{2}k$$

$$= 2(2.5) = 5V$$

$$V_{out} = -1 + \frac{1}{2} + 5 = 4.5V$$

6)