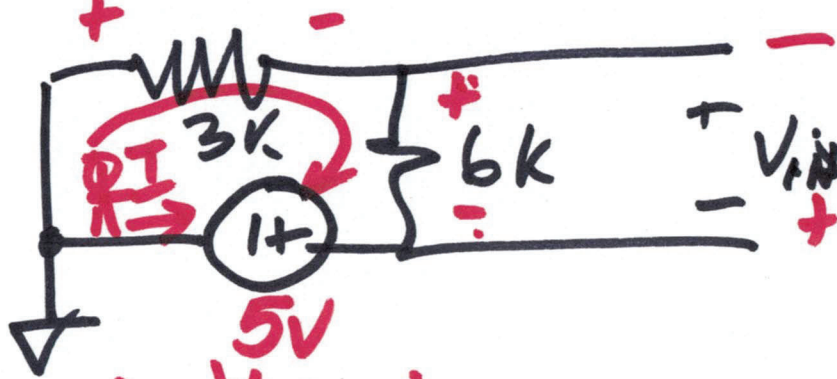


EE 220 Circuits I

OCT. 11, 2023

Lecture 13, 2023

$$5 + \frac{5 \cdot 10}{3} \cdot \frac{15}{3} + \frac{50}{3} = \frac{65}{3} \text{ V}$$




$$5 + I \cdot 6k + I \cdot 3k = 0$$


$$I = -\frac{5}{9} \text{ mA}$$

$$V_{in} = I \cdot 6k,$$

$$V_{in} = -\frac{5}{9} (6)$$

$$V_{in} = -\frac{10}{3} \text{ V}$$

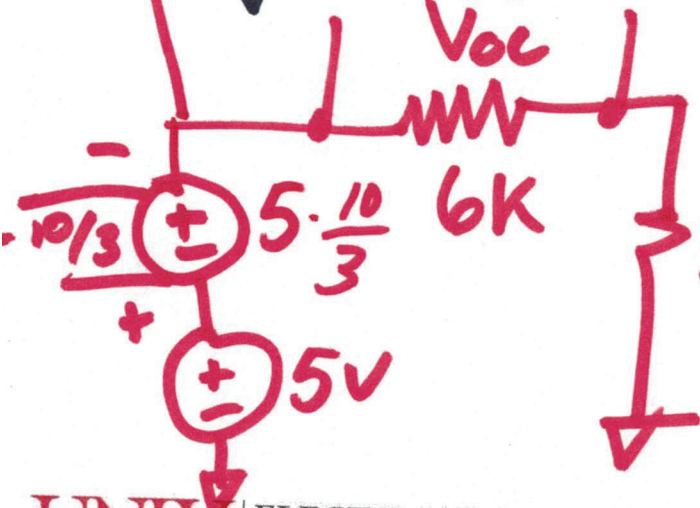

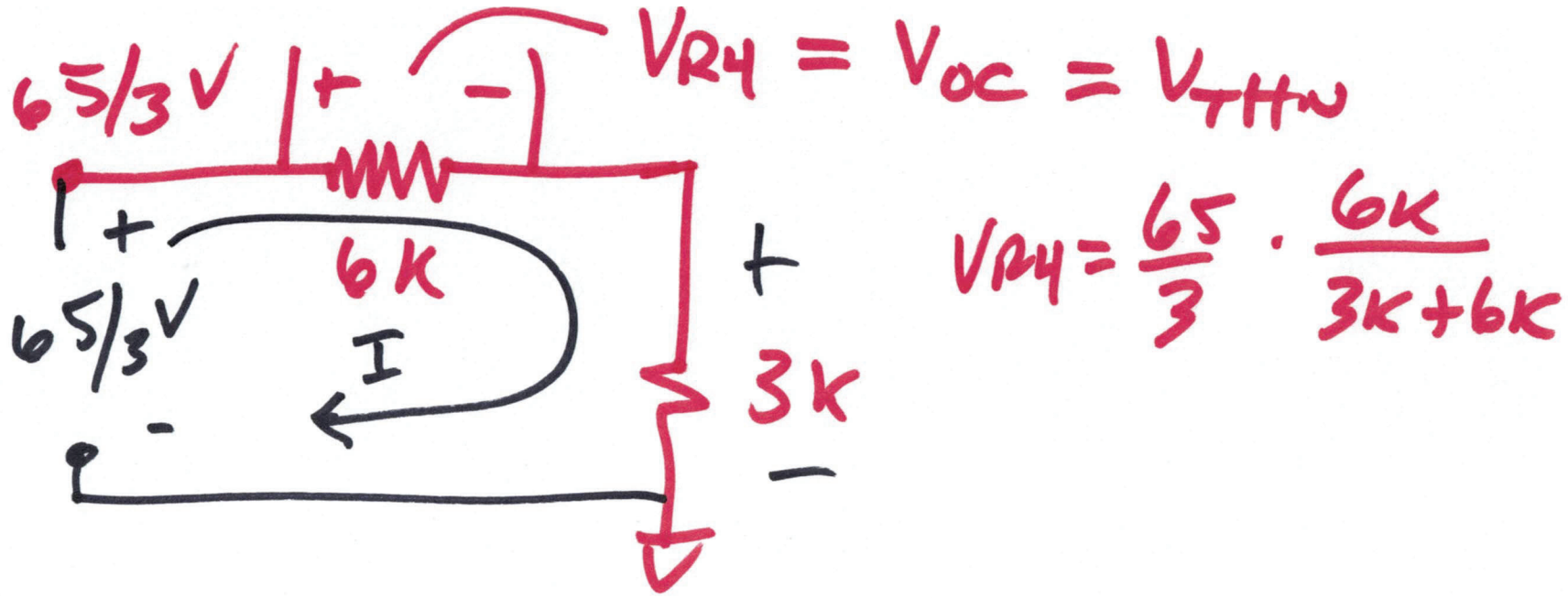




$$V_{R4} = \frac{65}{3} \cdot \frac{6 \text{ k}}{3 \text{ k} + 6 \text{ k}}$$

$$\frac{65}{3} - 6 \text{ k} I - 3 \text{ k} I = 0$$

$$I = \frac{65}{3.9} \text{ mA}$$

$$V_{R4} = 6 \text{ k} I = 6 \text{ k} \cdot \frac{65}{3.9} \text{ mA} = \frac{130}{9} \text{ V} = 14 \frac{4}{9} \text{ V}$$

$$3k // 4.5k = R_{TH}$$

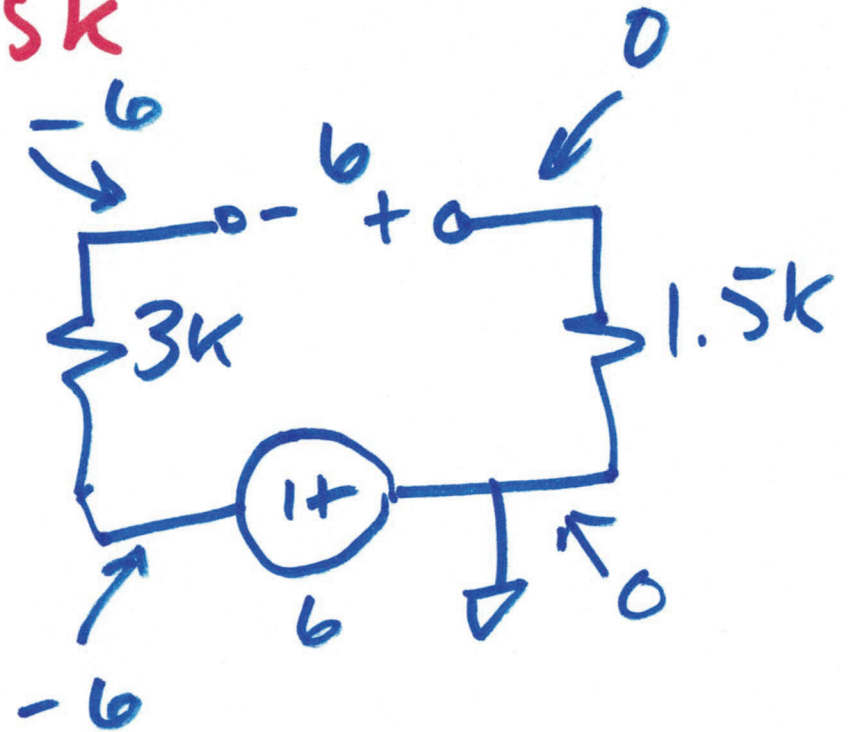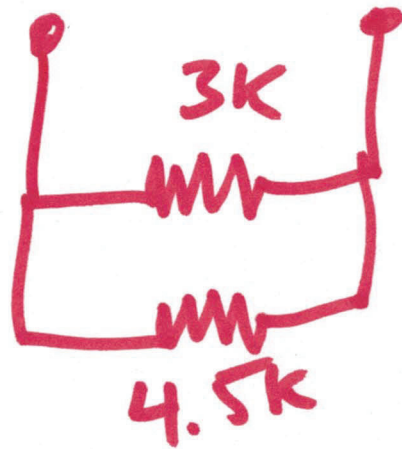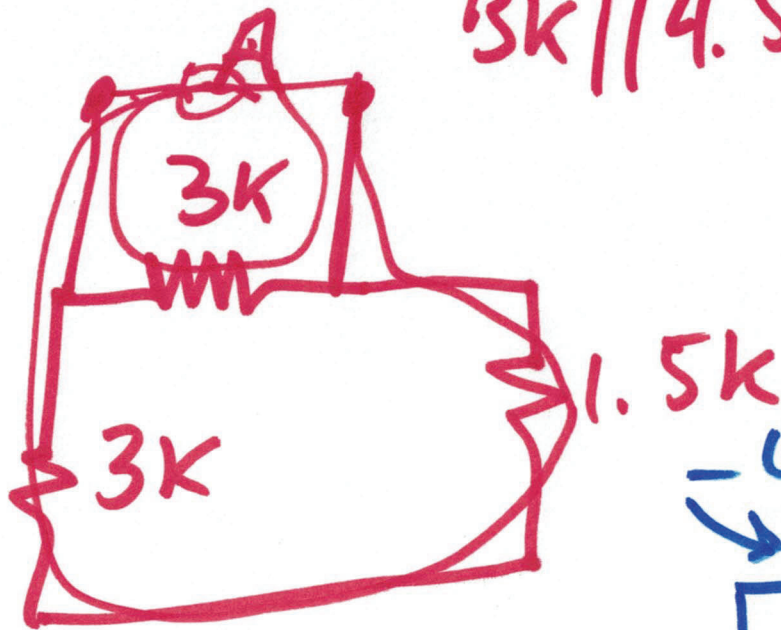

3)


NAME: _____

Closed book and notes.

Show your work for credit and put a box around your answers.

$$\frac{V_{bot} I}{R} = I \downarrow \begin{matrix} V_{bot} \\ + \\ - \\ V_{bot} \end{matrix}$$

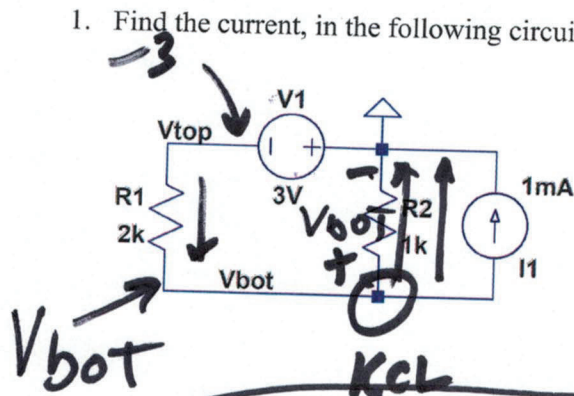1. Find the current, in the following circuit, that flows in R2. (10 points)






$$1 \text{ mA} + \frac{V_{bot}}{1k} = \frac{-3 - V_{bot}}{2k}$$


$$2V + 2V_{bot} = -3 - V_{bot}$$

$$I_{R2} = \frac{-5}{3 \cdot 1k} = \frac{-5 \mu\text{A}}{3}$$

$$V_{bot} = \frac{-5V}{3}$$

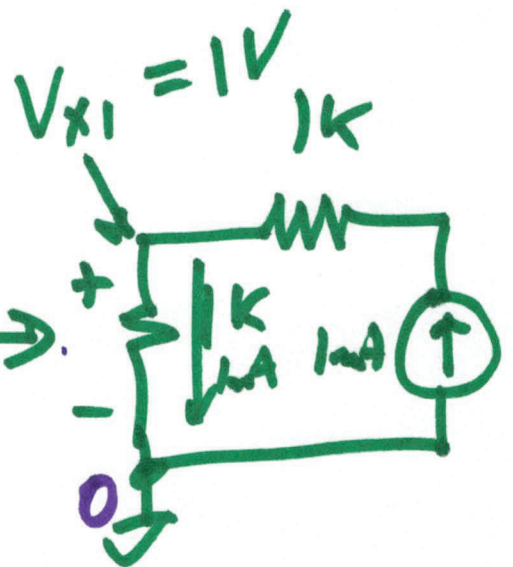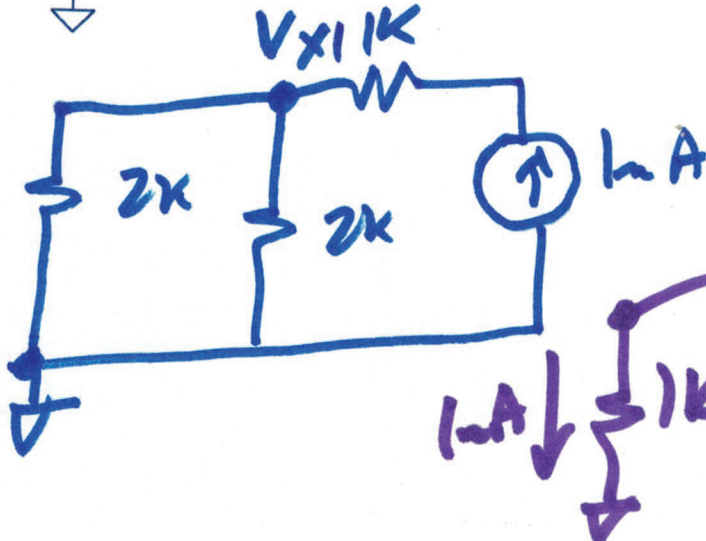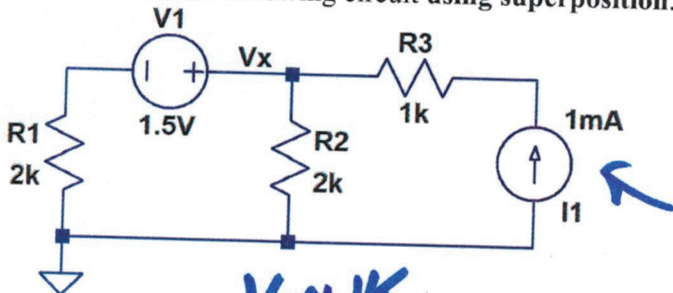2. Find V_x in the following circuit using superposition. (10 points)



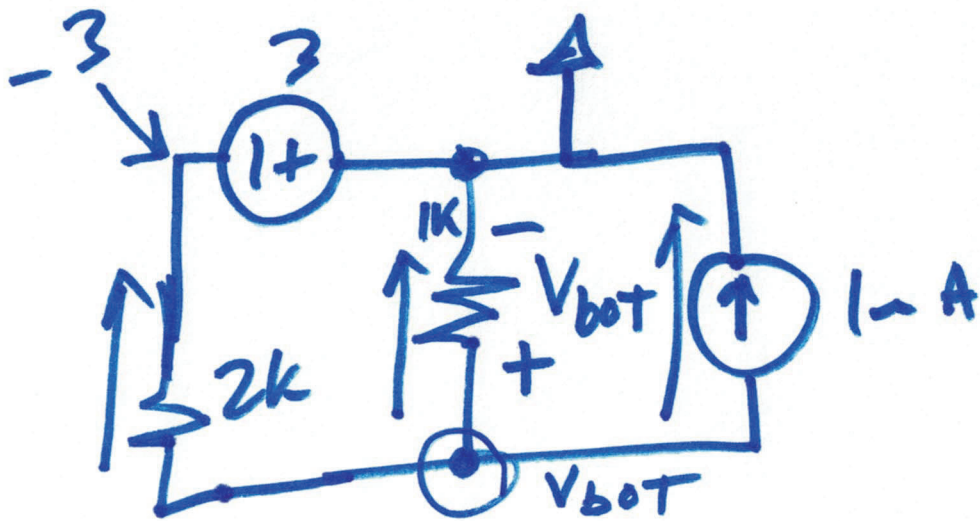


KCL

$$0 = 1\text{mA} + \frac{V_{boot} - 0}{1\text{k}} + \frac{V_{boot} - (-3)}{2\text{k}}$$

$$V_x = 1 + 0.75$$

$$V_x = 1.75\text{V}$$

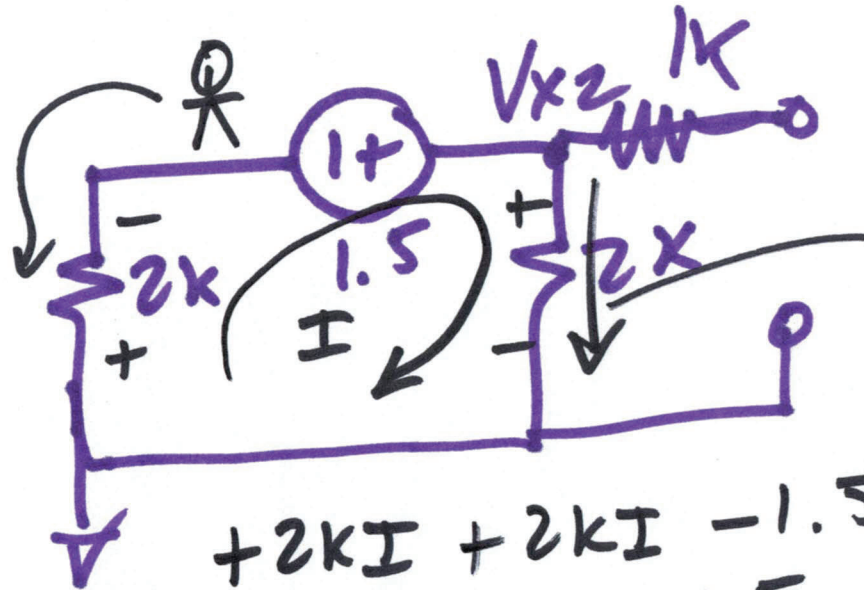

$$V_{x2} = 2\text{k} \cdot \frac{3}{8}\text{mA}$$


$$= \frac{6}{8}\text{V}$$

$$= \frac{3}{4}\text{V}$$

$$+2\text{kI} + 2\text{kI} - 1.5 = 0$$

$$\frac{3}{8}\text{mA} \cdot I = \frac{1.5}{4\text{k}} = \frac{1.5}{4}\text{mA}$$

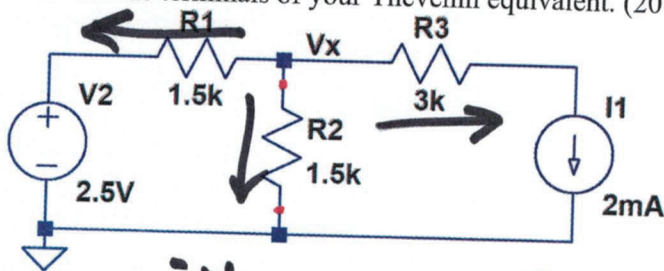3. Find the voltage V_x in the circuit seen below. Then find the Thevenin equivalent circuit, with R_2 removed, at the terminals marked by dots. Show that your Thevenin circuit is correct by comparing the value you calculated for V_x to the one you get when you put R_2 across the terminals of your Thevenin equivalent. (20 points)




$$2\text{mA} + \frac{V_x}{1.5\text{k}} + \frac{V_x - 2.5}{1.5\text{k}} = 0$$

with R_2 in

$$0 = 3\text{V} + V_x + V_x - 2.5$$

$$2V_x = -\frac{1}{2}$$

$$V_x = -\frac{1}{4}$$

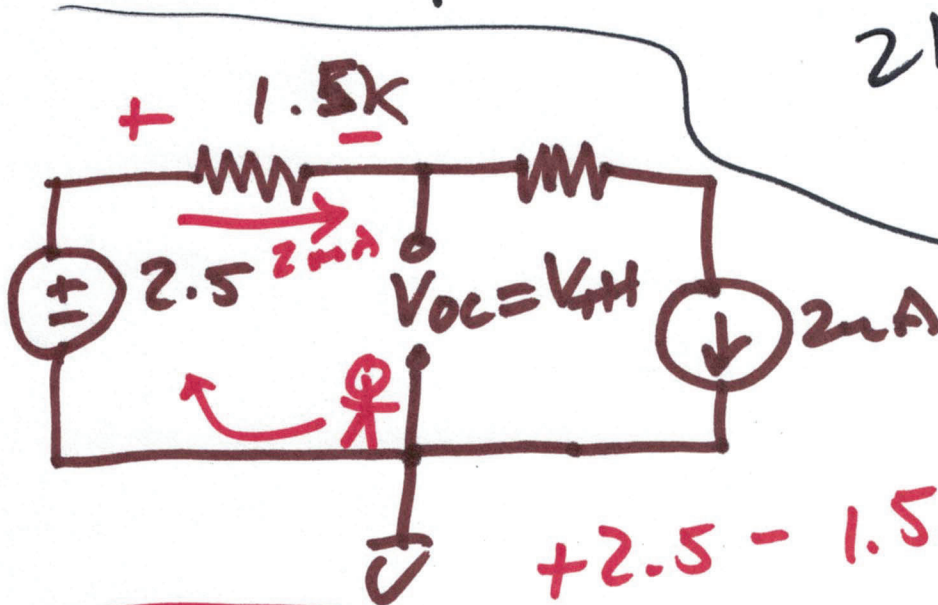


$$+2.5 - 1.5\text{k}(2\text{mA}) = 0 \text{ Voc}$$

$$V_{oc} = 2.5 - 3$$


$$V_{TH} = V_{oc} = -\frac{1}{2}\text{V}$$

$$R_{TH} = 1.5\text{k}$$

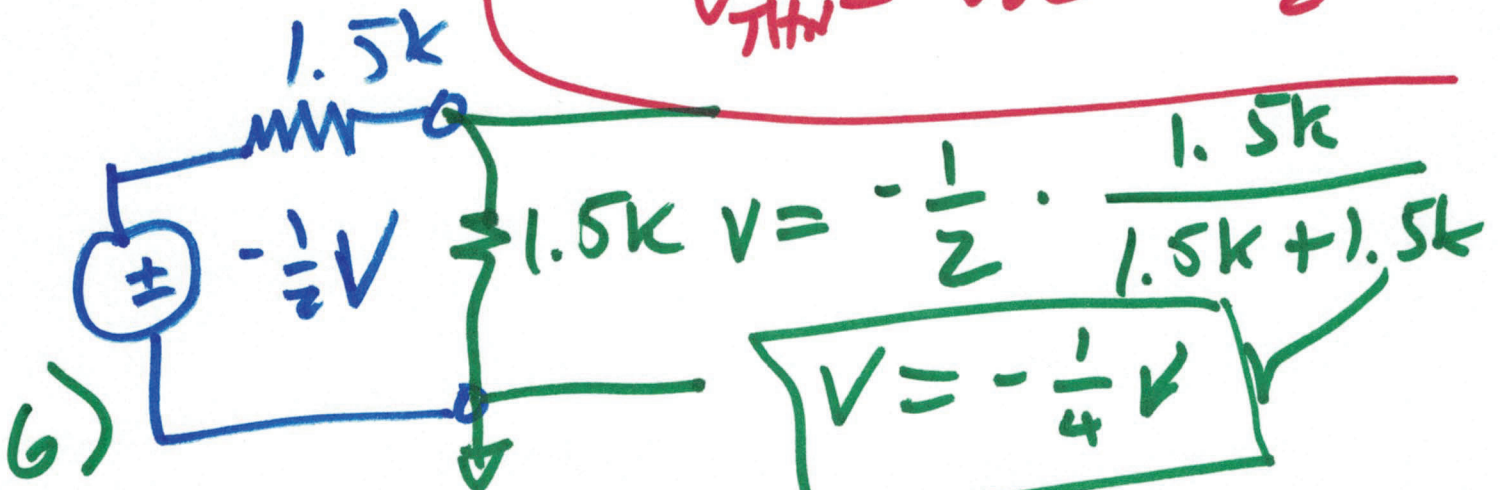

$$V = -\frac{1}{4}\text{V}$$

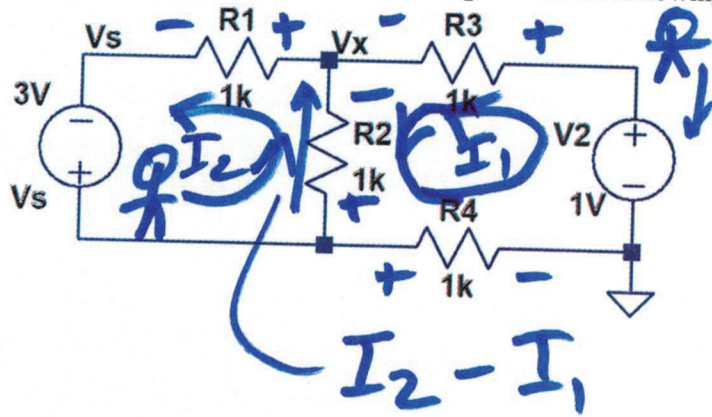4. Using mesh analysis find the voltage V_x in the following circuit. (20 points)




$$\textcircled{1} \quad -1k(I_2 - I_1) - 1kI_2 + 3 = 0$$

$$\textcircled{2} \quad -1V + 1kI_1 - 1k(I_2 - I_1) + 1kI_1 = 0$$

7)

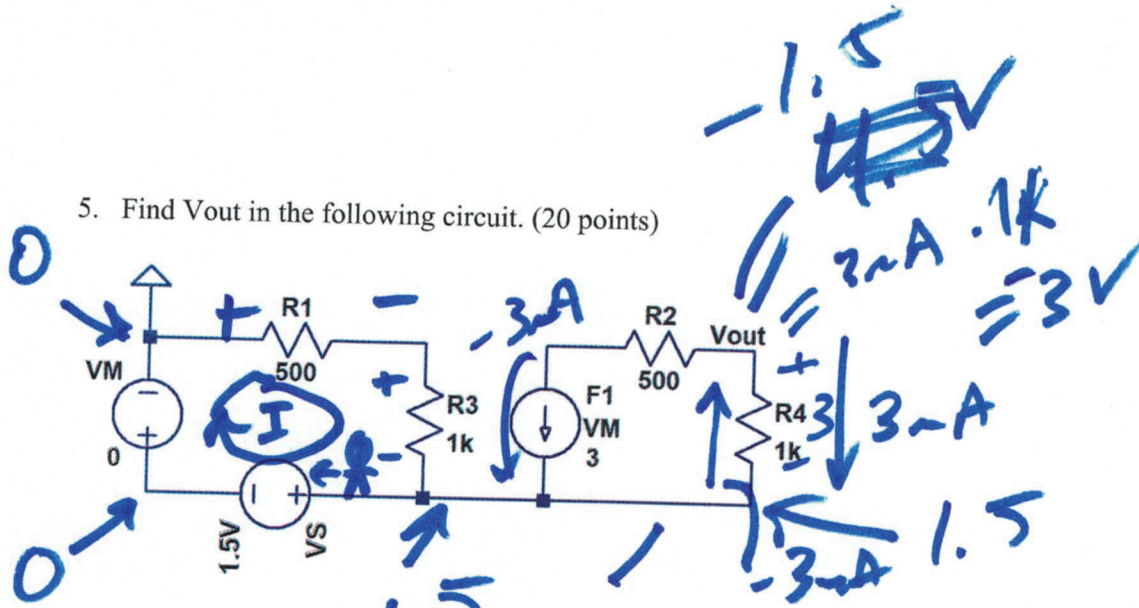5. Find V_{out} in the following circuit. (20 points)





$$-1.5 - 500I - 1kI = 0$$

$$I = \frac{-1.5}{1.5k} = -1\mu A$$


$$V_{out} = 1.5 + 3$$

$$V_{out} = \boxed{4.5V}$$

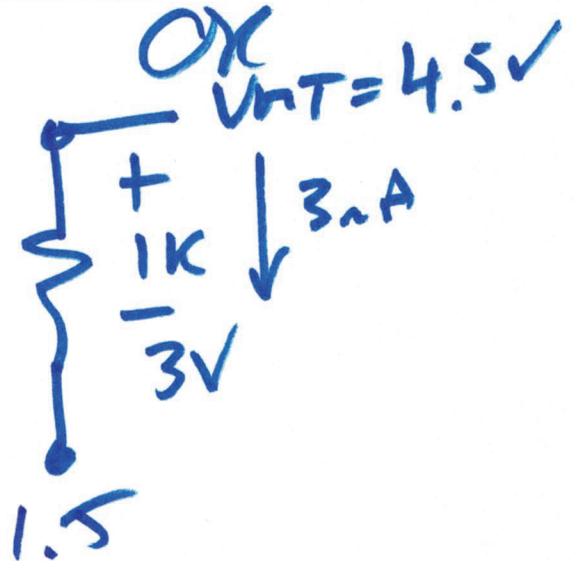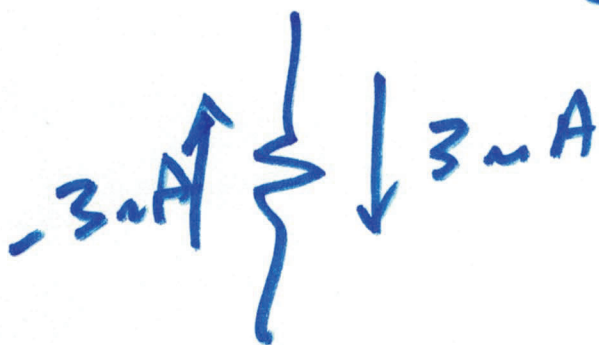

8)

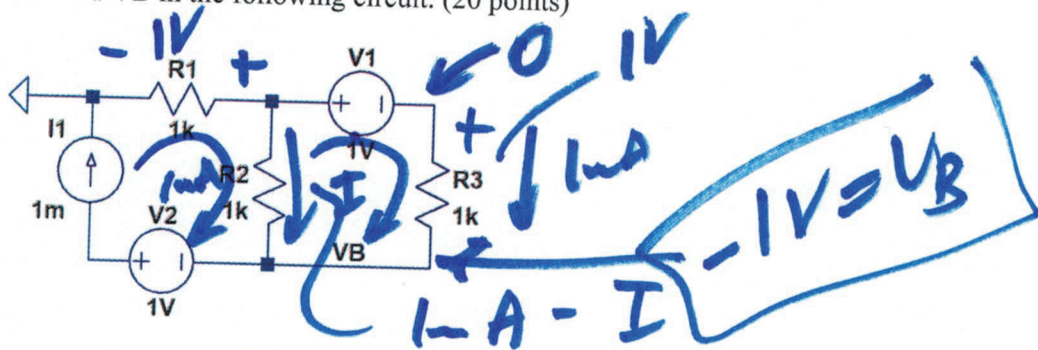6. Find V_B in the following circuit. (20 points)



9)