


# EE 220 CIRCUITS I

Lecture 14

October 18, 2023

Capacitors

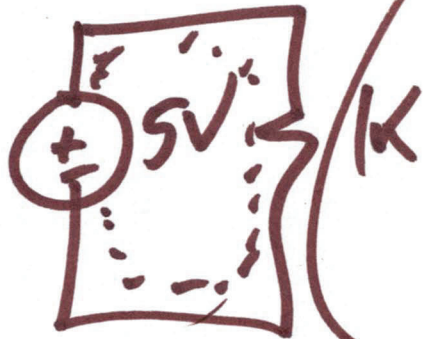free space  
 $\epsilon_0 = 8.85 \times 10^{-12} \frac{C^2}{N \cdot m^2}$   
 $C_{\text{cond}} = \frac{\epsilon}{\epsilon_0}$




$$C = \frac{A \cdot \epsilon}{t}$$

Capacitance to store charge





CHARGE, Q

$$CV = Q$$

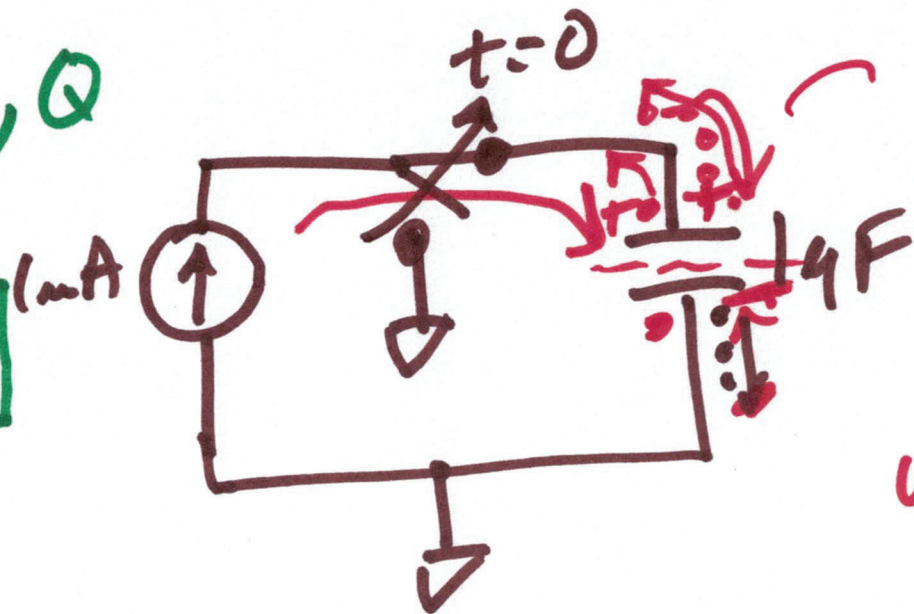



displacement current

conduction

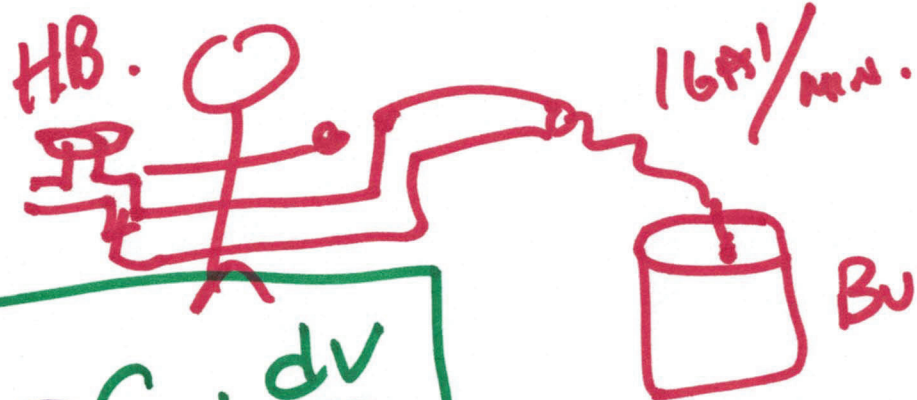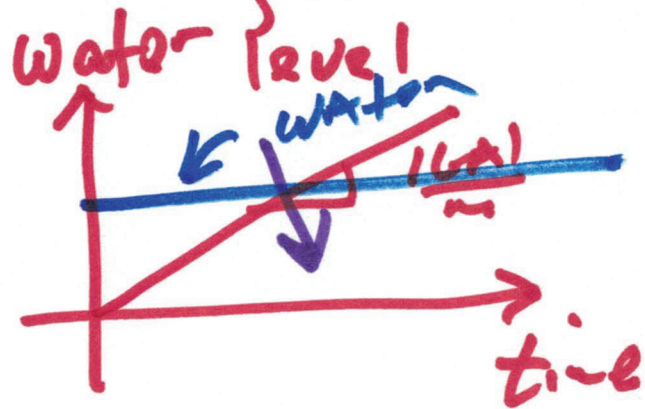


$$I = C \cdot \frac{dv}{dt}$$


constant current

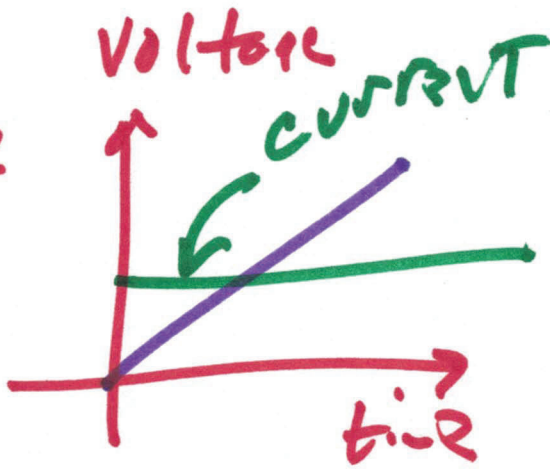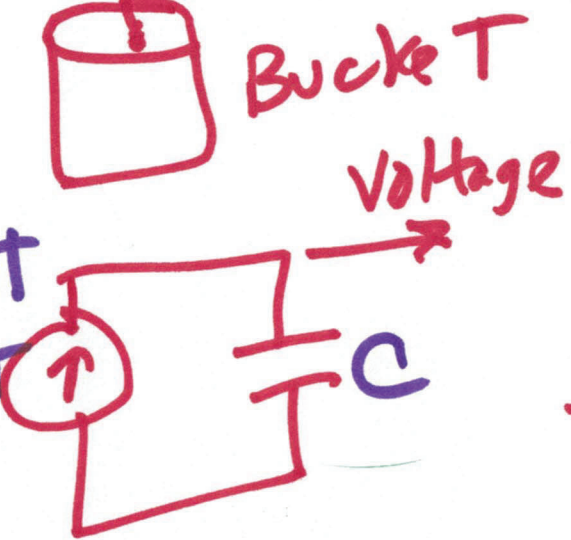

$$CV = Q$$

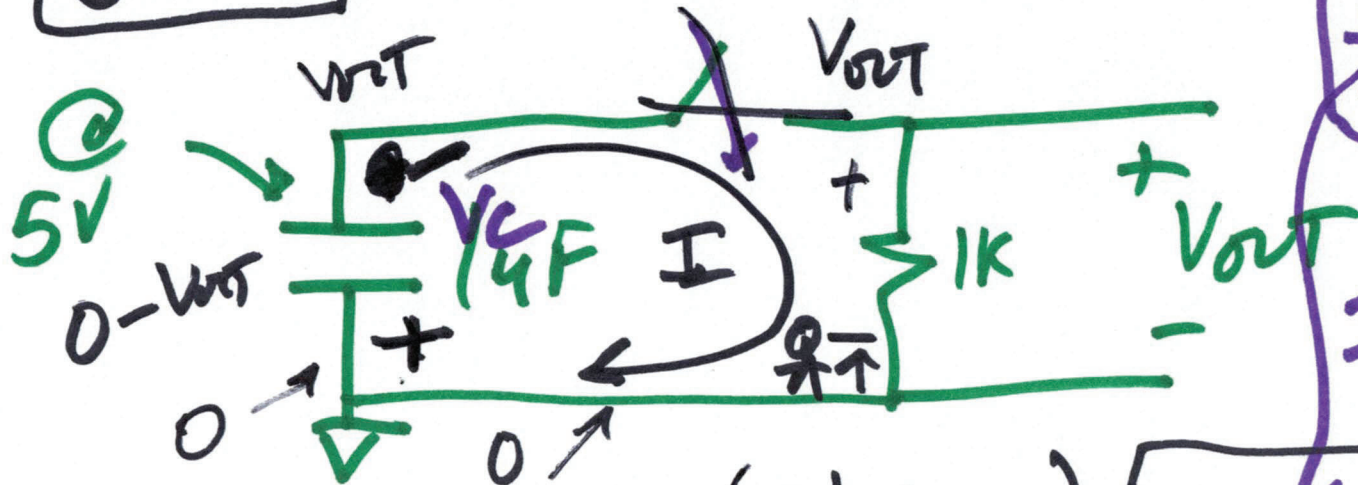

$$I = \frac{C dv_c}{dt}$$

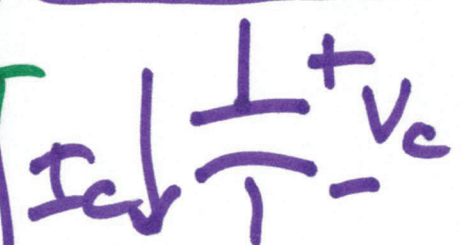

$$14 \cdot 5 = 54 \text{ C (charge)}$$

↑  
Coulombs



$$+1kI + (-V_{out}) = 0$$

$$V_c = -V_{out}$$

$$1k C \frac{dv_c}{dt} - V_{out} = 0$$

$$(1k) \cdot C \cdot \frac{d(-V_{out})}{dt} = V_{out}$$

$$\frac{dV_{out}}{V_{out}} = -RC dt$$

3)

$$\frac{dV_{out}}{V_{out}} = \int_0^t -\frac{1}{RC} dt$$

↙  $V_{init}$


ln c - ln b  
 $\ln \frac{a}{b}$

$$\ln V_{out}(t) - \ln V_{init} = -\frac{1}{RC} \Big|_0^t$$

$$e^{\ln \frac{V_{out}(t)}{V_{init}}} = e^{-RC t}$$

$$V_{out}(t) = V_{init} e^{-t/RC}$$

A)

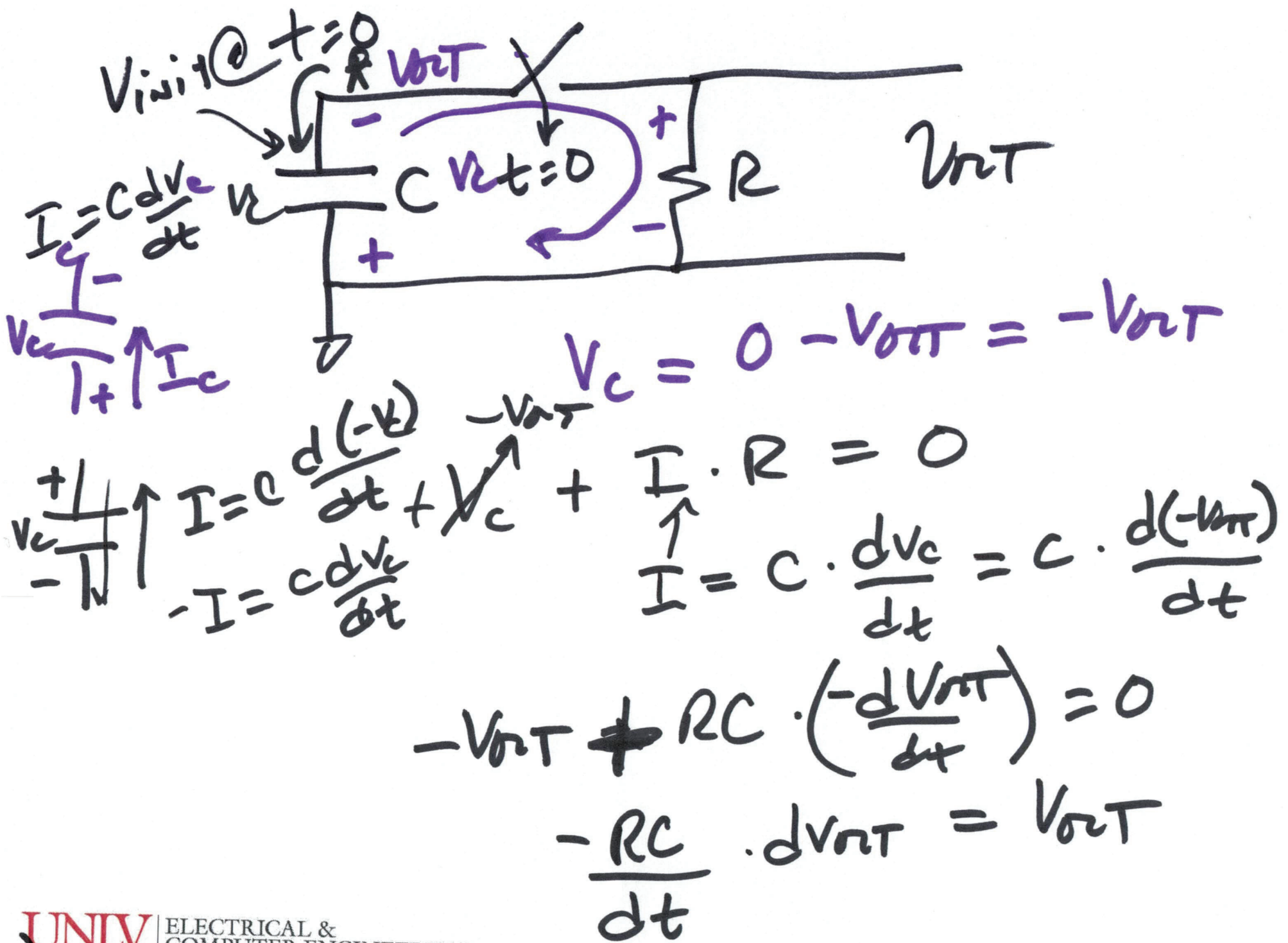

$$\int_a^b \frac{dx}{x} \Rightarrow \ln x \Big|_a^b$$

$$\int_{V_{init}} \frac{V_{out}(t)}{dV_{out}} = \int_0^t -\frac{dt}{RC}$$


$$\ln a - \ln b = \ln \frac{a}{b}$$

$$\ln x \Big|_{V_{init}}^{V_{out}(t)} = -\frac{t}{RC}$$

$$\ln V_{out}(t) - \ln V_{init} - \frac{1}{RC} \int_0^t dt$$

$$e^{-\frac{t}{RC}} = \ln \frac{V_{out}}{V_{init}}$$

$$V_{out}(t) = V_{init} e^{-t/RC} = \frac{1}{RC} t \Big|_0^t = \frac{1}{RC} (t-0)$$

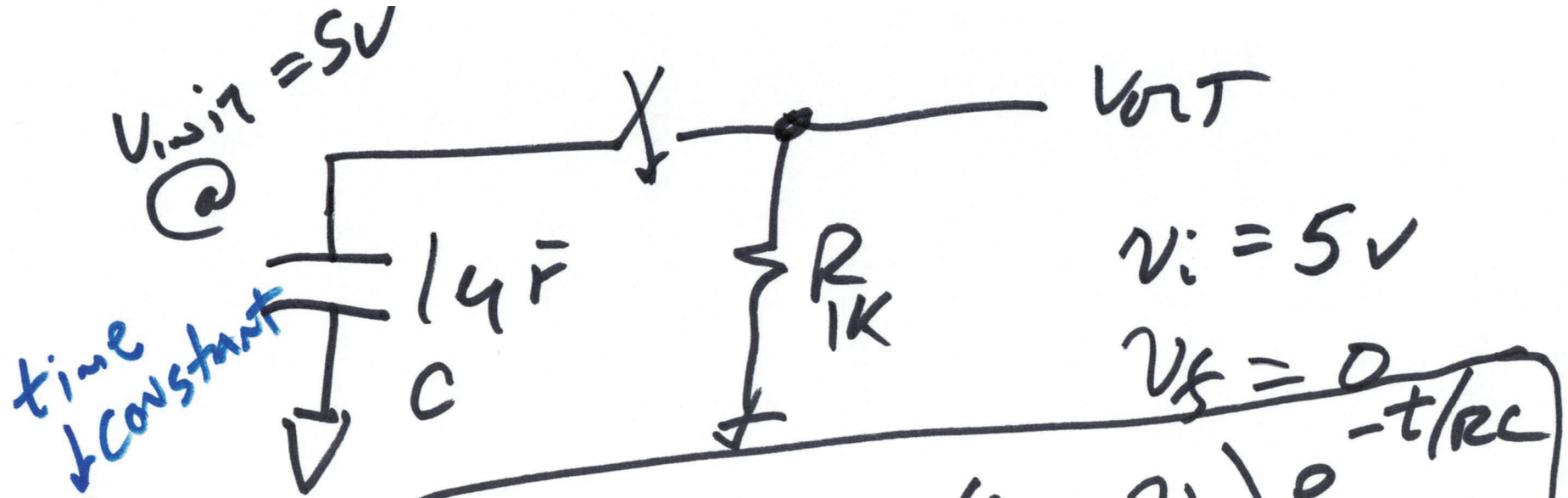

$$v_{out} = v_f + (v_i - v_f) e^{-t/RC}$$

$RC =$   
 $10^{-6} \cdot 10^3$   
 $= 10^{-3}$   
 $= 1ms$

$$v_{out} = 5 e^{-t/1ms}$$

five  
equation  
time constant

$5e^{-1} = \frac{5}{e} = 5.37\%$

5T 99.7%

