
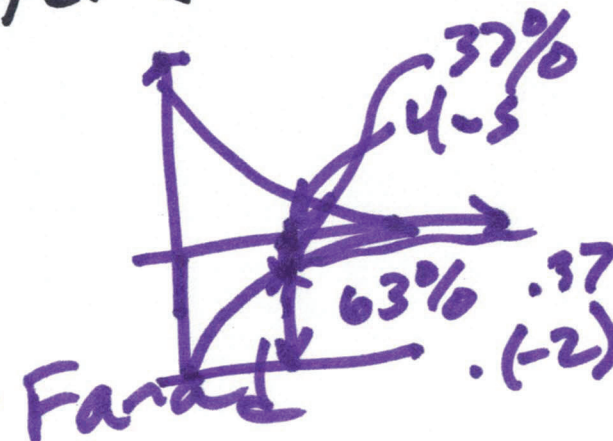


# EE 220 circuits I

## October 23, 2023
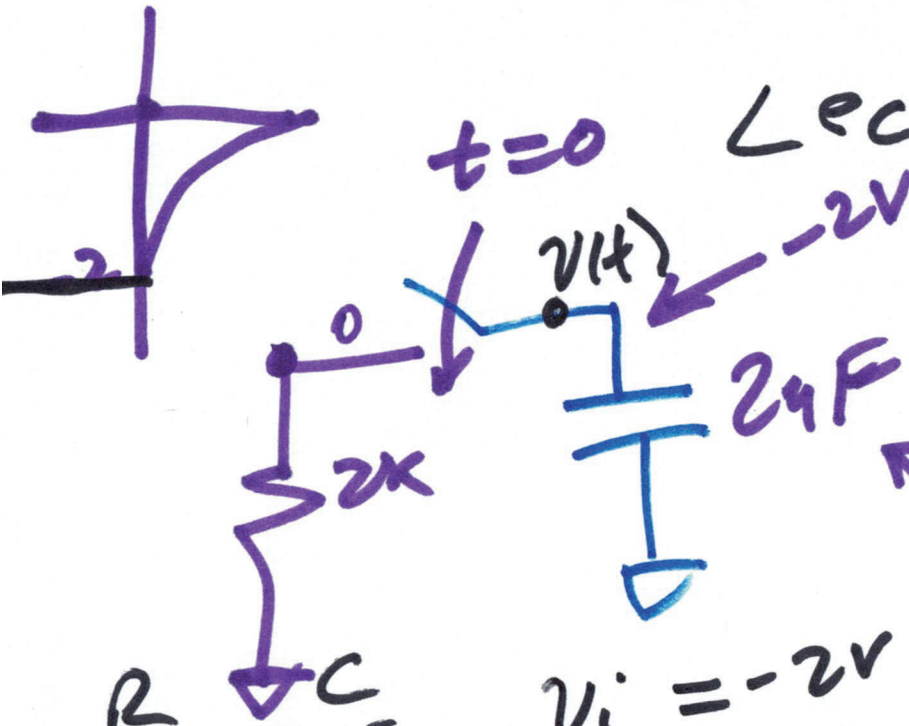
### Lecture 15

atto =  $10^{-18}$   
 pico =  $10^{-12}$   
 femto =  $10^{-15}$   
 nano =  $10^{-9}$   
 micro =  $10^{-6}$   
 milli =  $10^{-3}$



$v_i = -2V$      $v_f = 0$

$R = 2k$   
 $C = 24F$   
 $4 \cdot 10^3 \cdot 10^{-6}$   
 $4 \cdot 10^{-3}$

$$v(t) = v_f + (v_i - v_f) e^{-t/\tau}$$

$$= -2 e^{-t/4\mu s}$$


$\tau = 4\mu s$

$$v(t) = -2 e^{-t/4\mu s}$$


$$1\tau, t = 4\mu s$$

$$= -2 e^{-4\mu s / 4\mu s} = -2 e^{-1}$$
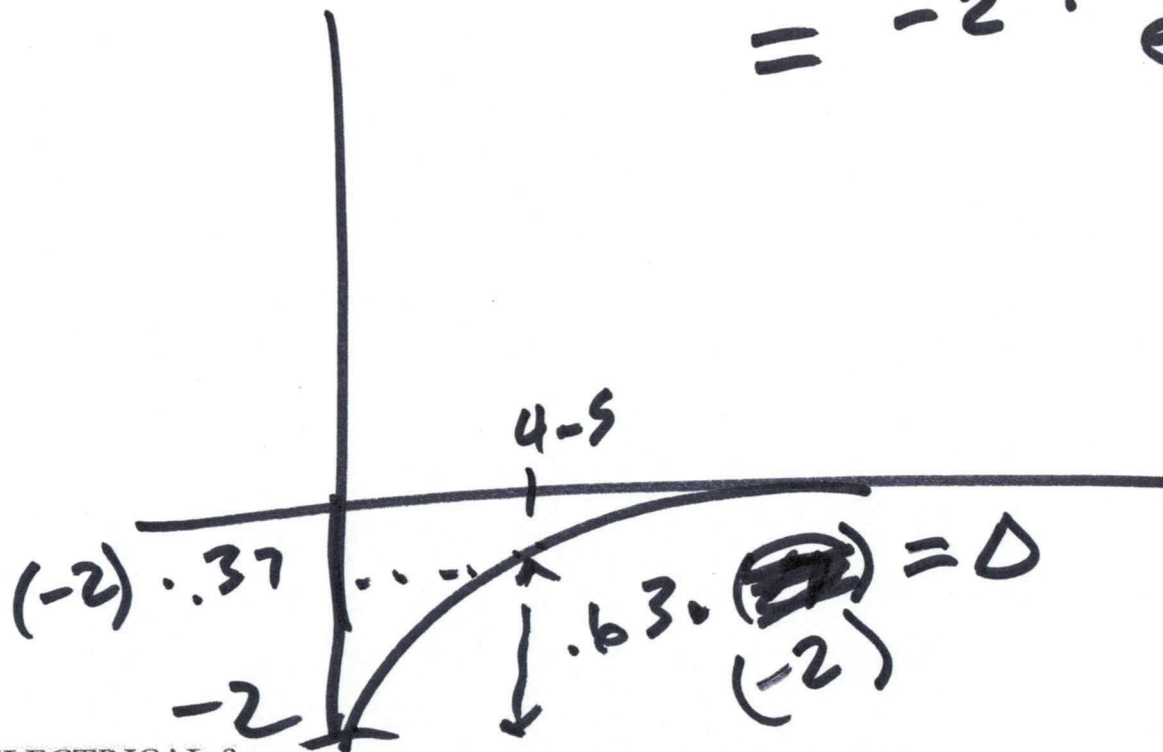
$$= -2 \cdot \frac{1}{e} \leftarrow 0.37$$




# XY MORON

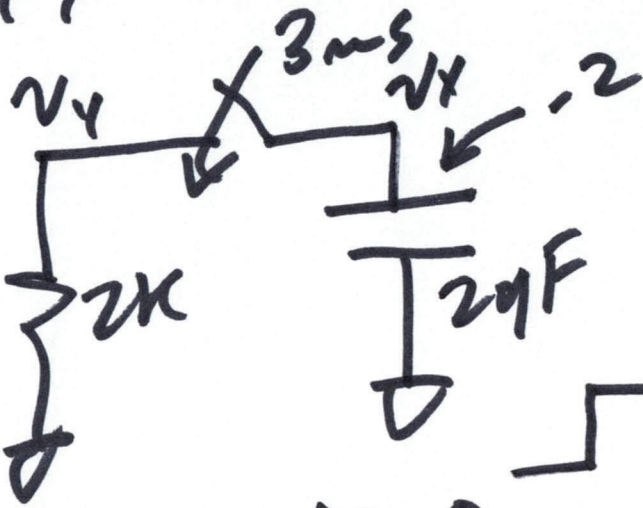

unit step  
 $u(t) = 1 \quad t > 0$   
 $u(t) = 0 \quad t < 0$

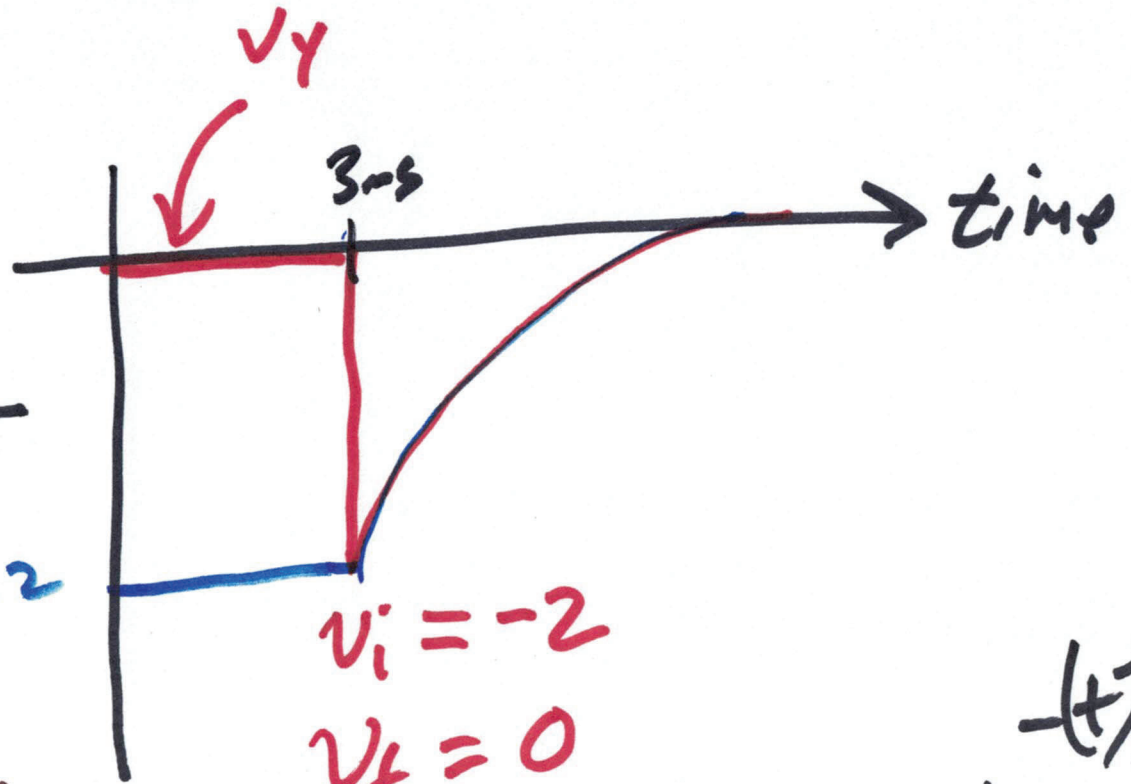$v_y = 0, t < 3ms$   
 $v_x = -2, t < 3ms$



$v_i = -2$   
 $v_f = 0$


$$v(t) = v_f + (v_i - v_f)e^{-\frac{(t-t_i)}{\tau}}$$

$$v(t) = -2e^{-\frac{(t-3ms)}{4ms}} \cdot u(t-3ms)$$

$t \geq 3ms$

$v(t)_{x,y}$



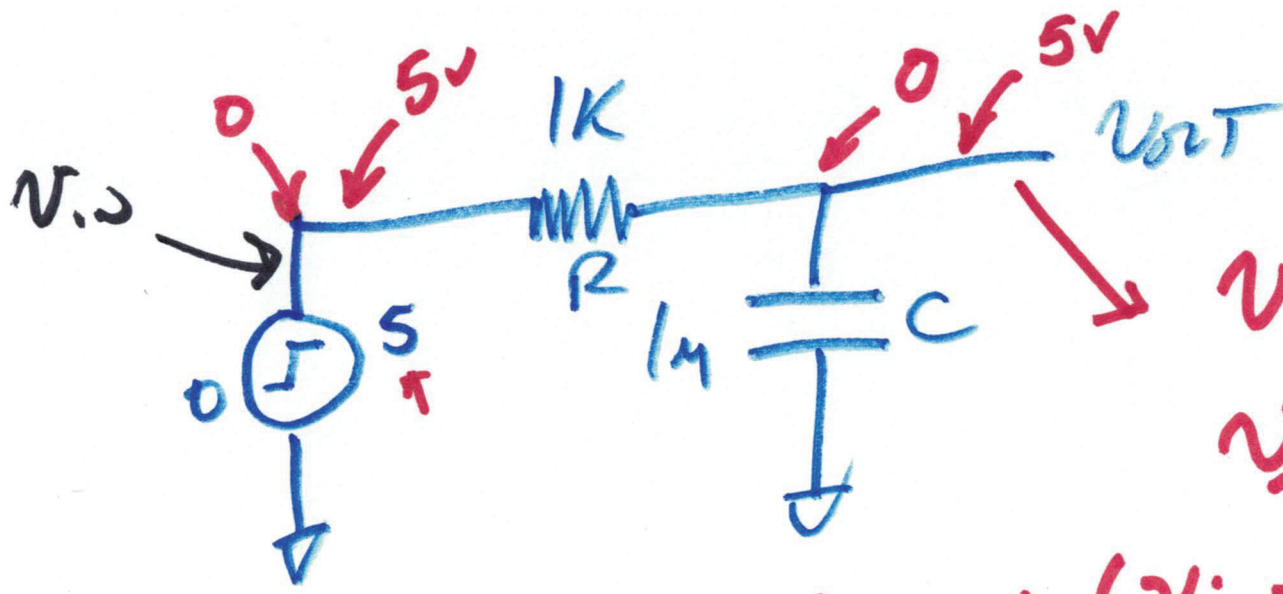


$$v_i = 0$$

$$v_f = 5V$$


$$v_{out}(t) = v_f + (v_i - v_f) e^{-t/\tau}$$

$$= 5 + (0 - 5) e^{-t/1\mu s} \quad t \geq 0$$

$$v_{out}(t) = 5(1 - e^{-t/1\mu s})$$

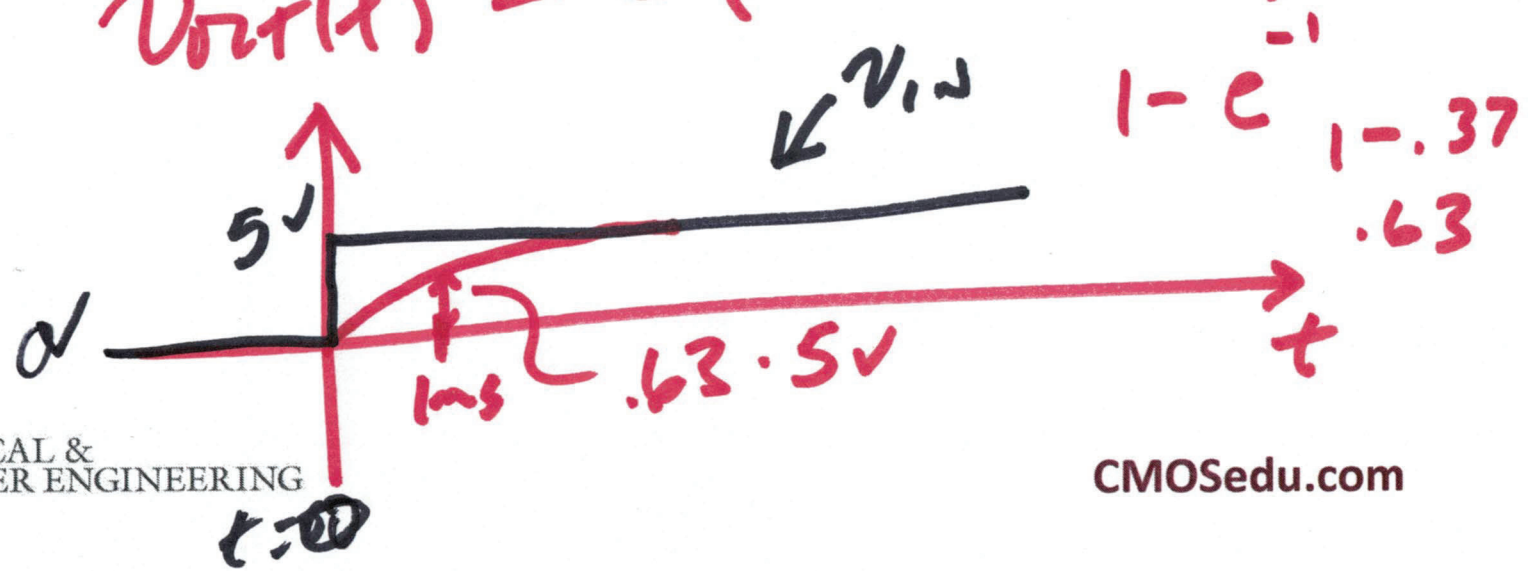

4)

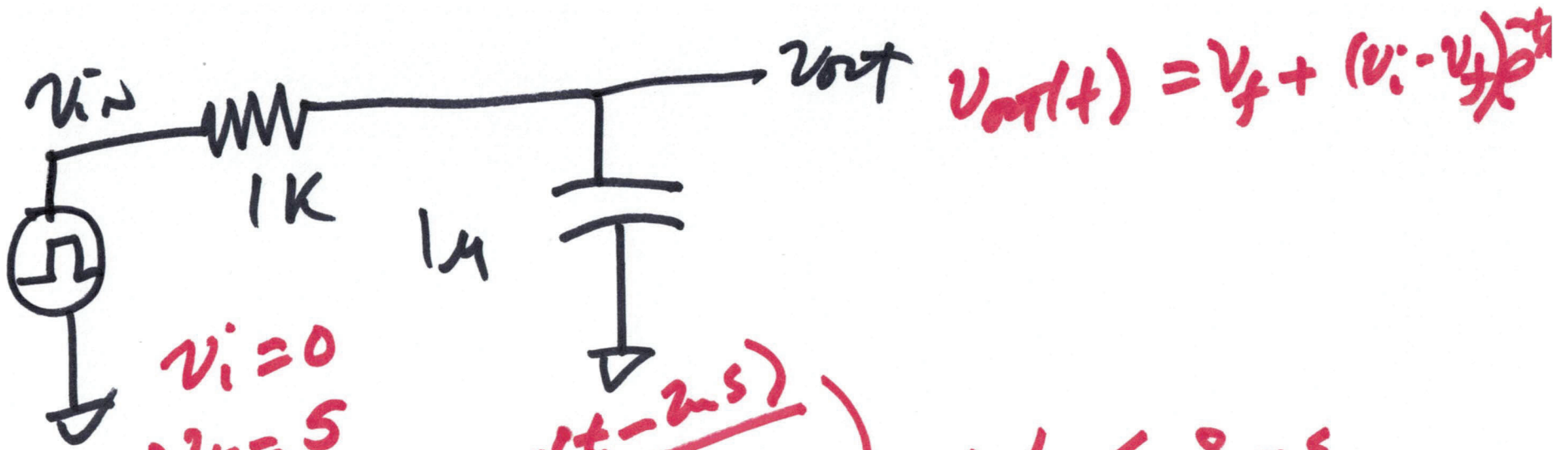


$$v_{out}(t) = v_f + (v_i - v_f)e^{-t/\tau}$$

$$v_i = 0$$

$$v_f = 5$$
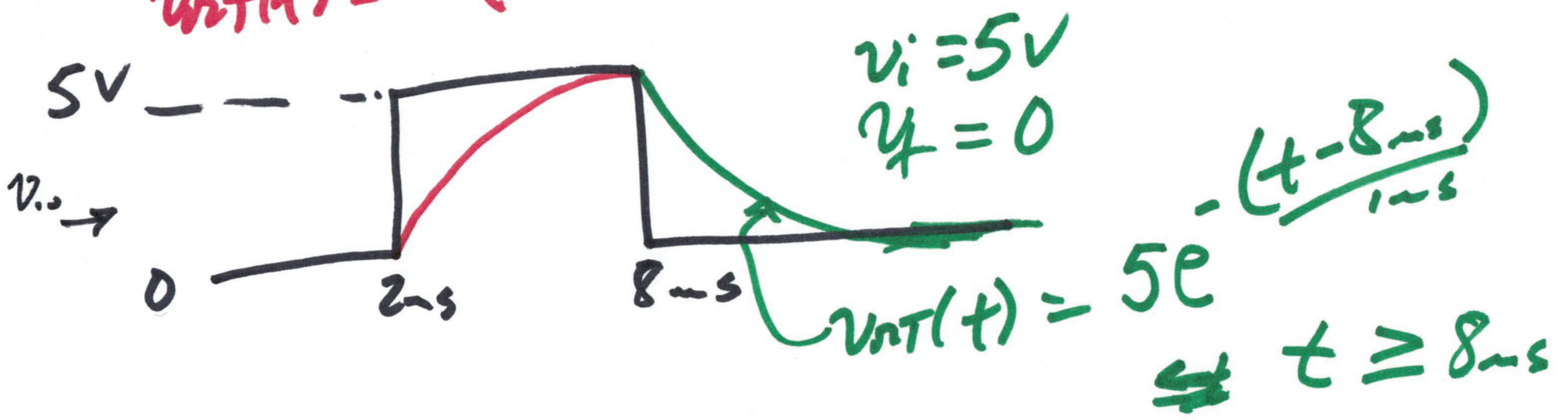
$$v_{out}(t) = 5 \left( 1 - e^{-\frac{(t-2\mu s)}{1\mu s}} \right) \quad 2\mu s \leq t \leq 8\mu s$$



$$CV = Q$$

$$I = C \frac{dV}{dt}$$

$$\text{Amps} = \frac{\text{Coulombs}}{\text{sec}}$$


$$I = 1 \mu\text{A} = 1 \mu\text{F} \cdot \frac{dV}{dt}$$

$$\frac{dV}{dt} = \frac{1 \mu\text{A}}{1 \mu\text{F}} = \frac{10^{-3} \text{A}}{10^{-6} \text{F}}$$


$$\frac{dV}{dt} = \frac{1 \text{V}}{\text{ms}}$$

$$V(t) = \int_0^t dV = \int_0^t \frac{1 \text{V}}{\text{ms}} \cdot dt = \frac{1 \text{V}}{\text{ms}} t \Big|_0^t$$
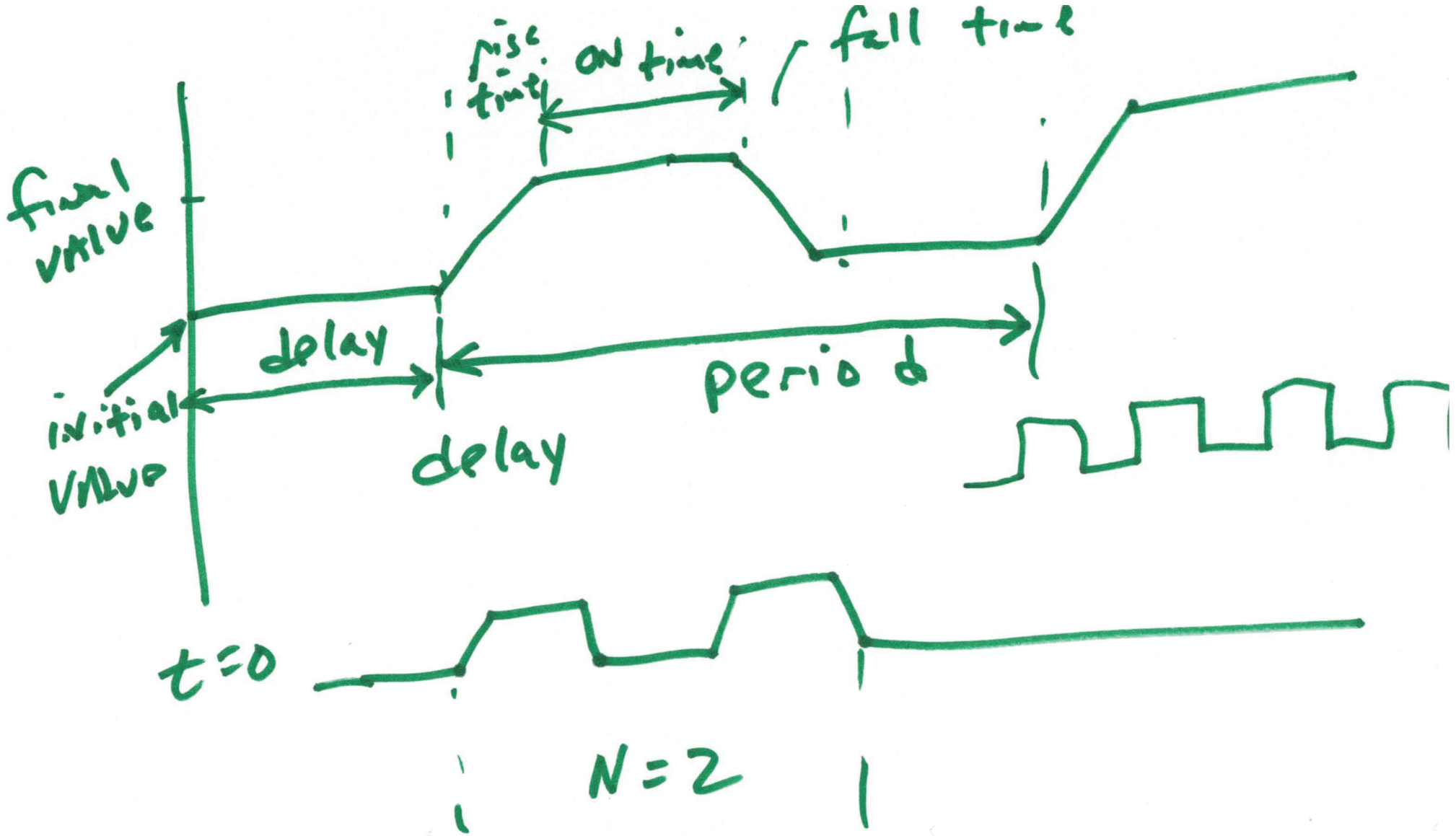
$$V(t) = \frac{1 \text{V}}{\text{ms}} \cdot t$$





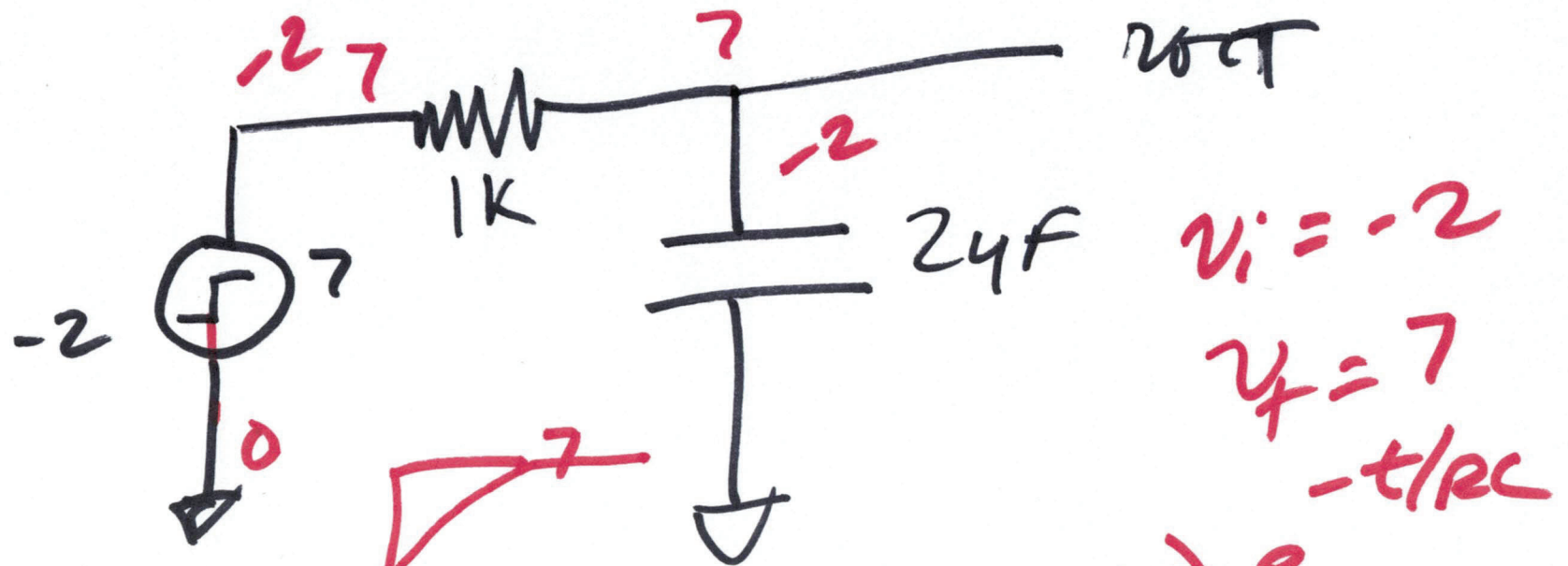

$$\begin{aligned}
 v_{out}(t) &= v_f + (v_i - v_f) e^{-t/RC} \\
 &= 7 + (-2 - 7) e^{-t/RC} \\
 t=0 &\rightarrow v_{out}(0) = -2 \\
 t=\infty &\rightarrow v_{out}(\infty) = 7
 \end{aligned}$$