
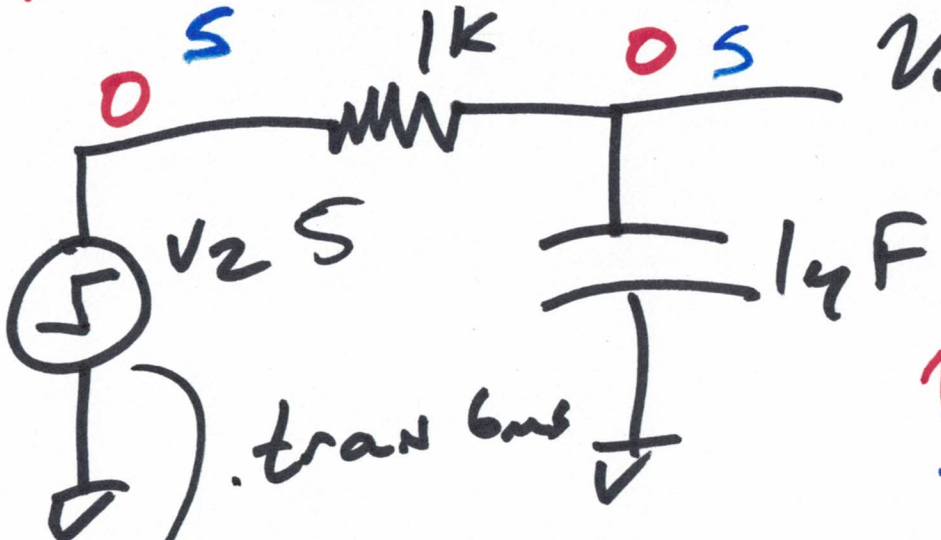



EE 220 Circuits I

Lecture 17

OCTOBER 30, 2023

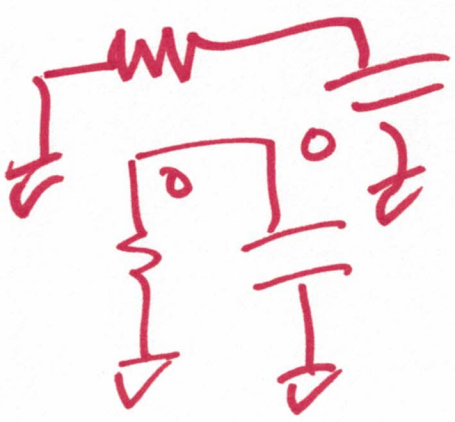
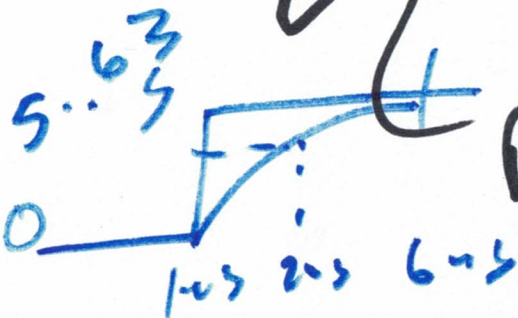
$$\tau = RC = 1\text{ms} = 10^3 \cdot 10^{-6}$$




tran 6ms

pulse (0 5 1ms 1μ 1μ 1 1)

$$v_i = 0$$


$$v_f = 5$$

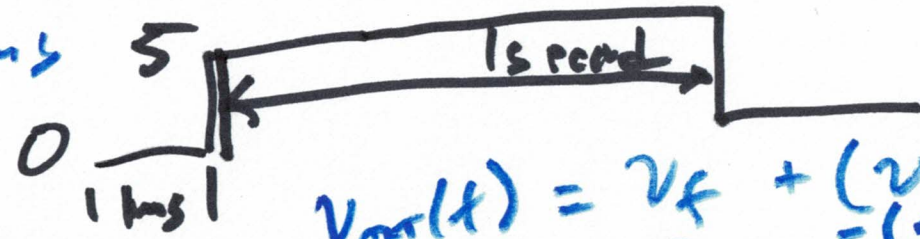

$$V_{out}(t) = V_f + (V_i - V_f)e^{-t/\tau}$$

$$= 5 + 5e^{-(t-1\text{ms})/1\text{ms}} \quad t \geq 1\text{ms}$$
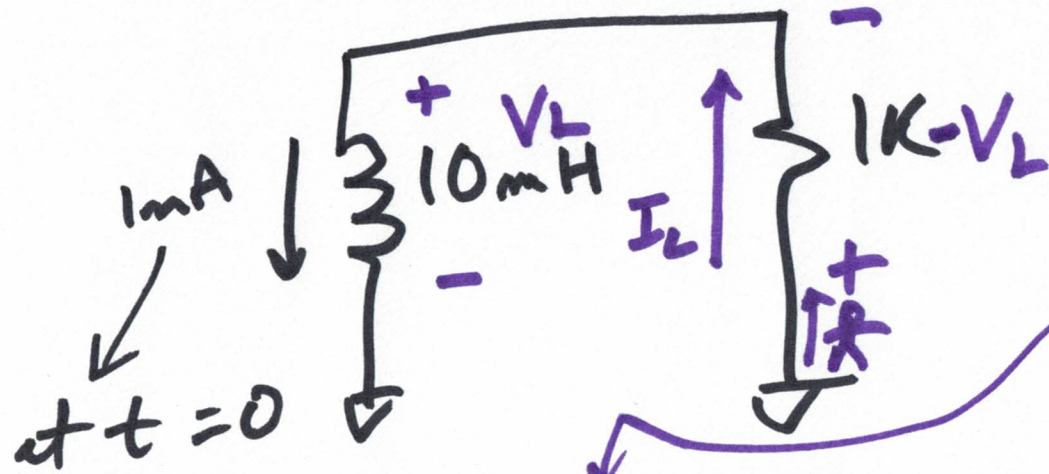
$$= 5(1 - e^{-(t-1\text{ms})/1\text{ms}}) \quad t \geq 1\text{ms}$$



$$-I_L \cdot 1\text{k} - V_L = 0$$

$$I_L \cdot R + L \cdot \frac{dI_L}{dt} = 0$$

$$I_L = -\frac{L}{R} \cdot \frac{dI_L}{dt}$$



$$-\frac{R}{L} \cdot dt = \frac{dI_L}{I_L}$$

$$\begin{aligned} \frac{V_L}{L} &= \frac{1}{1\text{mH}} \\ &= \frac{1\text{A}}{\text{ms}} \\ &= \frac{1\text{mA}}{4\text{s}} \end{aligned}$$

$$+ V_L$$

$$- I_L$$

$$V_L = L \cdot \frac{dI_L}{dt}$$

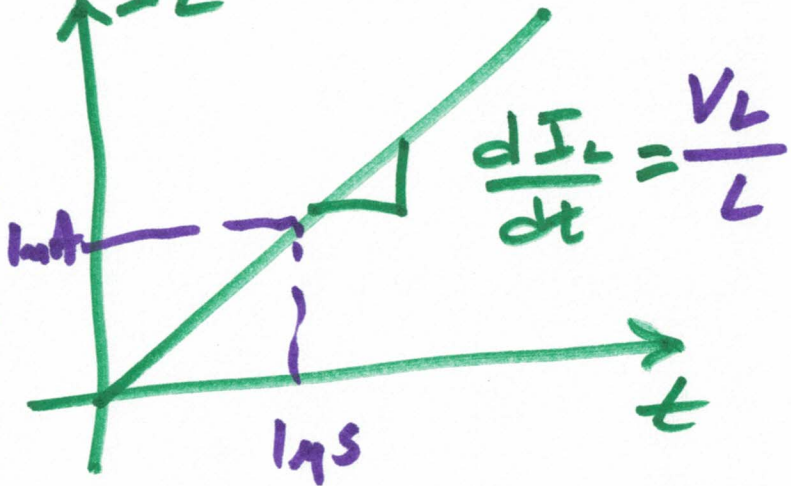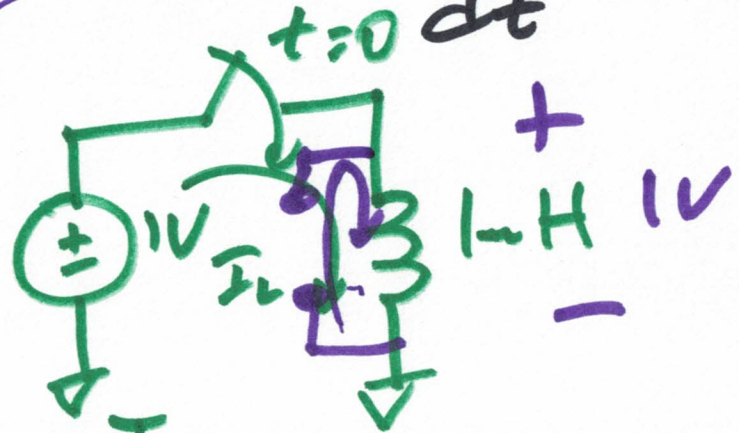

$$\int_{t_{init}}^t \frac{dt}{-\frac{L}{R}} = \int_{I_{init}}^{i(t)} \frac{dI_L}{I_L} = -\frac{R}{L} \cdot dt$$

$$\left. \frac{t}{-\frac{L}{R}} \right|_{t_{init}}^t = \ln I_L \Big|_{I_{init}}^{i(t)} = \frac{R \cdot dt \cdot \frac{1}{I_L}}{-L} = \frac{dt}{-\frac{L}{R}} = -\frac{dt}{L/R}$$

$$-\frac{(t - t_{init})}{\tau} = \ln i(t) - \ln I_{init}$$

$$e^{-\frac{(t - t_{init})}{\tau}} = \frac{i(t)}{I_{init}}$$

$$\tau = \frac{L}{R}$$

$$e^{-\frac{(t - t_{init})}{\tau}} = \frac{i(t)}{I_{init}}$$


$$t \geq t_{init}$$

3)

$$V = I \cdot R$$

$$i(t) = I_{init} e^{-\frac{(t-t_{init})}{L/R}}, t \geq t_{init}$$

$$V = -I \cdot R$$

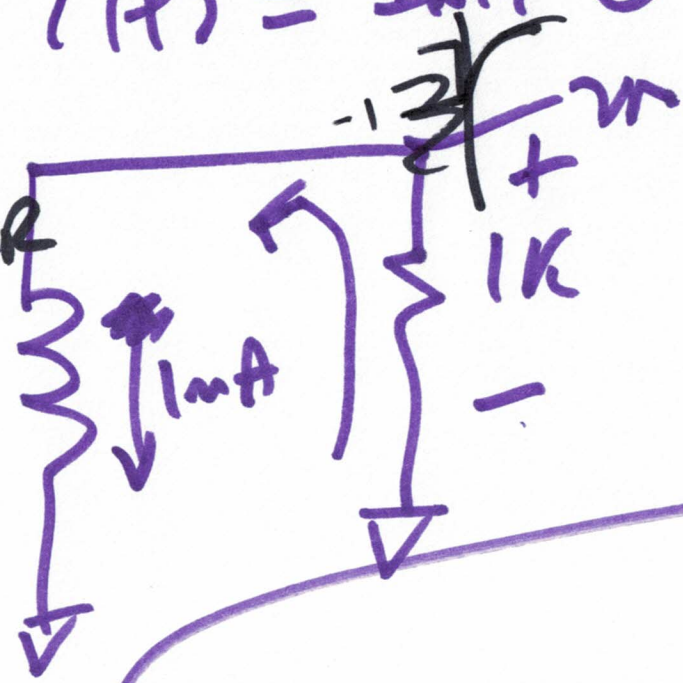

$$I_{init} = 1mA$$

$$\frac{L}{R} = \frac{10mH \cdot 10^{-3}}{1k \cdot 10^{-3}} = 10 \mu s$$

$$10^3 \cdot 10^{-3} = 10^{2-3} = 10^0 = 1$$

$$i(t) = 1mA \cdot e^{-\frac{(t-1ms)}{10\mu s}}, t \geq 1ms$$

$$V_{NT} = -1k \cdot i(t) = -1V e^{-\frac{(t-1ms)}{10\mu s}}$$

$$i(t) = i_f + (i_i - i_f) e^{-t/\tau}$$

4)

Quiz #13 EE 220 Fall 2022

Name: _____


Closed book and notes.

Show your work for credit!


$$= v_f + (v_i - v_f) e^{-t/\tau}$$

$$\tau/R = \frac{1\mu}{1k} = 1\mu s$$

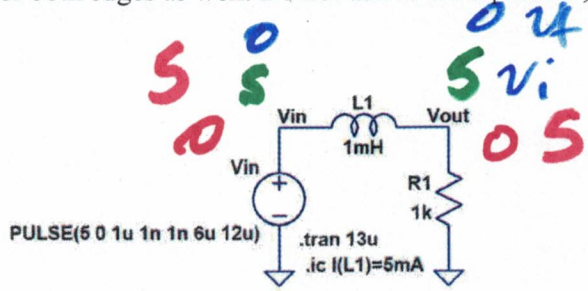1. Plot V_{out} for the following circuit on the plot seen below for both transitions of the input pulse. Write equations for both edges as well. Do not derive the equations, simply write them. (5 points)


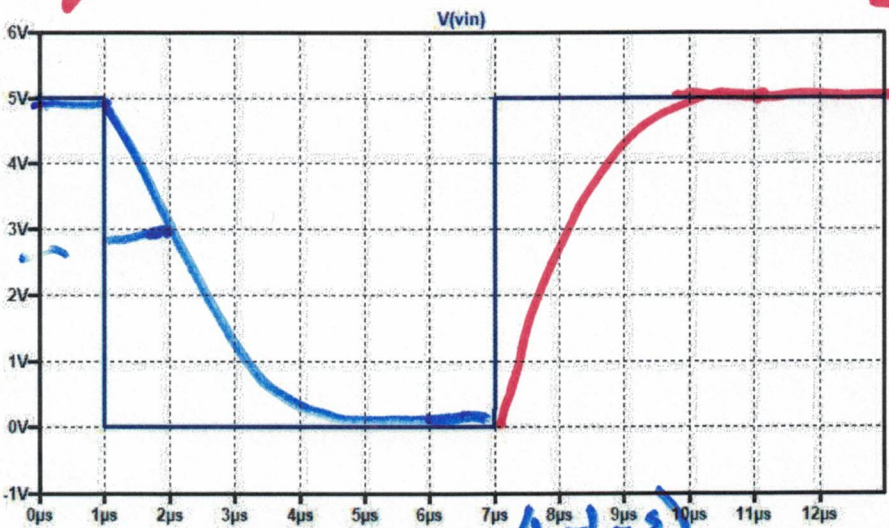
```
PULSE(6 0 1u 1n 1n 6u 12u)
.tran 13u
.ic (L1)=5mA
```





5.37

BGA
Arr
Lir
cday

$$v_{out}|_{falling} = 5e^{-\frac{t-1\mu s}{1\mu s}}, t \geq 1\mu s$$

$$v_{out}|_{rising} = 5 + (0 - 5)e^{-\frac{t-7\mu s}{1\mu s}}, t \geq 7\mu s$$

5)

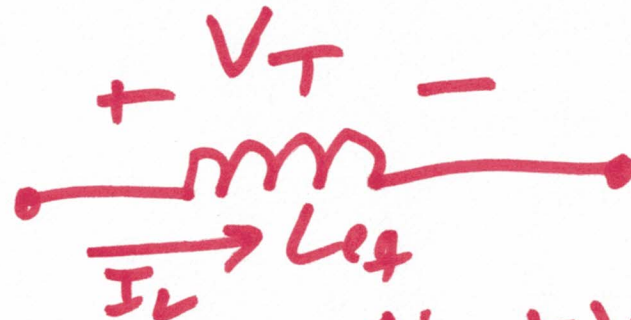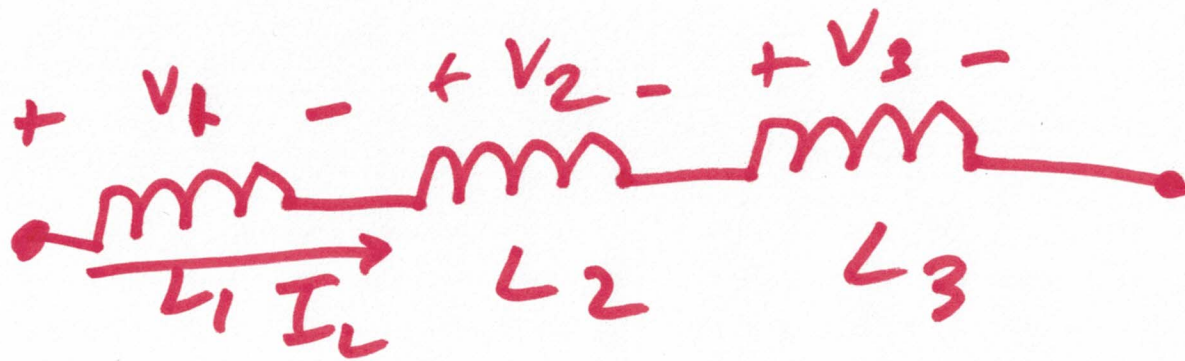

$$V_T = V_1 + V_2 + V_3$$


$$V_1 = L_1 \frac{dI_L}{dt}, \quad V_2 = L_2 \frac{dI_L}{dt}$$

$$V_3 = L_3 \frac{dI_L}{dt}$$

$$V_T = V_1 + V_2 + V_3 = \underbrace{(L_1 + L_2 + L_3)}_{L_{eq}} \frac{dI_L}{dt}$$

$$V_L = L \cdot \frac{dI_L}{dt}$$

$$I_L = \frac{1}{L} \int V_L \cdot dt$$

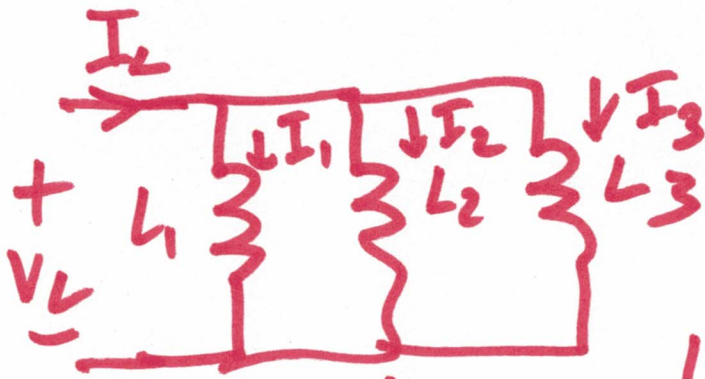

$$I_L = I_1 + I_2 + I_3$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} = \frac{1}{L_1} \int V_L \cdot dt + \frac{1}{L_2} \int V_L \cdot dt + \frac{1}{L_3} \int V_L \cdot dt$$

$$\frac{1}{L_{eq}} \int V_L \cdot dt = \left(\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right) \int V_L \cdot dt$$

7)