
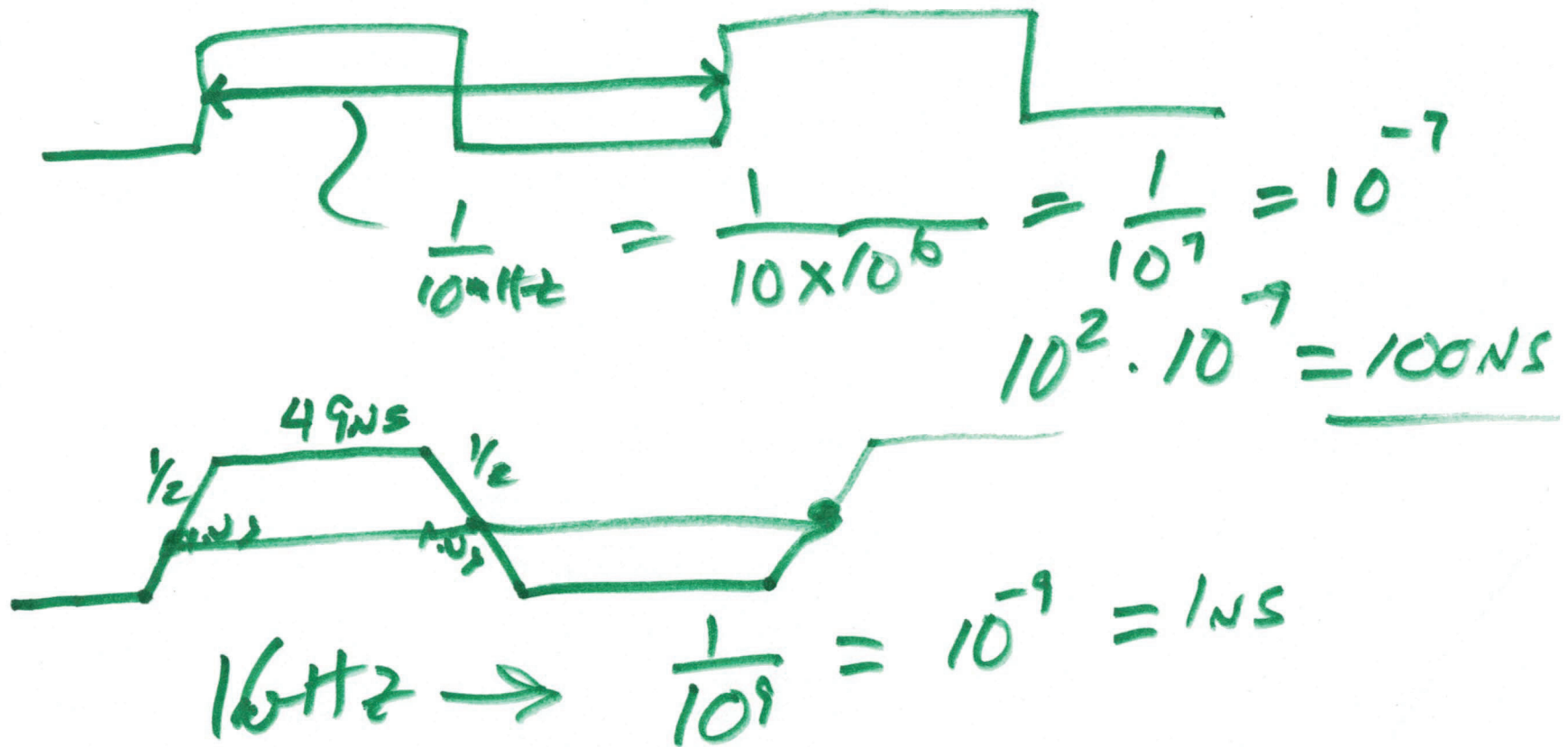


EE 220 circuits I

November 6, 2023

Lecture 19

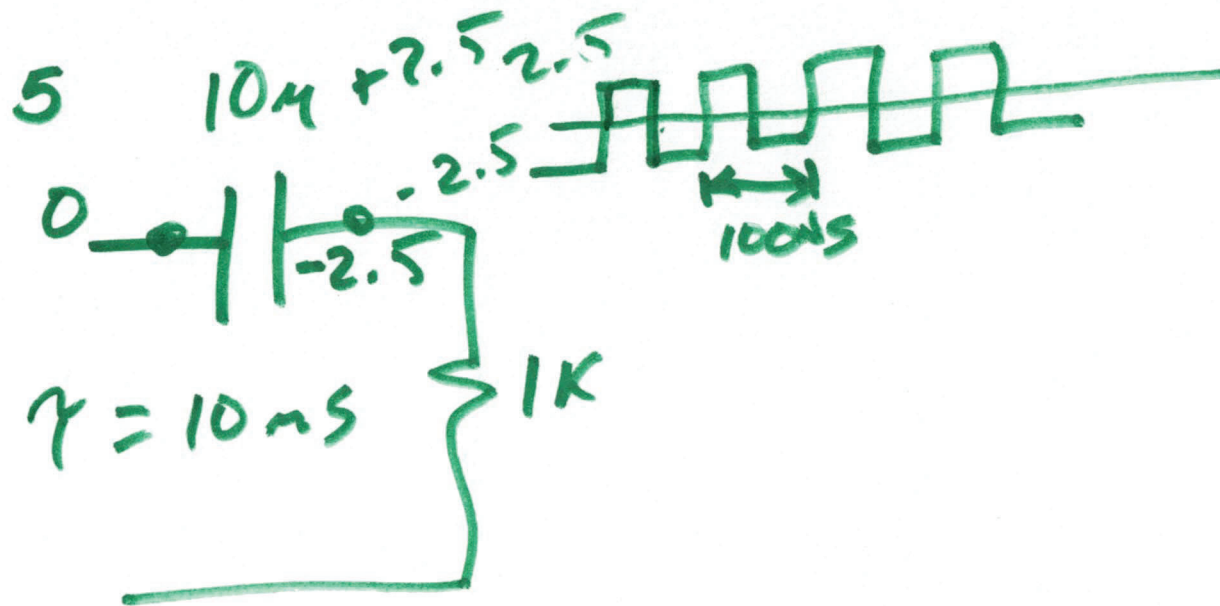




$$0 - (-2.5) = 2.5$$

$$5 - (2.5) = 2.5$$

2)

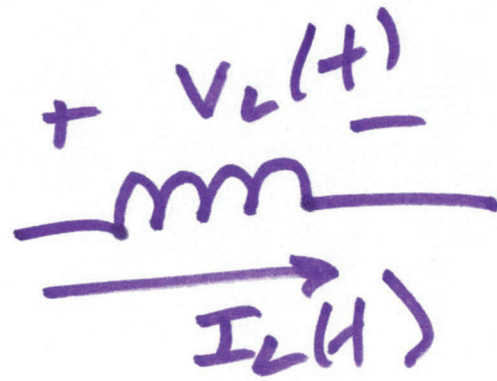

$$P = VI$$

↑
P_{DC}

$$v_L = L \cdot \frac{di_L(t)}{dt} \rightarrow dt = \frac{L}{v_L(t)} di_L(t)$$

Apparent power

$$P(t) = v_L(t) \cdot i_L(t)$$


$$E = \int_{t_1}^{t_2} v_L(t) \cdot i_L(t) \cdot dt$$

$$\int_{t_1}^{t_2} L \cdot \frac{di_L(t)}{dt} \cdot i_L(t) \cdot dt$$

$$\int_{i_0}^{I_0} L \cdot i_2(t) \cdot di_2(t)$$

$$\mathcal{E} = L \frac{x^2}{2} = \frac{1}{2} L I_{DC}^2$$

$$\mathcal{E} = \frac{1}{2} L I_{DC}^2$$

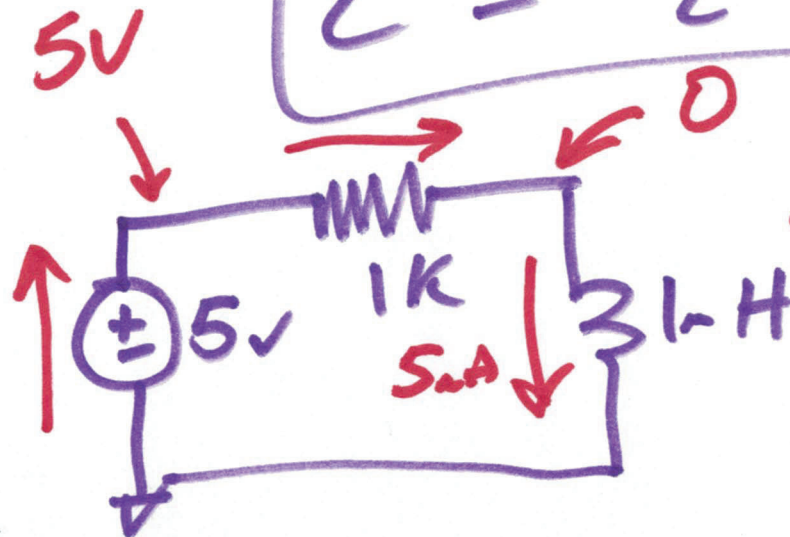

$$\mathcal{E} = \frac{1}{2} \cdot 10^{-3} \cdot (5 \text{mA})^2$$

$$= \frac{1}{2} \cdot 10^{-3} \cdot 25 \cdot 10^{-6}$$

$$= 12.5 \text{ nJ}$$

$$\frac{1}{T} v_c(t) \quad \mathcal{E} = \int_0^Q v_c(t) \cdot dt$$

$$= \frac{1}{2} v_c(t) \Big|_0^Q$$

$$\mathcal{E} = \int_{t_1}^{t_2} v_c(t) \cdot i_c(t) \cdot dt$$

$i = C \frac{dv}{dt} \quad dt = C \frac{dv}{i}$


$$= \int_{v_1}^{v_2} v_c(t) \cdot i_c(t) \cdot C \cdot \frac{dv_c(t)}{i_c(t)}$$

$$\mathcal{E} = C \int_{v_1}^{v_2} v_c(t) \cdot d v_c(t)$$

$$\Sigma = C \int_{V_1}^{V_2} \frac{1}{2} X^2$$

$$\Sigma = \frac{1}{2} C (V_2 - V_1)^2$$

$$\Sigma = \frac{1}{2} C V^2$$

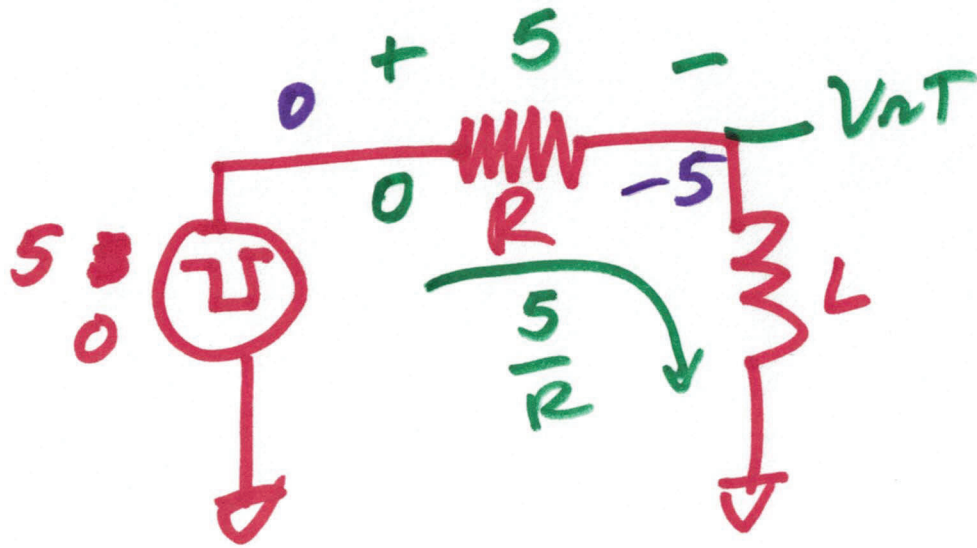

$P_w \gg \frac{L}{R}$
 $V_i = -5$
 $V_f = 0$

$V_i = 5$
 $V_f = 0$

