

EE 220 circuits I


NOVEMBER 8, 2023

$$v_i = 2.5$$

$$v_f = 5$$



Lecture 20

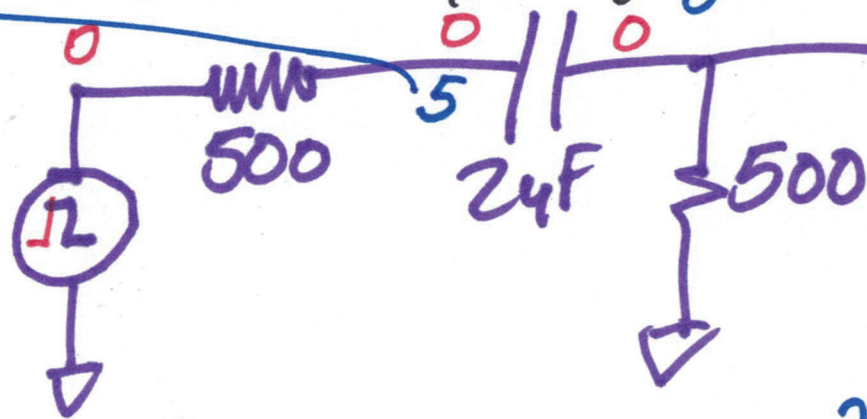


$$v_r = 2.5e^{-\frac{(t-1\mu s)}{2\mu s}} \quad t \geq 1\mu s$$

$$\tau = 2\mu(500 + 500)$$

$$v_i = 2.5$$


$$v_f = 0$$

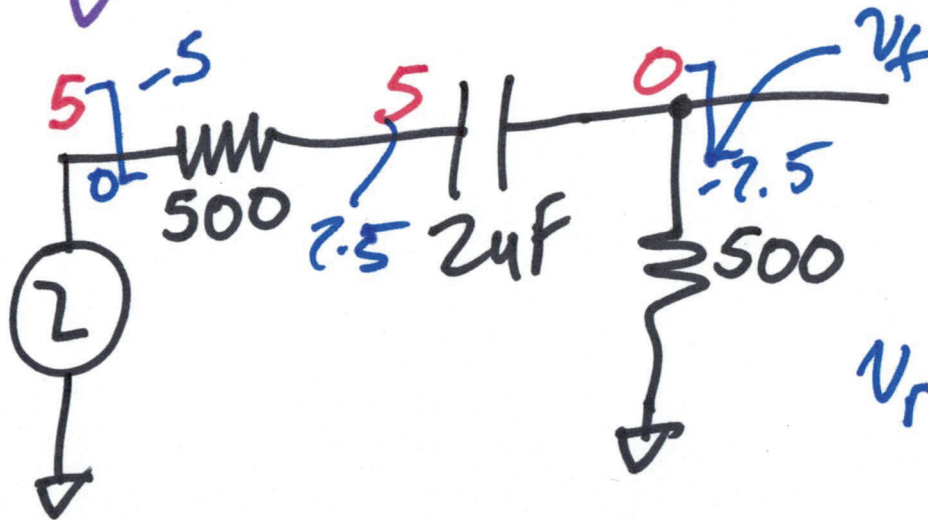

$$v_i = -2.5$$

$$v_f = 0$$

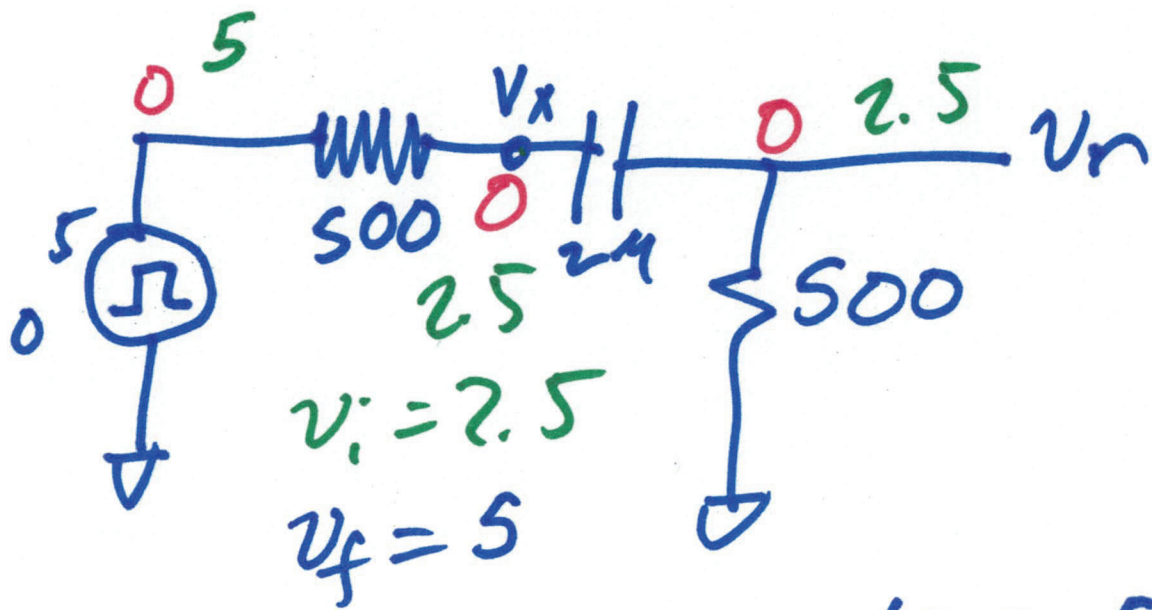
$$v_r = -2.5e^{-\frac{(t-11\mu s)}{2\mu s}} \quad t \geq 11\mu s$$




$$V_x(t) = 5 + (2.5 - 5)e^{-\frac{(t - 1\text{ms})}{2\mu\text{s}}}$$

$$V_x(1\text{ms}) = 2.5$$

$$V_n(16\mu\text{s}) = 5\checkmark$$

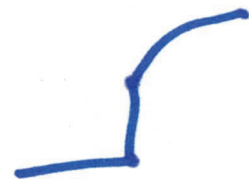

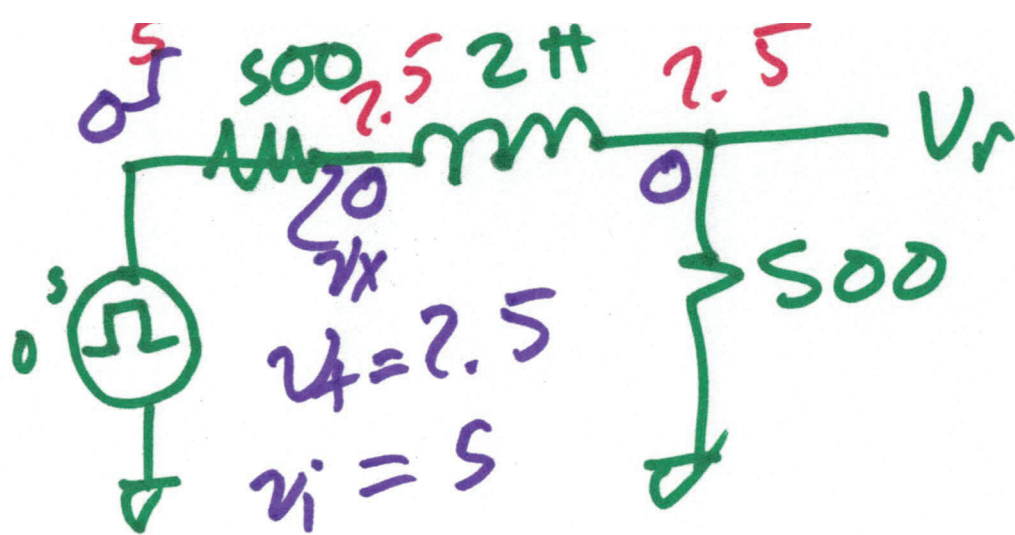

$V_i = 0$
 $V_x = 2.5$
 $V_i = 5$



$V_i = 0$
 $V_x = 2.5 \leftarrow$

$$V_x(t) = 2.5 + (5 \cdot 2.5) e^{-\frac{t-1ms}{2ms}}$$

$$2.5 + (2.5) e^{-\frac{t-1ms}{2ms}}$$

$$2.5(1 - e^{-\frac{t-1ms}{2ms}})$$

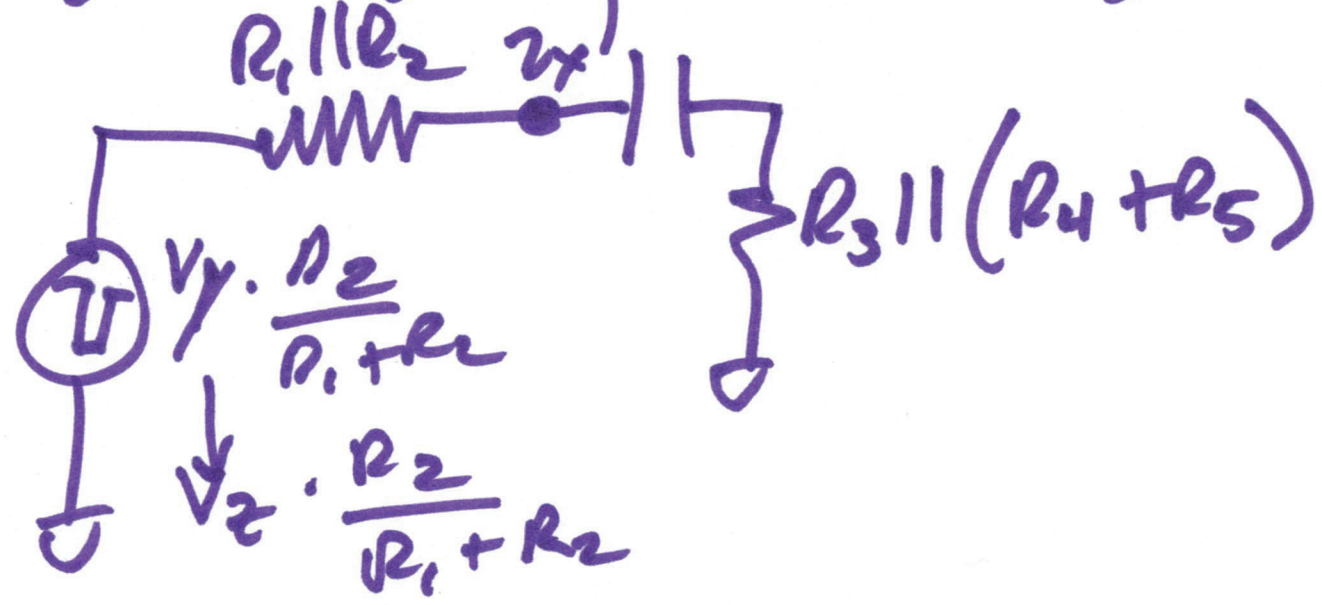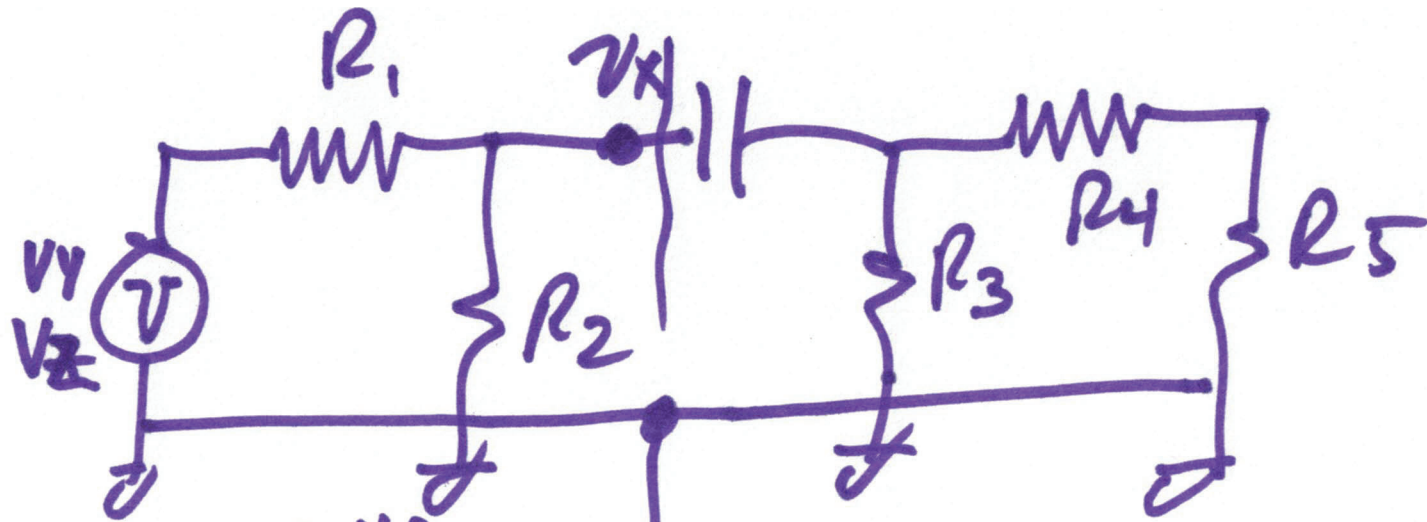
$V_x(t) = 2.5 + (0 - 2.5) e^{-\frac{t-1ms}{2ms}}$




Integrators

Switch closed
 $t < 0$


Switch open
 $t > 0$

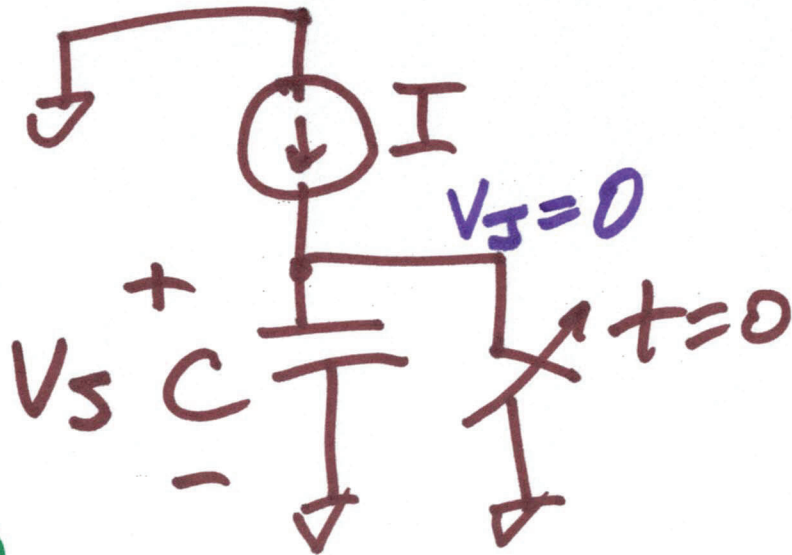

$$I = C \frac{dV}{dt}$$

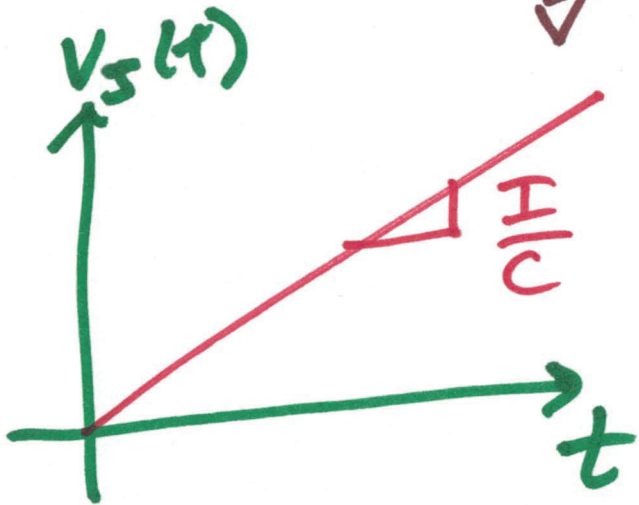
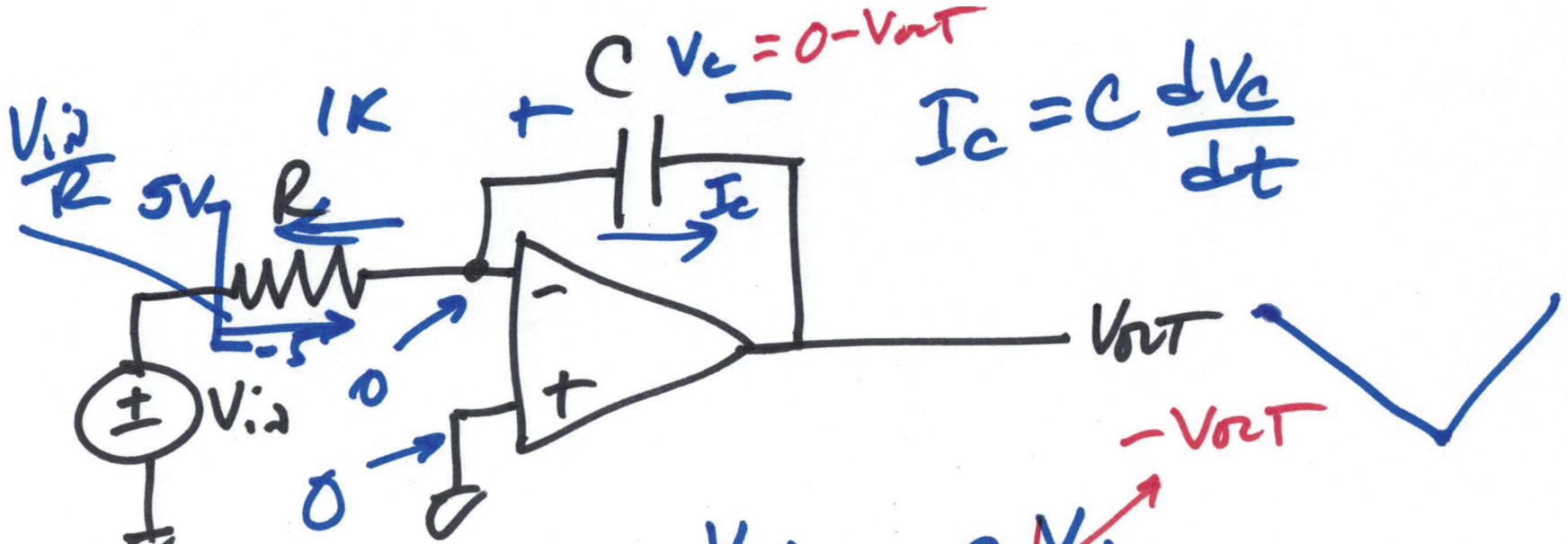
$$\int_0^t dV_S = \int_0^t \frac{I}{C} dt$$
$$V_S(t) = \frac{I}{C} \cdot t$$



5V
 $\tau = RC = 1K \cdot 14F = 14ms$

$$V_{out}(t) = -\frac{1}{RC} \int_0^t V_{in} dt$$

$$V_{out}(t) = -\frac{1}{RC} \cdot V_{in} \cdot t$$

$$\begin{aligned}
 V_{out} &= -\frac{5}{1K \cdot 14} \cdot t \\
 &= -\frac{5V}{14ms} \cdot t
 \end{aligned}$$