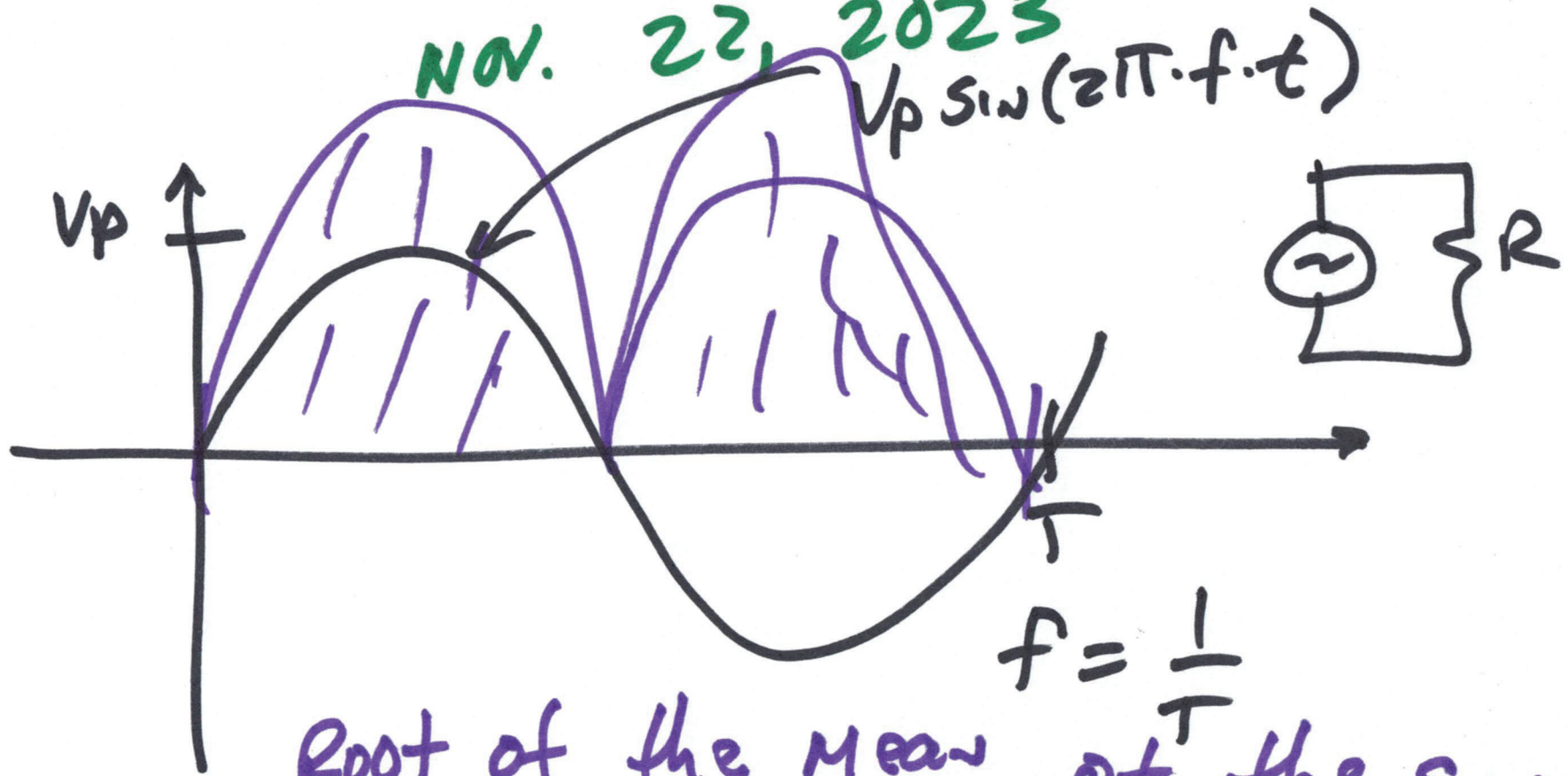


EE 221 Circuits I

Lecture 23

NOV. 22, 2023



$$f = \frac{1}{T}$$

Root of the Mean of the Square

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T V_p^2 \sin^2(2\pi f t) \cdot dt}$$

$$V_{Rms} = \sqrt{\frac{1}{T} \int_0^T V_p^2 \cdot \sin^2(2\pi ft) \cdot dt}$$

$$\sin^2 x = \frac{1 - \cos 2x}{2}$$


$$= \sqrt{\frac{V_p^2}{2T} \int_0^T (1 - \cos 4\pi ft) \cdot dt}$$

$$= \sqrt{\frac{V_p^2}{2T} \left(t - \frac{1}{4\pi f} \sin(4\pi ft) \right)_0^T}$$


$f = \frac{1}{T}$

$$V_{Rms} = \frac{V_p}{\sqrt{2}} = \sqrt{\frac{V_p^2}{2T} (T - 0) - \frac{1}{4\pi f} (\sin(4\pi \cdot \frac{1}{T} \cdot T) - \sin 0)}$$

$$V_{rms} = \frac{V_p}{\sqrt{2}}$$

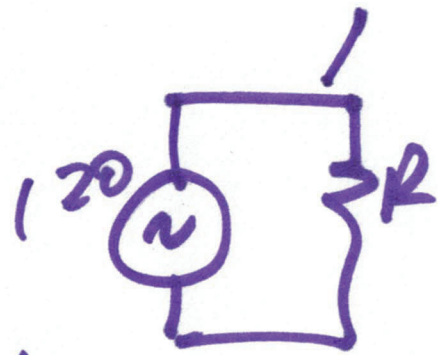


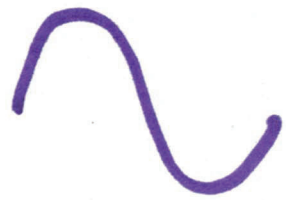
$$120 = V_{rms} = \frac{V_p}{\sqrt{2}} \quad 120V_{DC}$$



$$V_p = \sqrt{2} \cdot 120 = 169.7$$
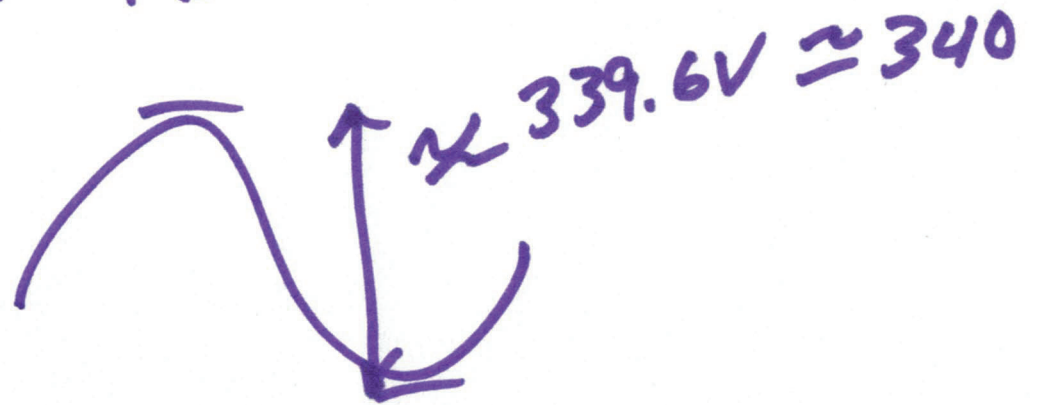
$$120V_{rms} \rightarrow 169.7 \text{ Sine } (2\pi \cdot 60 \cdot t)$$



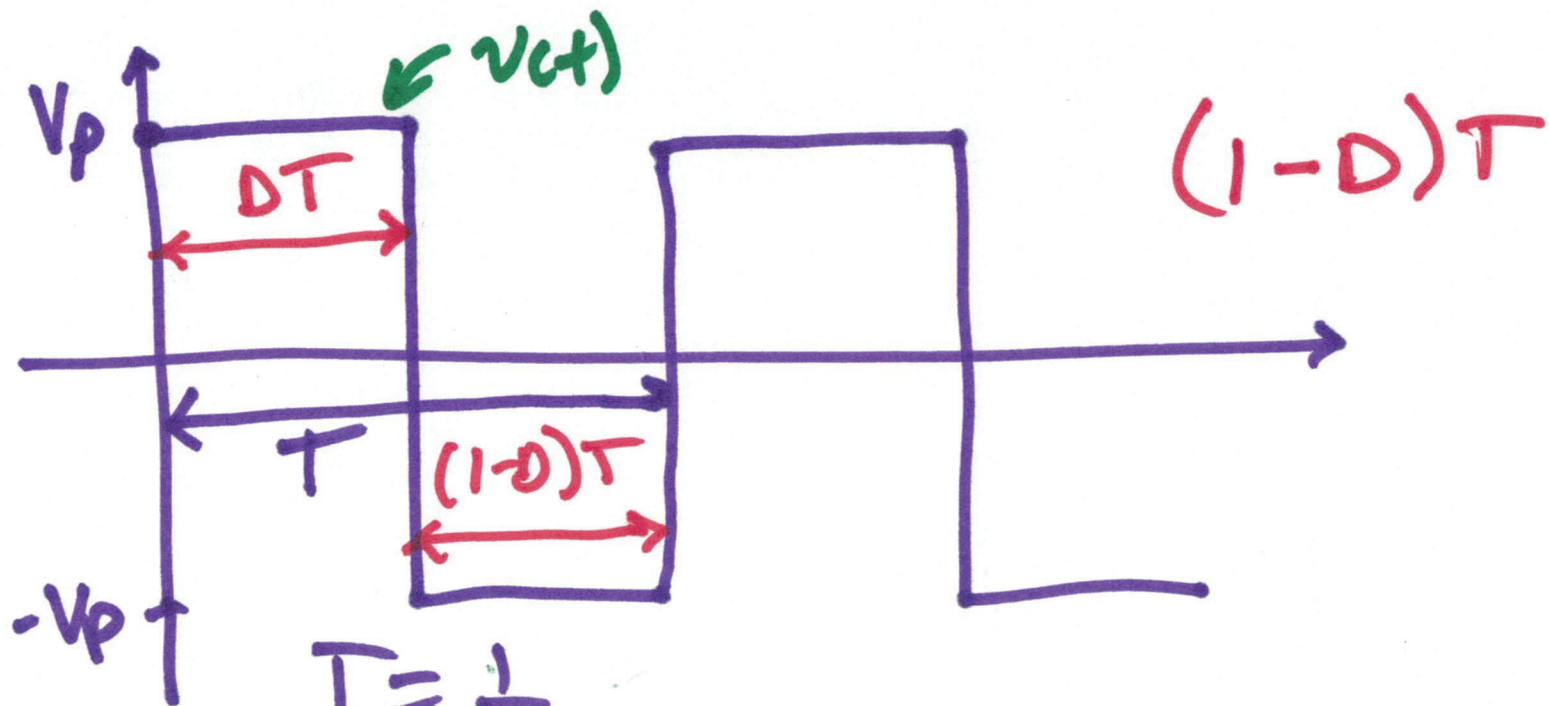


$$T = \frac{1}{f}$$

$$\frac{1}{T} \int_0^T V_p^2 \cdot dt$$

$$= \frac{1}{T} (V_p^2 t) \Big|_0^T$$



$$V_{Rms} = V_p$$
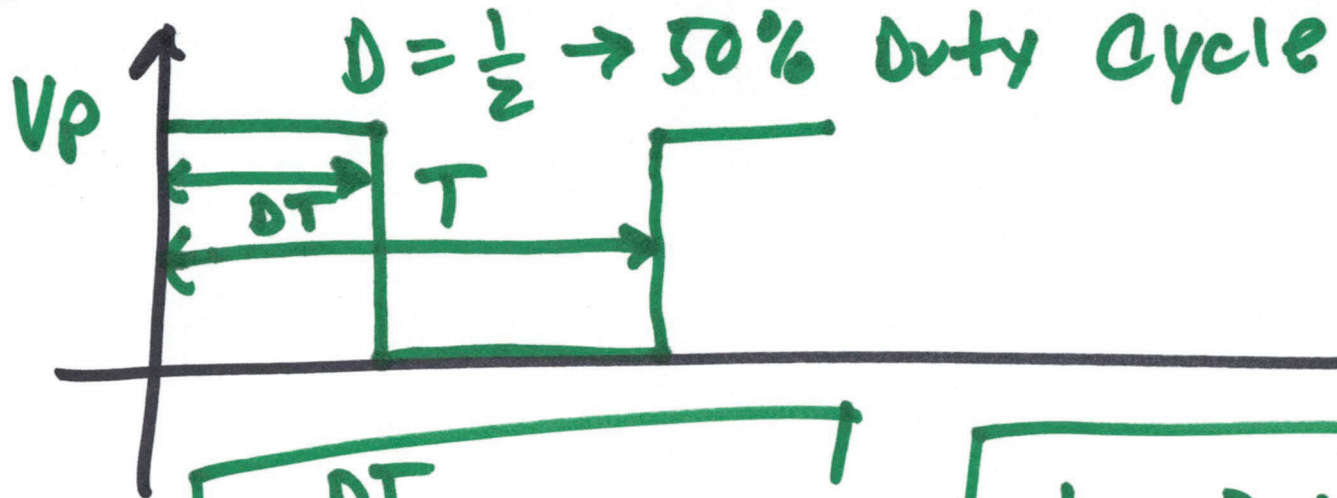
$$V_{RMS} = \sqrt{\int_0^T v^2(t) \cdot dt}$$




$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^{DT} V_p^2 \cdot dt} = \sqrt{\frac{1}{T} V_p^2 \cdot t \Big|_0^{DT}}$$

$$V_{RMS} = \sqrt{D} \cdot V_p$$

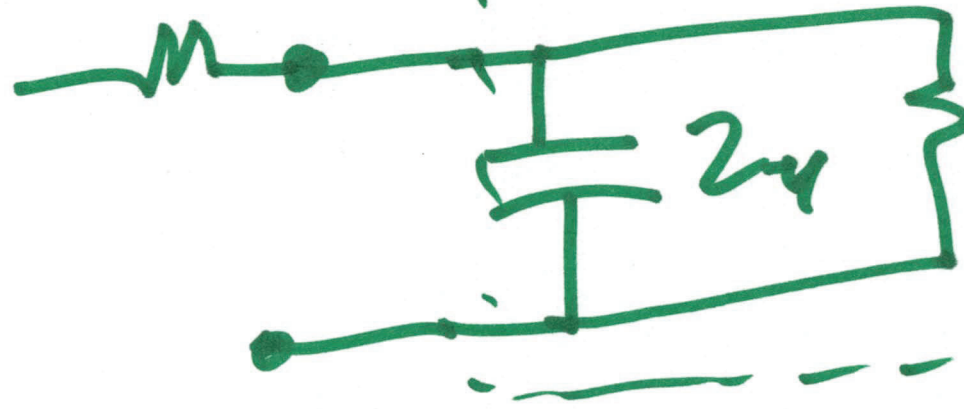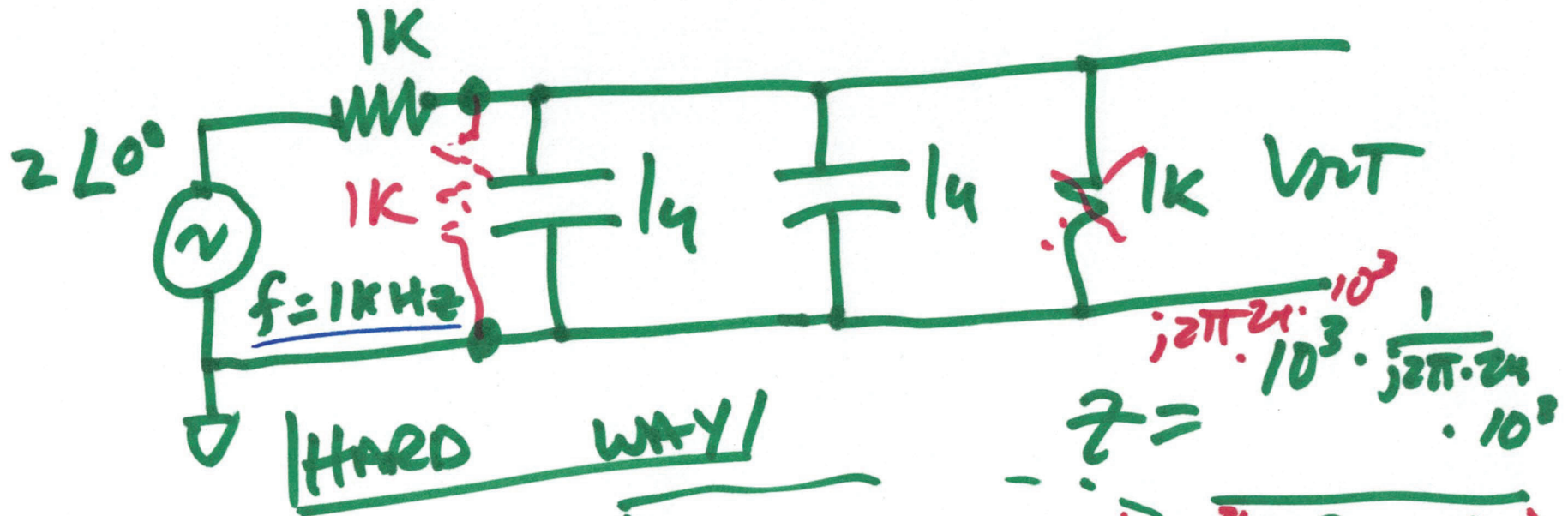


$$Z = \frac{1}{j2\pi \cdot 24 \cdot 10^3 \cdot \frac{1}{j2\pi \cdot 24 \cdot 10^3} + \frac{1}{j2\pi \cdot 24 \cdot 10^3}}$$
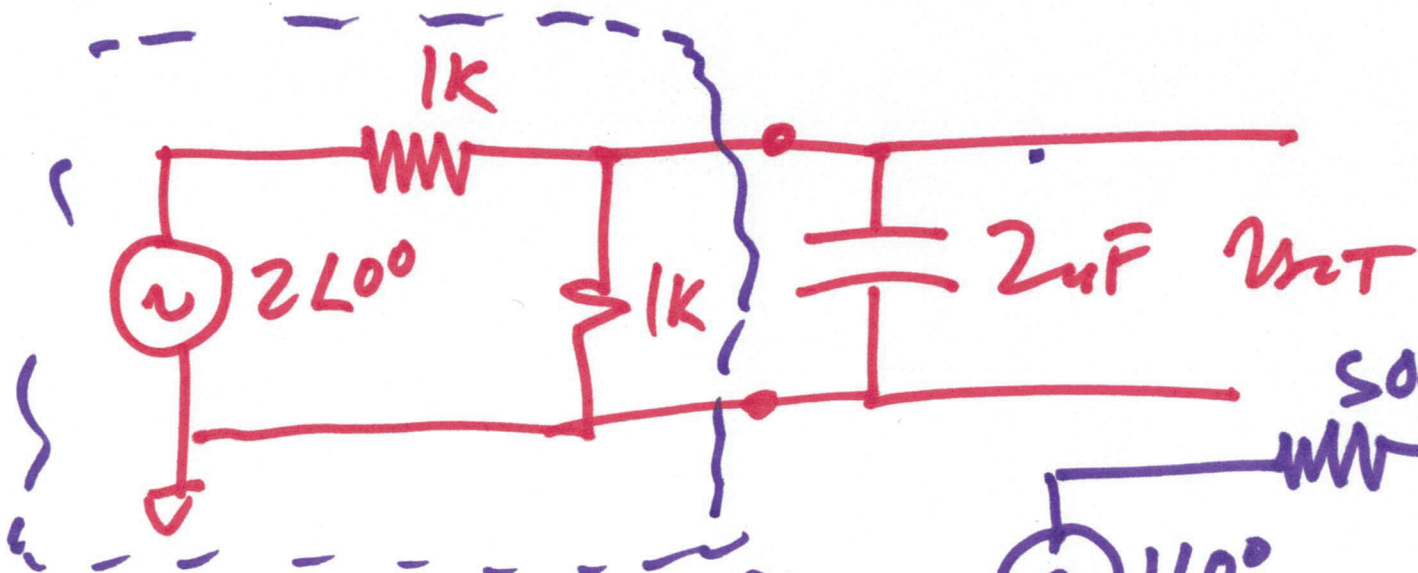
$$V_{out} = 2\angle 0^\circ \cdot \frac{Z}{Z + 10^3} \quad Z = \frac{10^3}{1 + j2\pi \cdot 24 \cdot 10^6}$$




Theremin R

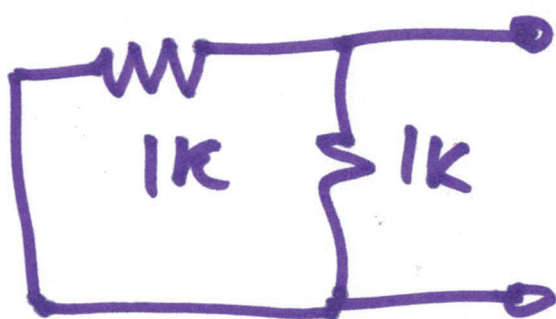

Open ckt



$R_{TH} = 500$

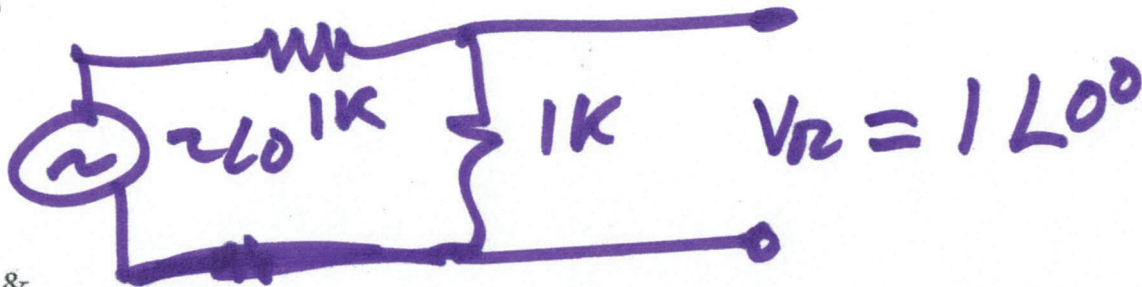


$$Z_c = \frac{1}{j \cdot 2\pi \cdot 10^3 \cdot 24} = -j79.6$$

$$\frac{1}{j} = \frac{1}{\sqrt{-1}}$$

$$\frac{j}{j} \frac{1}{j} = \frac{j}{j^2}$$

$$-j = \frac{j}{(\sqrt{-1})^2}$$

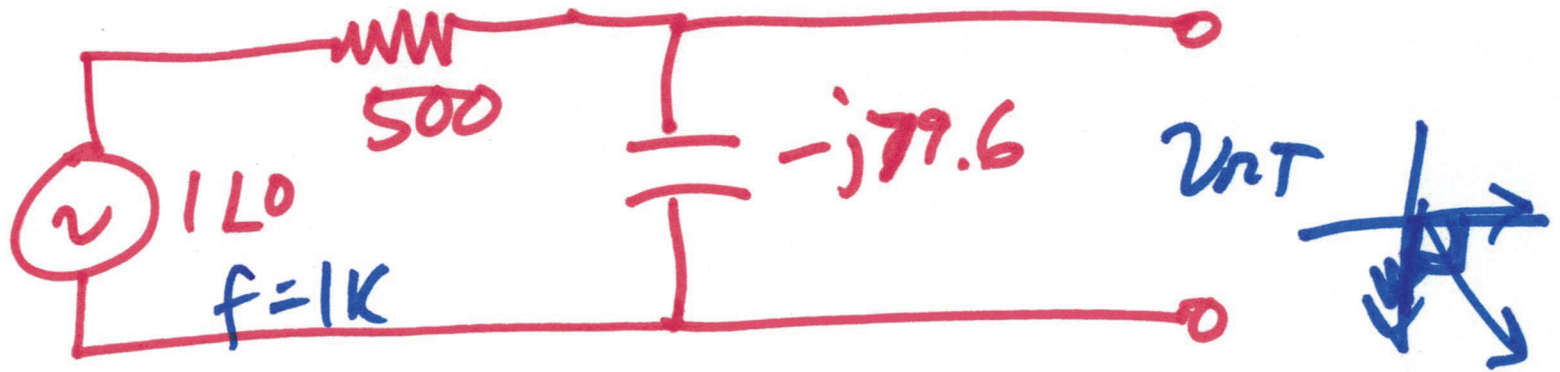

$$V_{out} = 110 \cdot \frac{0 - j79.6}{500 + (-j79.6)}$$

$$= \frac{1100 \cdot 79.6 \angle -90^\circ}{506.3 \angle -9^\circ}$$

$$|1| = \sqrt{(500)^2 + (-79.6)^2}$$

$$\angle \tan^{-1}\left(\frac{-79.6}{500}\right)$$

$$V_{nT} = \frac{1200 \cdot 79.6 \angle -90^\circ}{506.3 \angle -90^\circ} \quad -90 - (-90)$$

$$V_{nT} = 157 \mu\text{V} \angle -81^\circ$$

$$360 \cdot \frac{t_d}{T} = \frac{t_d}{10^{-3}} \cdot 360 = -81^\circ$$

$$t_d = 225 \mu\text{s}$$

period = $\frac{1}{f} = \frac{1}{10^3} = \frac{1}{1\text{kHz}}$

$$V_{nT} = 157 \mu\text{V} \sin(2\pi \cdot 10^3 \cdot t - 81^\circ)$$

$$z_c = \frac{1}{j \cdot 2\pi \cdot 4 \cdot 10^4 \cdot 250 \text{ nF}}$$

$$f = 0$$

$$z_c = \text{open} = \infty$$

$$f = 10^6$$

$$z_c = \frac{1}{j \cdot 2\pi \cdot 10^6 \cdot 250 \cdot 10^{-9}}$$
$$= \frac{1}{j \cdot 2\pi \cdot (0.25)} = -j0.64$$