

EE 220 CIRCUITS I

Lecture 24

NOVEMBER 27, 2023

$$\frac{1}{j \cdot 2\pi \cdot 500 \cdot 1\mu\text{F}} = -j318.5 \Omega$$




2.5V

$2.5 + j0$

$2.5 \sin(2\pi \cdot 500t)$


$12.5 + j0$
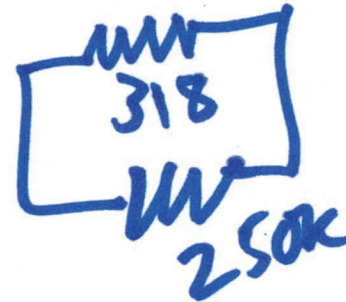
$$\sqrt{2.5^2 + 0^2} = 2.5$$
$$\angle 2.5 + j0 \rightarrow \tan^{-1} \frac{0}{2.5} = 0$$



$$\frac{250k \cdot 318}{250k + 318}$$
$$\frac{318}{1 + \frac{318}{250k}}$$

1.0017 2.5V

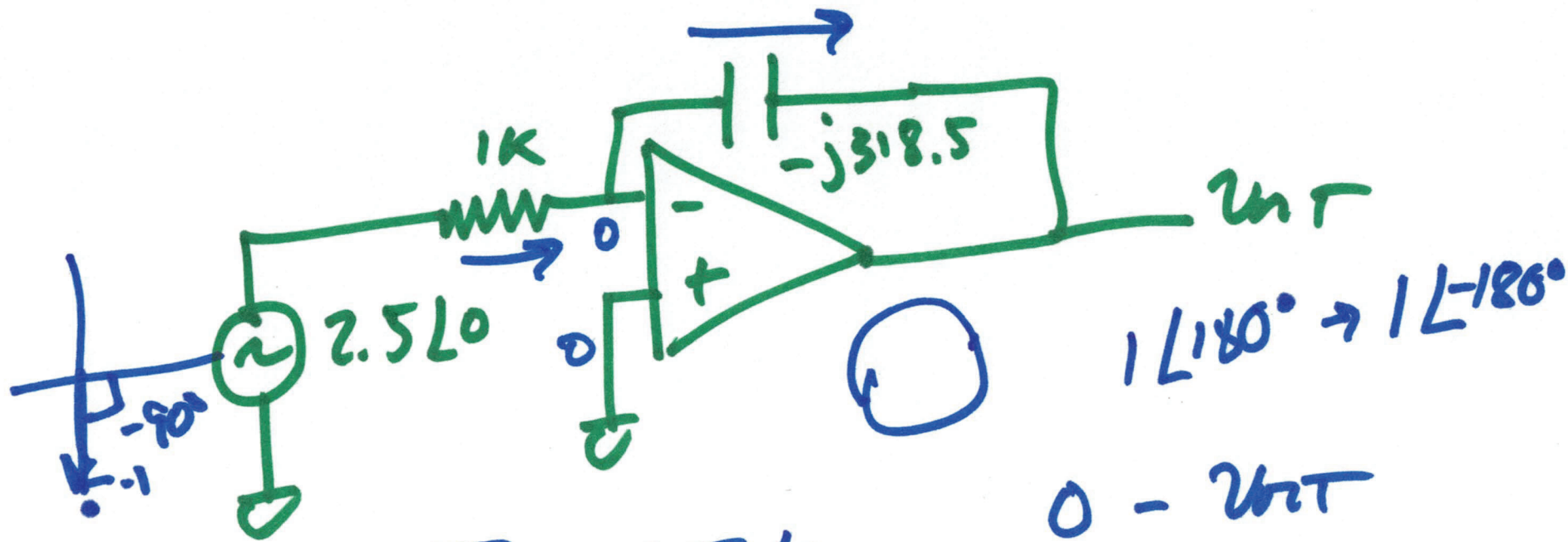

$$|-j318.5| = \sqrt{318.5^2} \times 10^2$$

$$\frac{2.5\angle 0}{1k} = \frac{0 - v_{out}}{-j318.5}$$

$$f_{av}^{-1} = \frac{-j}{0}$$

$$f_{av}^{-1} = \infty$$

$$-f_{av}^{-1} = \infty$$

$$-90 - (-180) = 90$$


$$-90 - 180 = -270$$

$$-v_{out} = v_{out} \angle 180^\circ = (2.5 \angle 0^\circ) \cdot (318 \angle -90^\circ)$$

$$v_{out} \angle 180^\circ = .795 \angle -90^\circ$$

$$v_{out} \angle 0^\circ \cdot 1 \angle 180^\circ$$
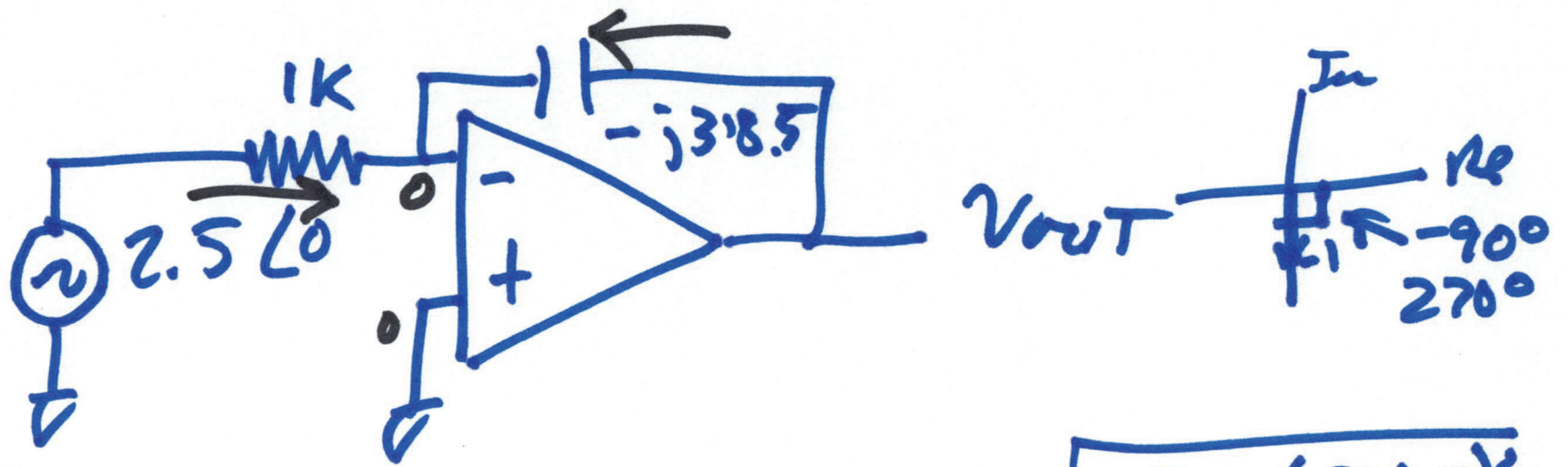
$$v_{out} = \frac{.795 \angle -90}{1 \angle 180} = \underline{\underline{.795 \angle 90}}$$



$\tan^{-1}(x) =$
 $-\tan^{-1}(x)$
 odd function

$$\begin{aligned}
 |0 + j(-318.5)| &= \sqrt{0^2 + (-318.5)^2} \\
 &= 318.5 \\
 \angle 0 + j(-318.5) &= \tan^{-1} \frac{-318.5}{0} \\
 &= -\tan^{-1} \infty \\
 &\angle -90^\circ
 \end{aligned}$$

$$\frac{a}{-b} = -\frac{a}{b} = \frac{-a}{b} = \frac{2.5 \mu A L_0}{2.5 \mu A L_0} + \frac{V_{out} - 0}{-j318.5} = 0$$

$$2.5 \mu A L_0 = \frac{V_{out}}{j318.5}$$


$$2.5 \mu A L_0 = \frac{V_{out}}{318.5 \angle 90^\circ}$$


$$V_{out} = 2.5 \mu A L_0 \cdot 318.5 \angle 90^\circ$$

$$\frac{t_d}{T} \cdot 360 = 90$$

$$t_d = T \cdot \frac{1}{4}$$

$$V_{out} = 0.795 \angle 90^\circ$$

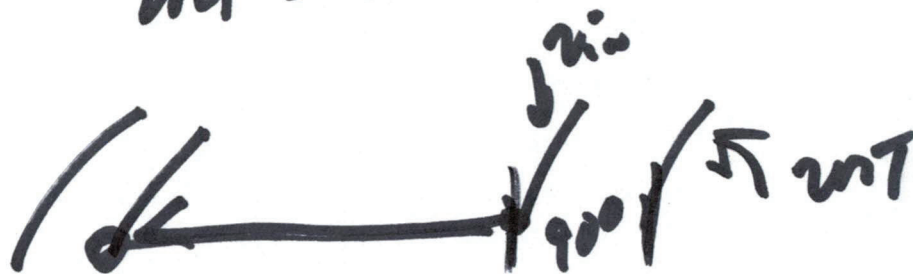

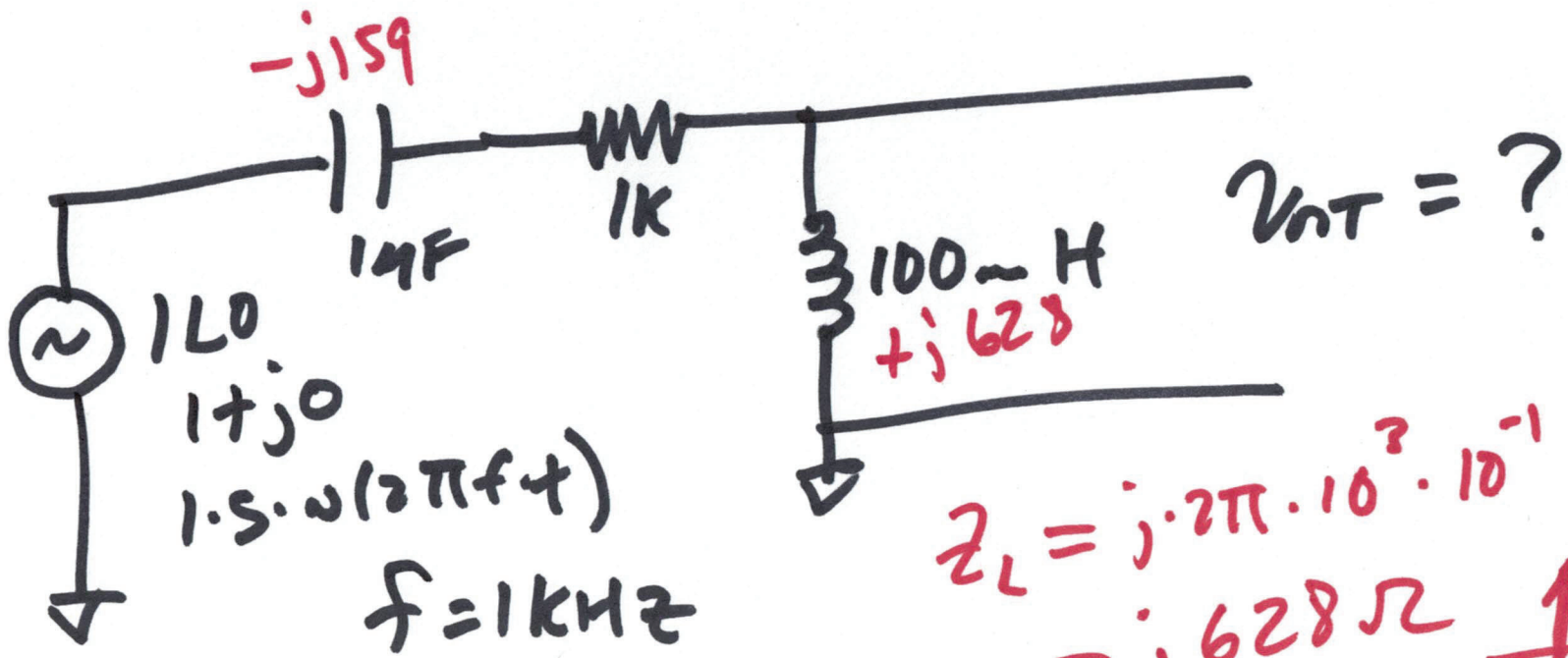

$$Z_L = j \cdot 2\pi \cdot 10^3 \cdot 10^{-1}$$

$$= j628 \Omega$$

$$V_{out} = 1\angle 0 \cdot \frac{j628}{j628 + 10^3 + j(-159)}$$

$$= \frac{628 \angle 90}{1000 + j469} = \frac{628 \angle 90}{1105 \angle 25}$$


$$V_{out} = 568 \text{ mV} \angle 65^\circ$$


$$v_{out}(t) = 568 \text{ mV} \sin(2\pi \cdot 10^3 \cdot t + 65)$$

$\frac{60}{1ms}$

$$\frac{t_d}{1ms} \cdot 360 = 65$$

$$t_d = 180\mu s$$

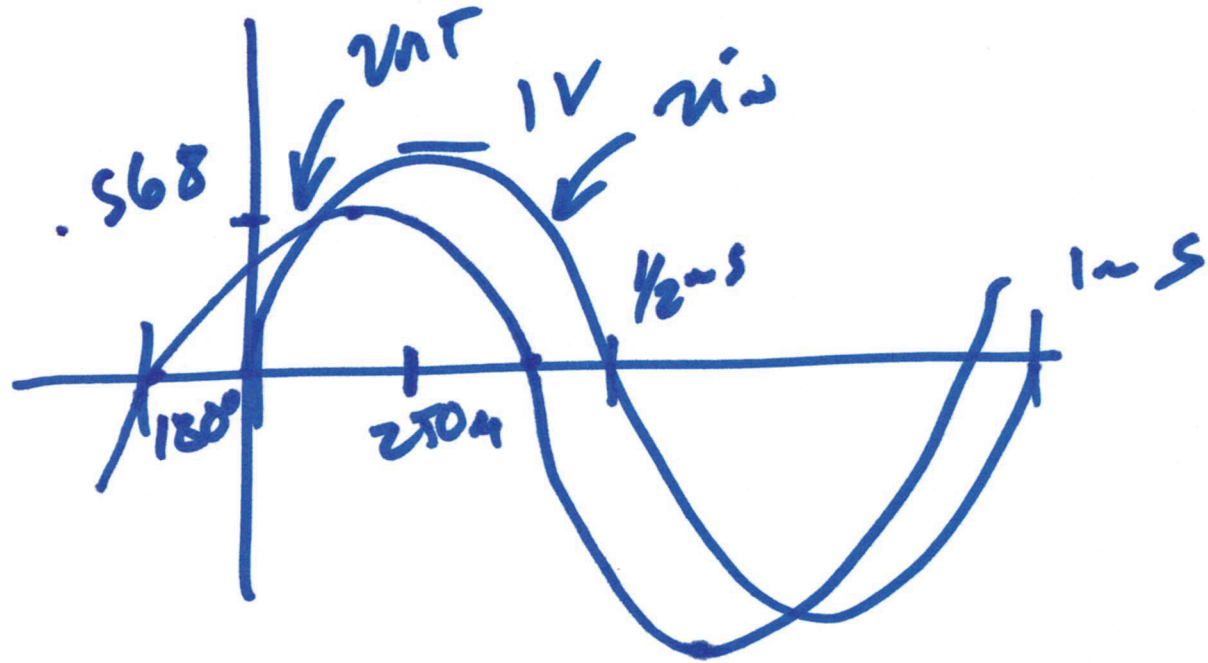


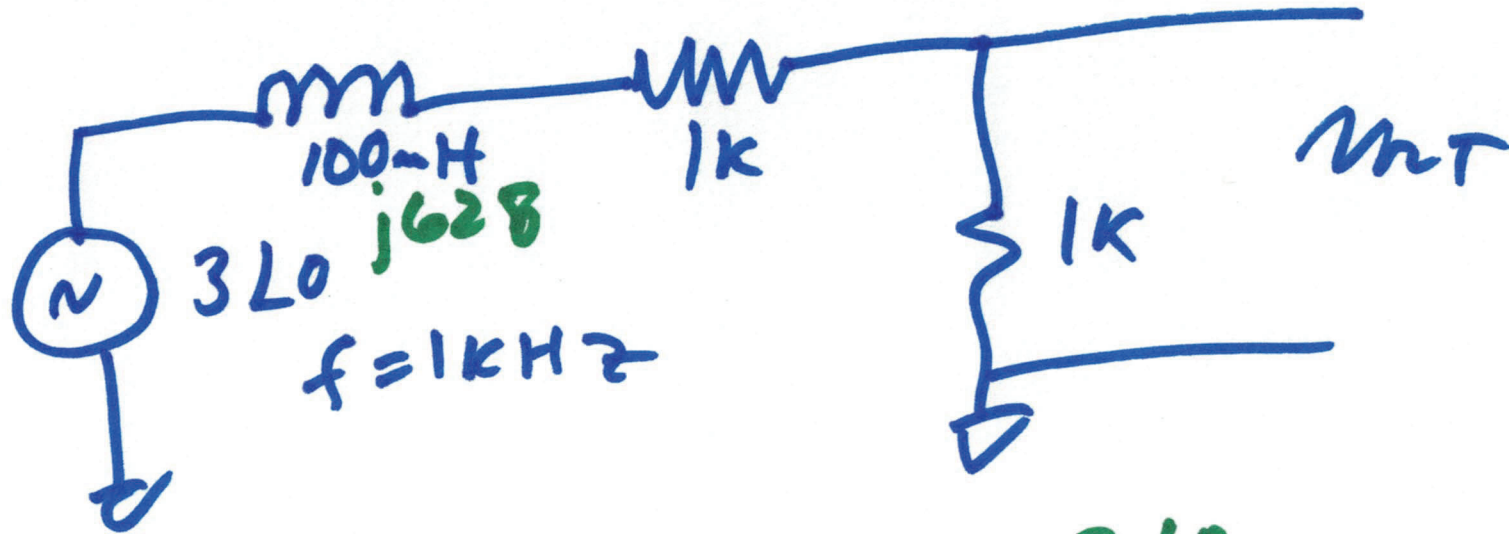

$$\begin{aligned}
 V_{out} &= \frac{10^3 \cdot 320}{10^3 + 10^3 + j628} \\
 &= \frac{320}{2 + j.628} = \frac{320}{2.1 \angle 17.4^\circ} \\
 &= 1.43 \angle -17.4^\circ
 \end{aligned}$$

$$\frac{t_d}{1\text{ms}} \cdot 360 = 17.4$$

$$t_d = 4845$$

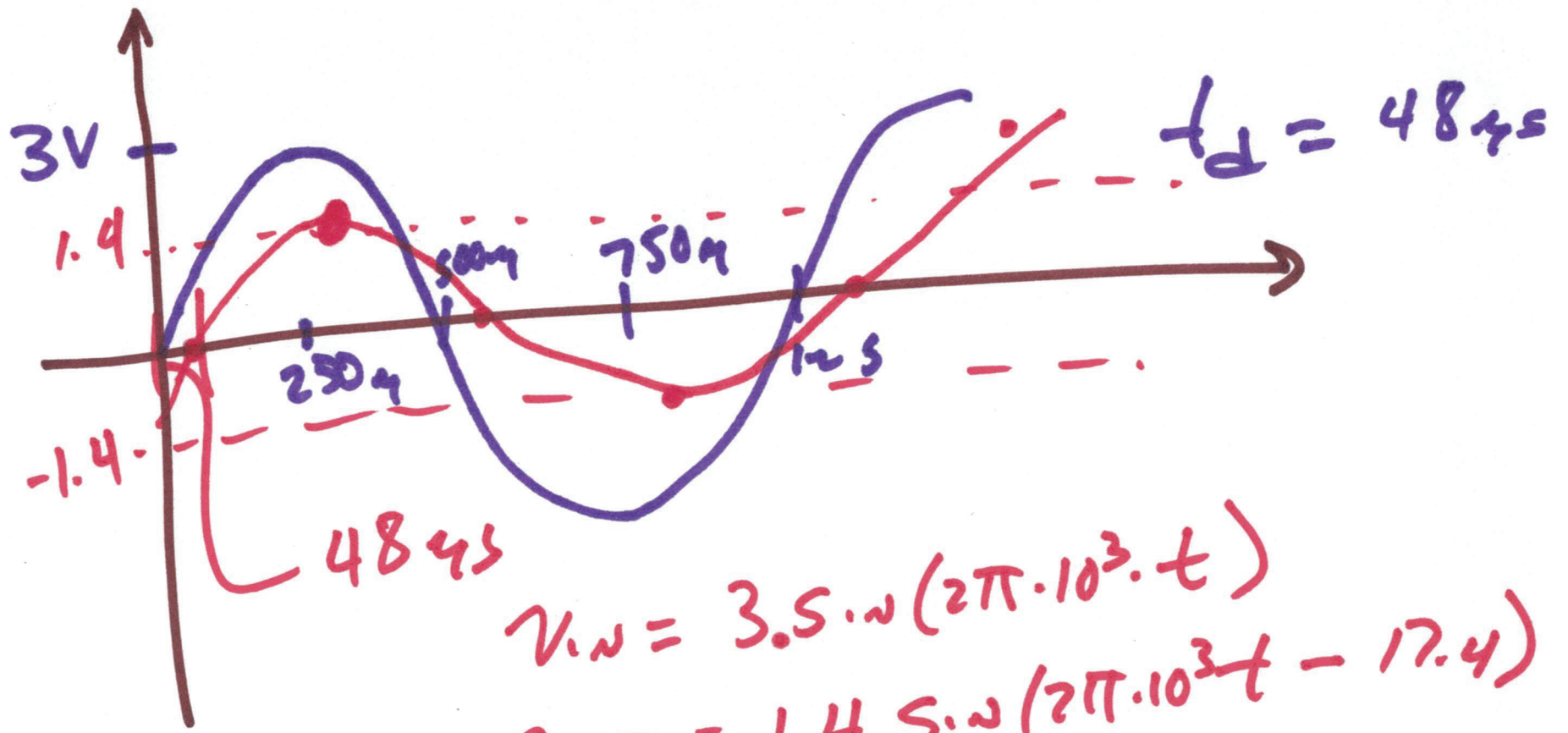

$$v_{in} = 3.5 \sin(2\pi \cdot 10^3 \cdot t)$$

$$v_{out} = 1.4 \sin(2\pi \cdot 10^3 \cdot t - 17.4)$$