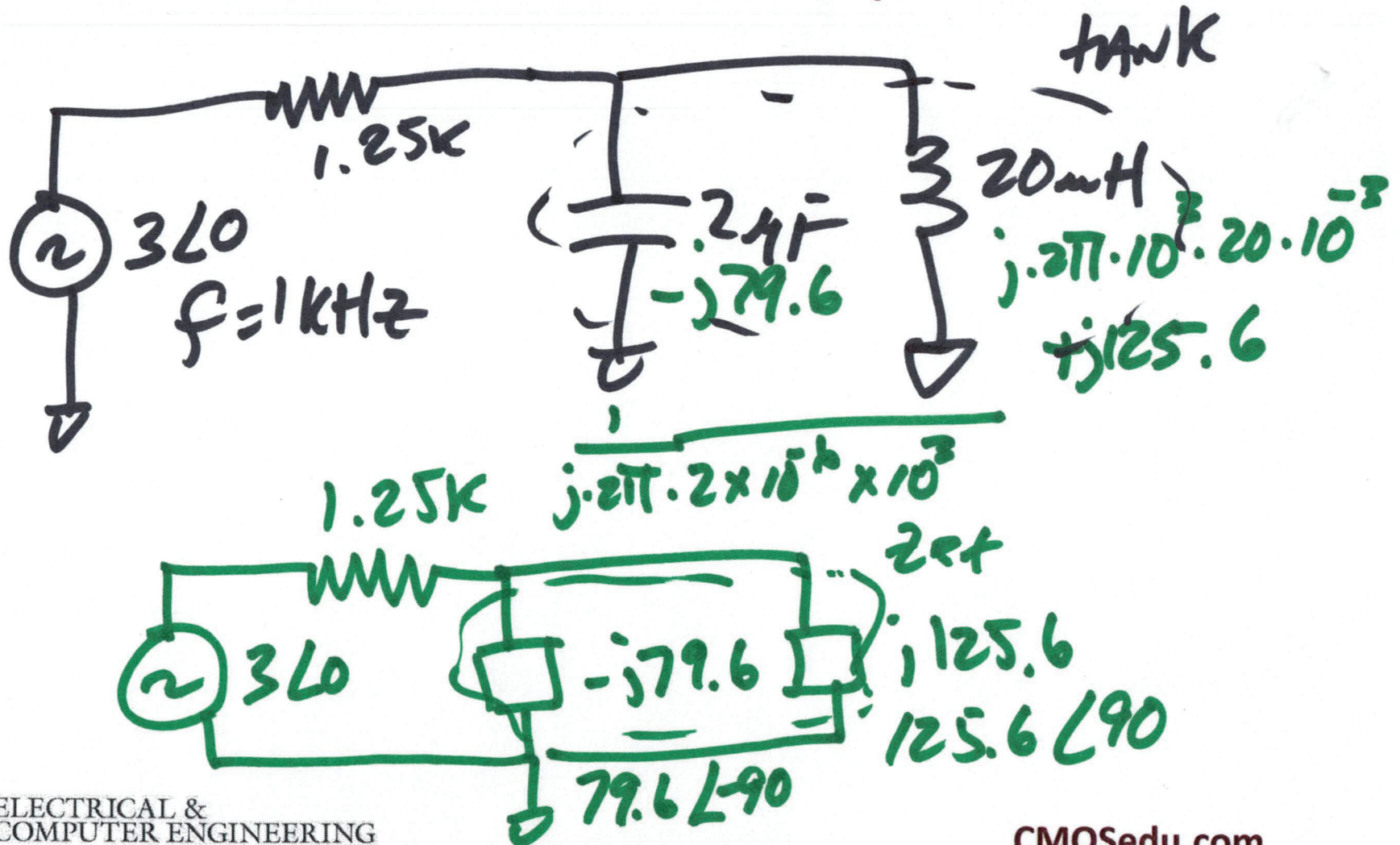


EE 220 Circuits I

Lecture 25

NOVEMBER 29, 2023



$$Z_{eq} = \frac{79.6 \angle -90^\circ \cdot 125.6 \angle 90^\circ}{j(125.6 - 79.6)}$$

$$= \frac{10k \angle 0^\circ}{46 \angle 90^\circ}$$

$$= 217.4 \angle -90^\circ$$

$$Z_{eq} = 217.4 \angle -90^\circ$$


$$Re = 217.4 \cos(-90^\circ)$$


$$Im = 217.4 \sin(-90^\circ)$$

$$I_m = -217.4$$

$$Z_{eq} = j(-217.4)$$

$$Re + j \cdot Im$$

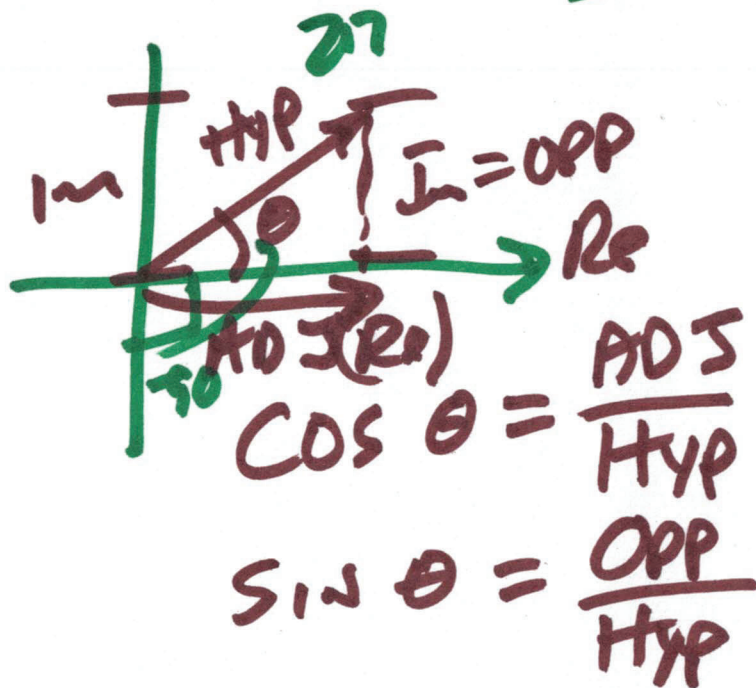

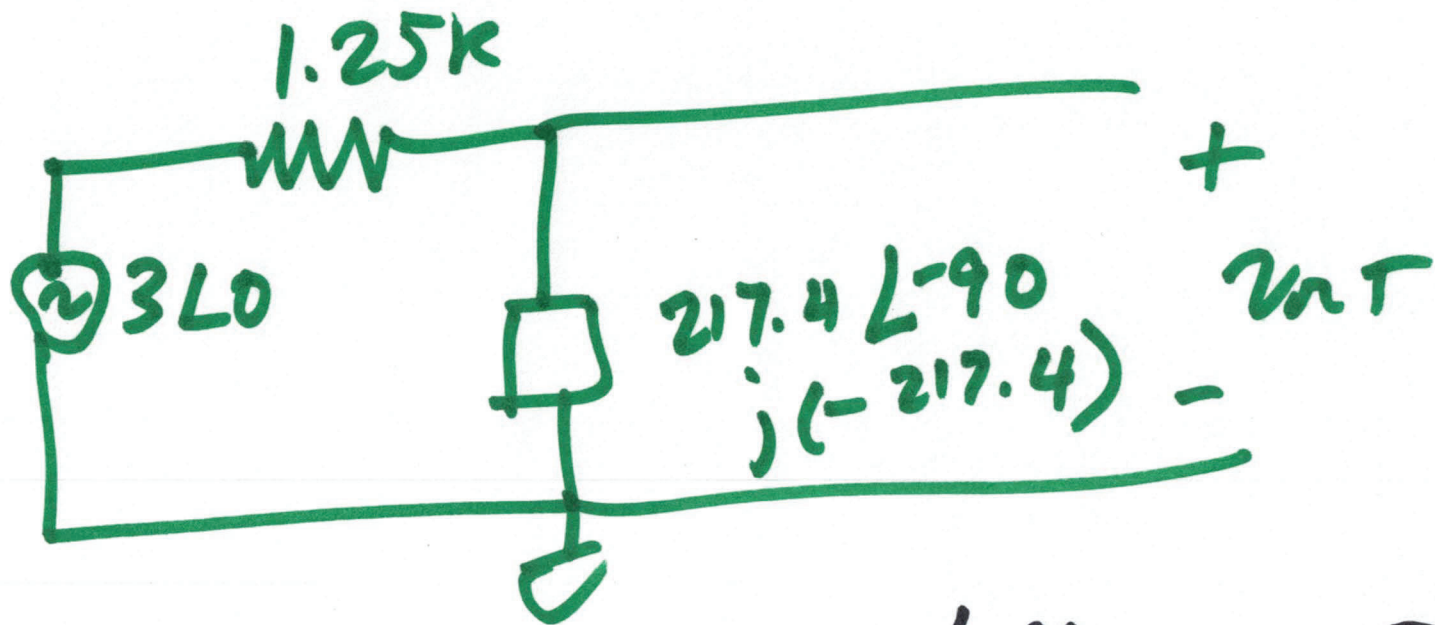

$$V_{th} = \frac{217.4 \angle -90 \cdot 3\text{V}}{1.25\text{k} + j(-217.4)}$$

$$V_{th} = \frac{217.4 \angle -90}{1268.7 \angle -9.8}$$


$$V_{th} = .51 \angle -80.2$$


$$V_{th} = .51 \sin(2\pi 10^3 t - 80.2)$$

$$v_{in} = 3 \sin(2\pi 10^3 t)$$

$$\frac{t_d}{1\mu s} \cdot 360 = 80.2$$

$$t_d = 223\mu s$$

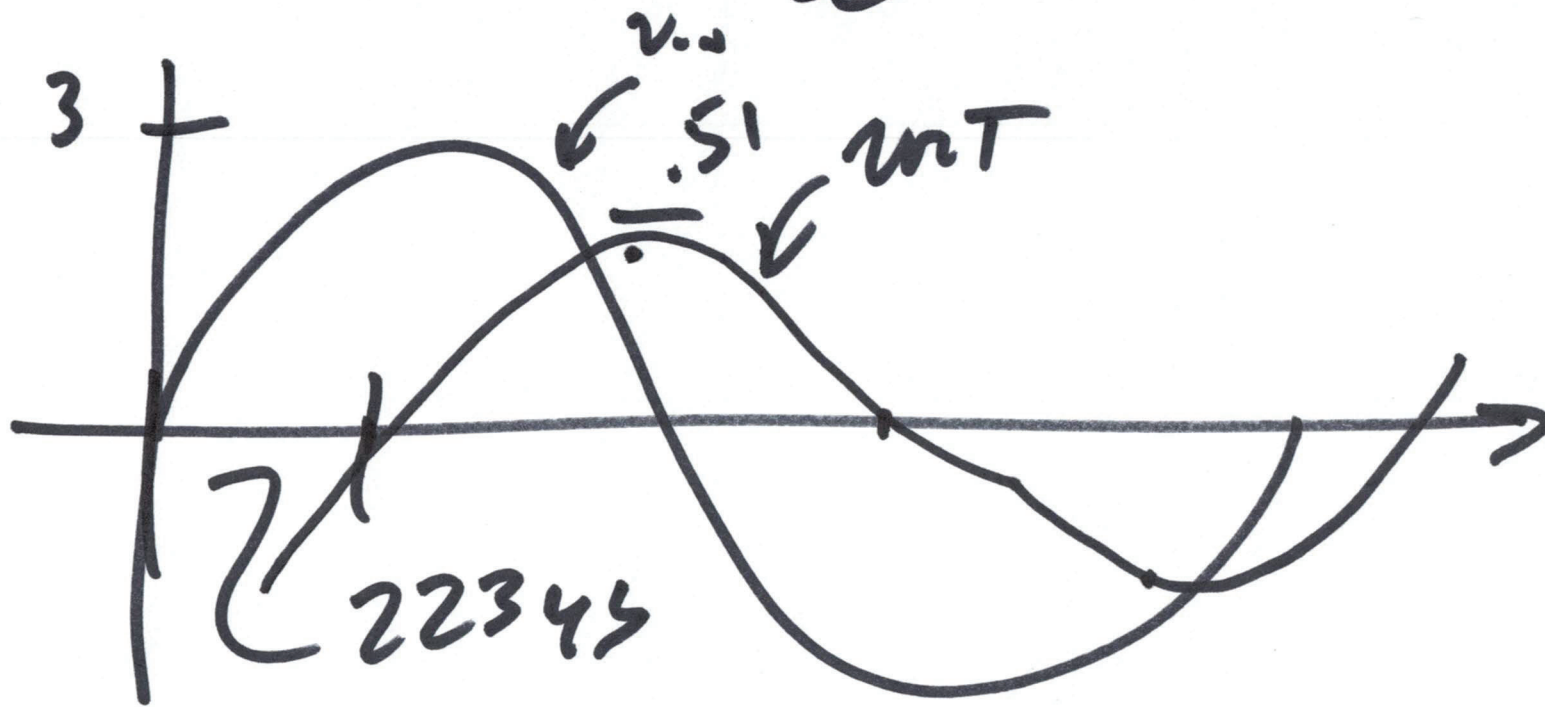

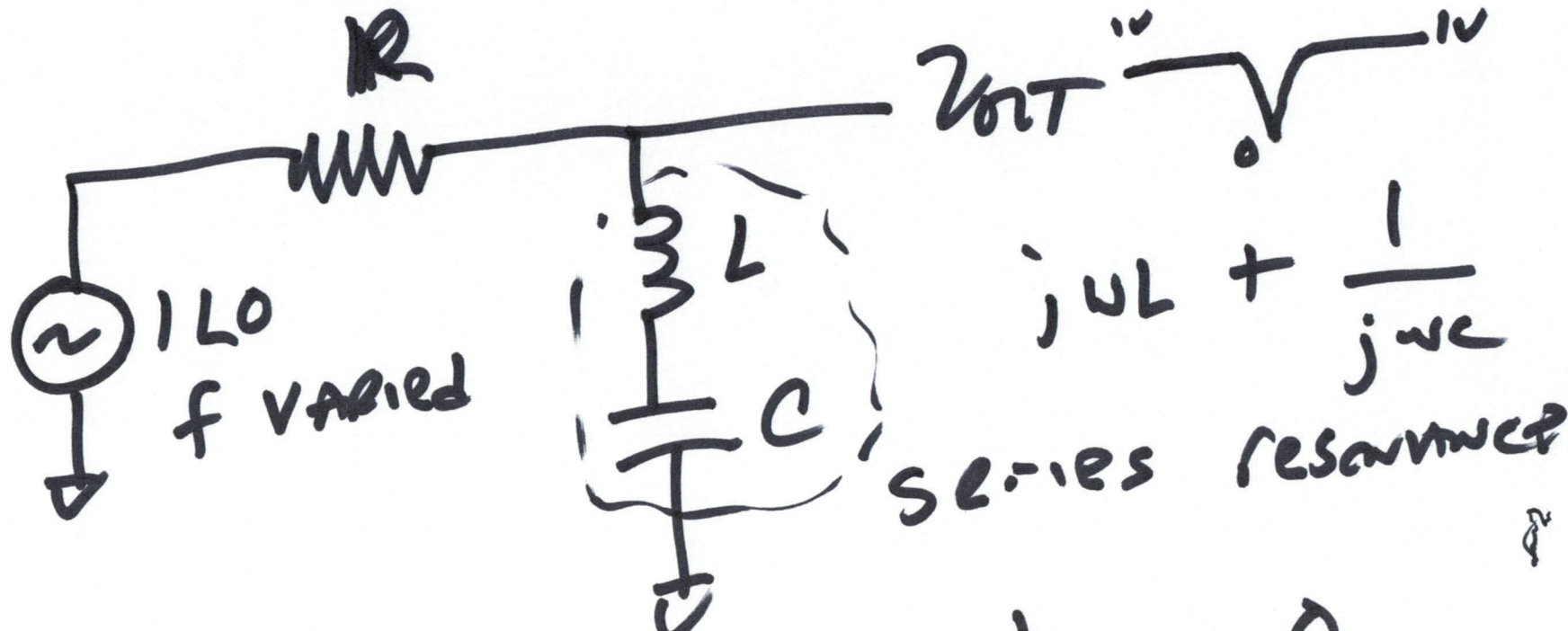


$$j\omega L - j\frac{1}{\omega C} = 0$$

$$f_{res} = \frac{1}{2\pi\sqrt{LC}}$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$
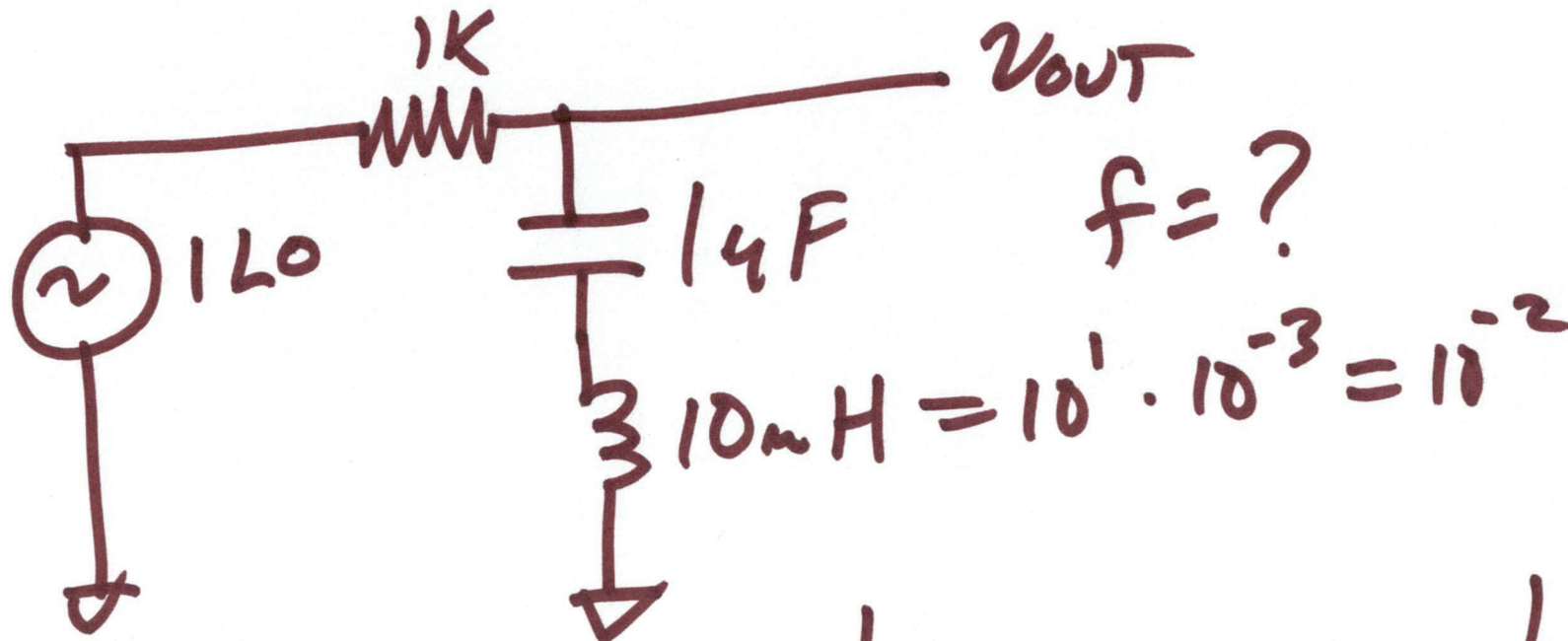
$$\omega^2 = (2\pi f_{res})^2 = \frac{1}{LC}$$



$$f_{res} = \frac{1}{2\pi \sqrt{10^{-6} \cdot 10^{-2}}} = \frac{1}{2\pi \sqrt{10^{-8}}}$$

$20 \log V$

$$f_{res} = 1592.4 \text{ Hz}$$

$$V = 1$$

$$20 \log 1 = 0 \text{ dB}$$

$$20 \log \frac{1}{10} = 20 \log 10^{-1} = -20 \text{ dB}$$

6)



parallel resonance

$$Z_{eq} = \frac{j\omega L \cdot \frac{1}{j\omega c}}{\left(\frac{1}{j\omega c} + j\omega L\right) \rightarrow 0} = \frac{L}{c}$$

$$f_{res} = \frac{1}{2\pi\sqrt{LC}}$$

$$Z_{eq} \rightarrow \infty$$