

EE 220

Circuits I


Lecture 2

$I = -2\text{A}$

Aug. 30, 2023
 $V_x = 8\text{V}$

2023

Ohm's law

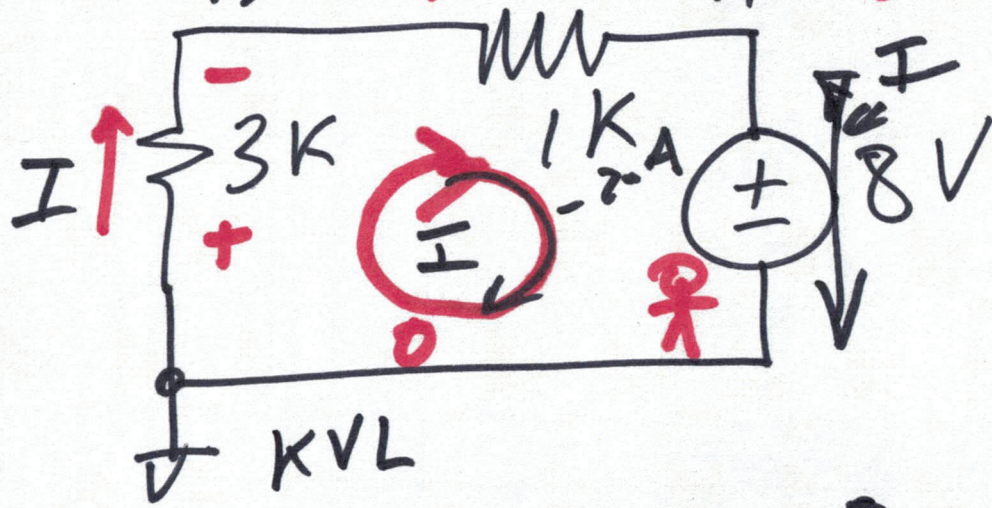

Ohm's law


$$V = IR$$

Amp Ω

$$+I \cdot 1\text{k} + I \cdot 3\text{k} + 8 = 0$$

$$I = \frac{-8}{4\text{k}} = -2\text{A}$$

$$V = -IR$$

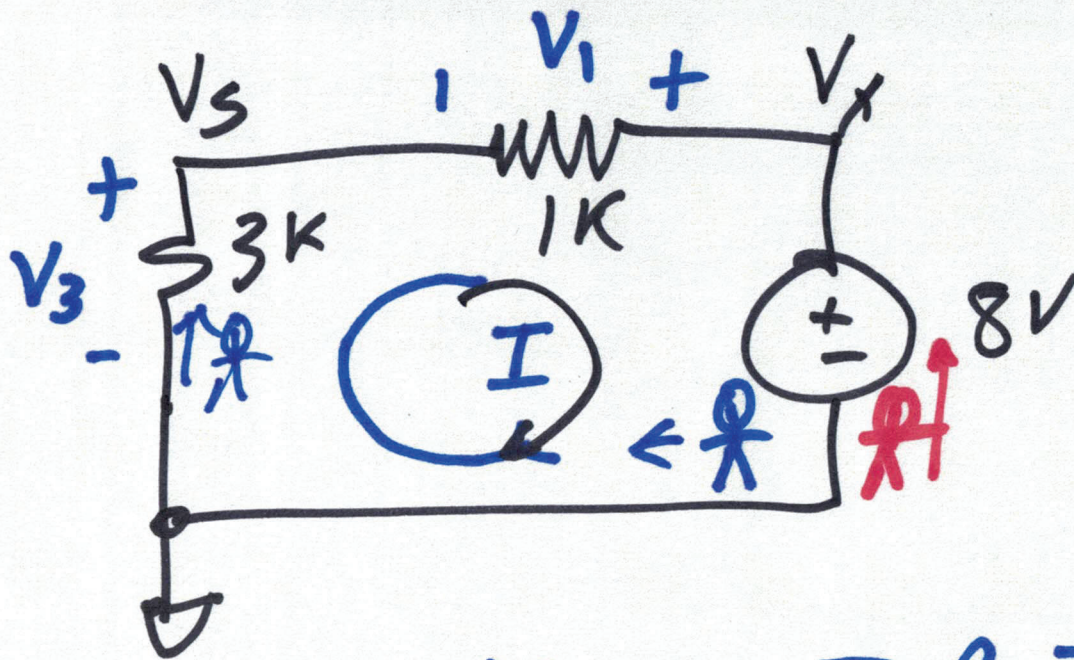

$$\left. \begin{array}{c} \uparrow \\ \downarrow \end{array} \right\} V = -IR$$

$$V_3 = -I \cdot R = -I \cdot 3k$$

$$V_1 = -I \cdot R = -I \cdot 1k$$


$$+V_3 + V_1 - 8 = 0 \rightarrow -I \cdot 3k - I \cdot 1k - 8$$

$$+8 - V_1 - V_3 = 0$$

$$\downarrow$$

$$-I \cdot 4k = 8$$

$$I = -2\mu A$$


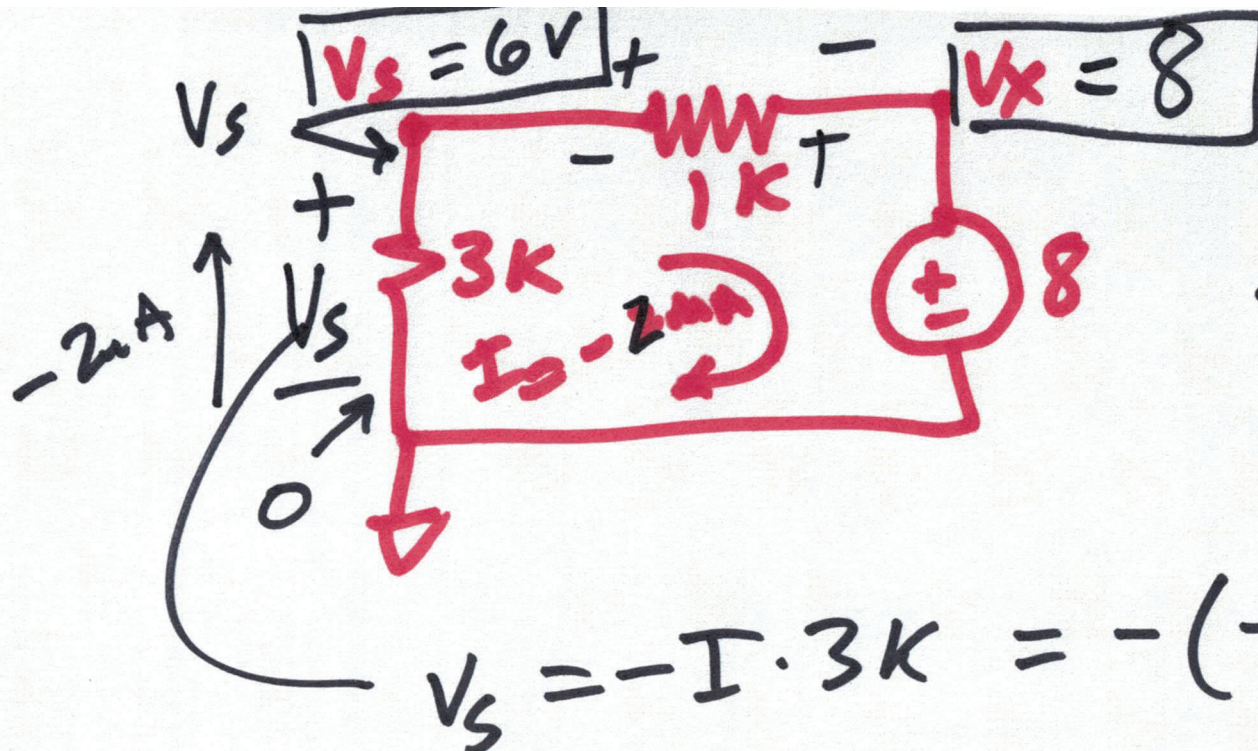


$$V = -I \cdot R$$

$$V_s = -I \cdot 3\text{k} = -(-2\text{A}) \cdot 3\text{k} = 6\text{V}$$


$$8 - 6 = 2$$


$$6 - 8 = -2$$

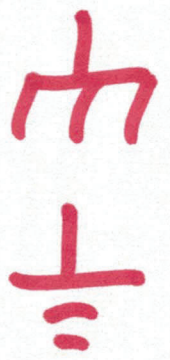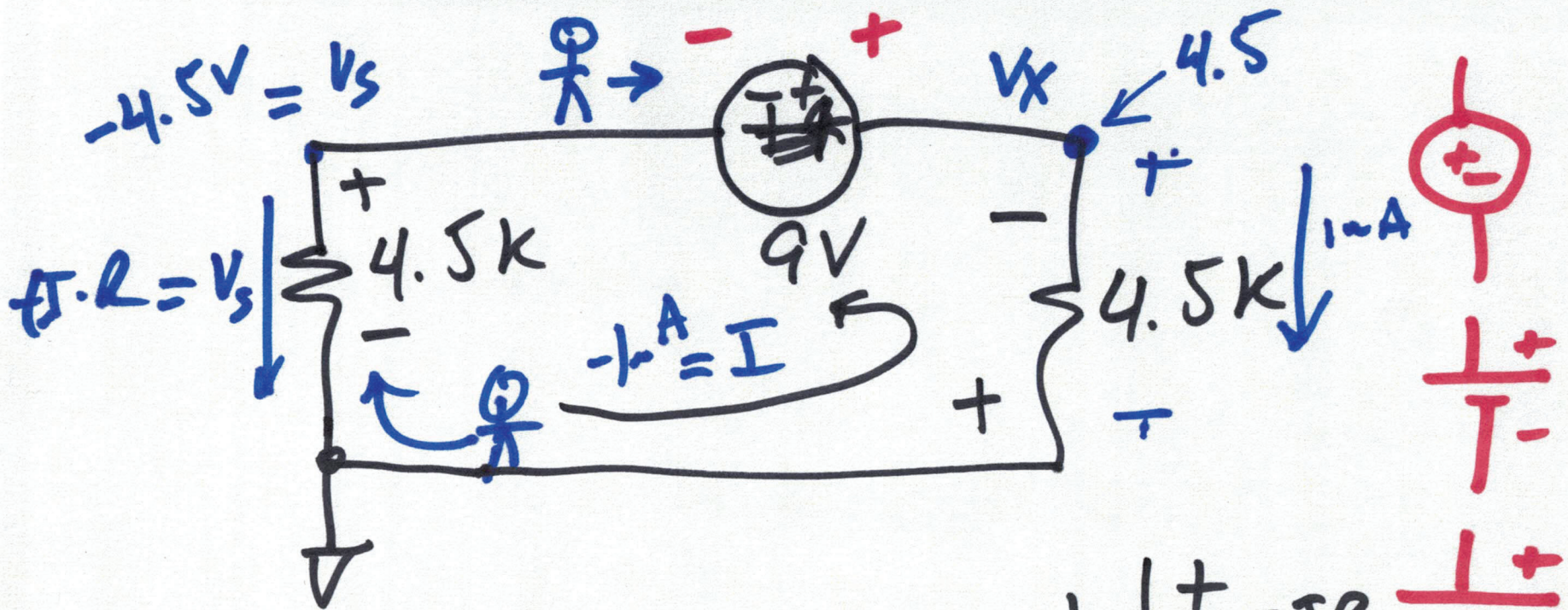

$$+9 + I \cdot 4.5k + I \cdot 4.5k = 0$$


$$I = -1mA$$

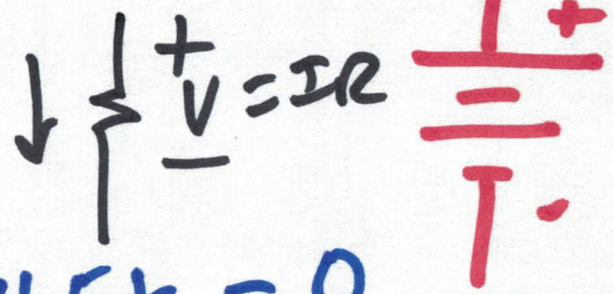

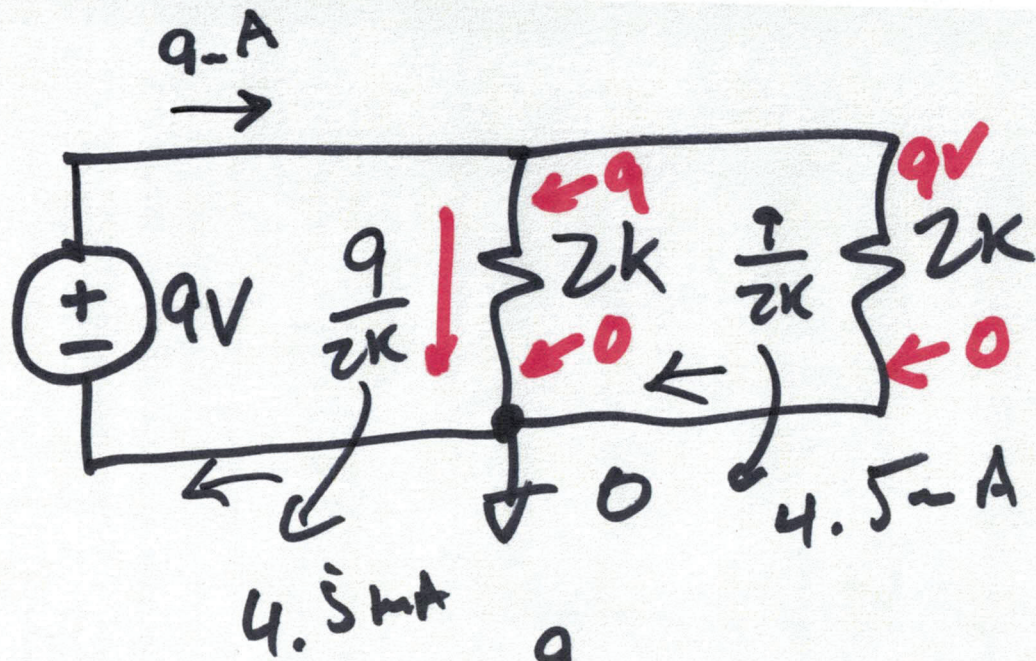

$$I = \frac{V}{R}$$
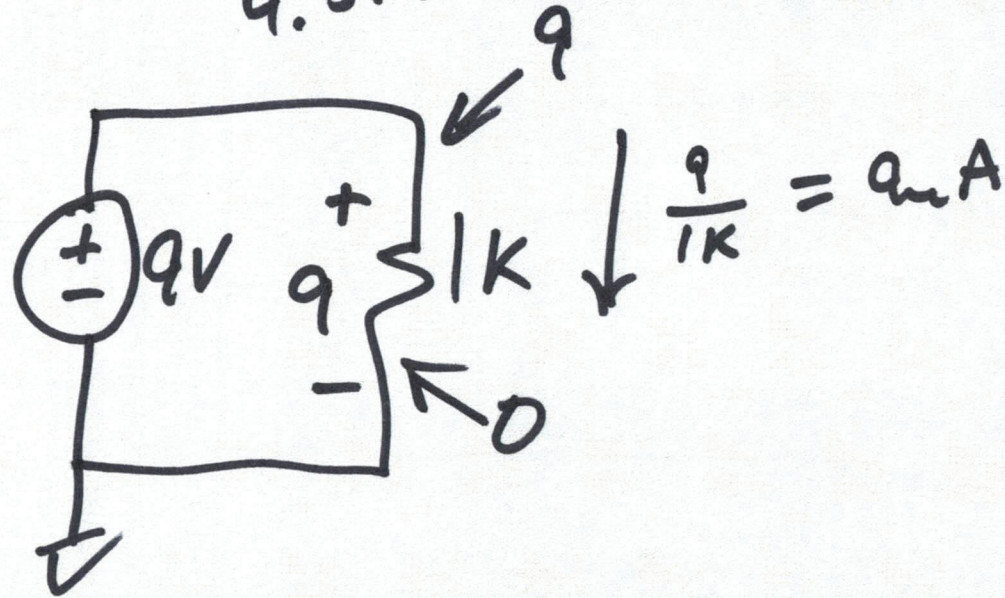
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$



$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\frac{1000}{X} = \frac{1000}{20} + \frac{1000}{30}$$

$$\frac{1}{X} = \frac{1}{20} + \frac{1}{30}$$

$$\frac{1}{\text{TOT}} = \frac{1}{h_1} + \frac{1}{h_2} + \frac{1}{h_3}$$


$$1 = \frac{X}{X} = X \left(\frac{1}{20} + \frac{1}{30} \right)$$

$$1 = X \left(\frac{30 \cdot 1}{20 \cdot 30} + \frac{20 \cdot 1}{30 \cdot 20} \right)$$

$$1 = X \left(\frac{30 + 20}{20 \cdot 30} \right)$$


$$X = \frac{20 \cdot 30}{20 + 30} = \frac{600}{50} = 12 \text{ hrs}$$

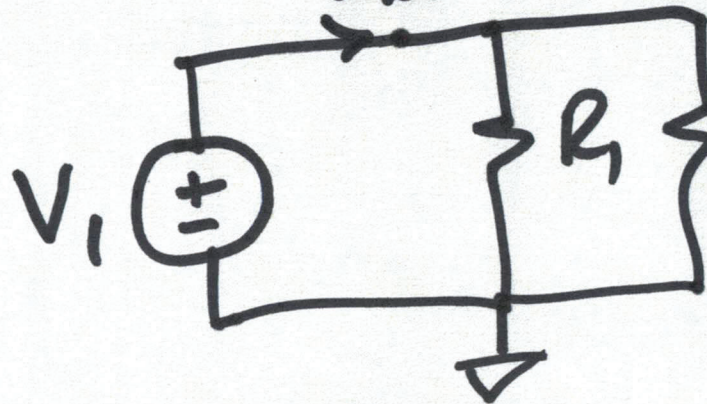$V = I \cdot R$ SERIES R_3 $R_3 + R_4$ R_4



$$\frac{V_1}{R_1} + \frac{V_1}{R_2} = I_{TOT}$$

parallel

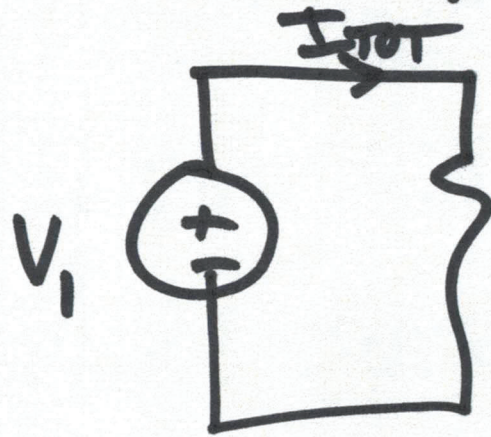


$$\frac{V_1}{R_{eq}} = I_{TOT}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$\frac{V_1}{R_{eq}} = \frac{V_1}{R_1} + \frac{V_1}{R_2}$$

7)

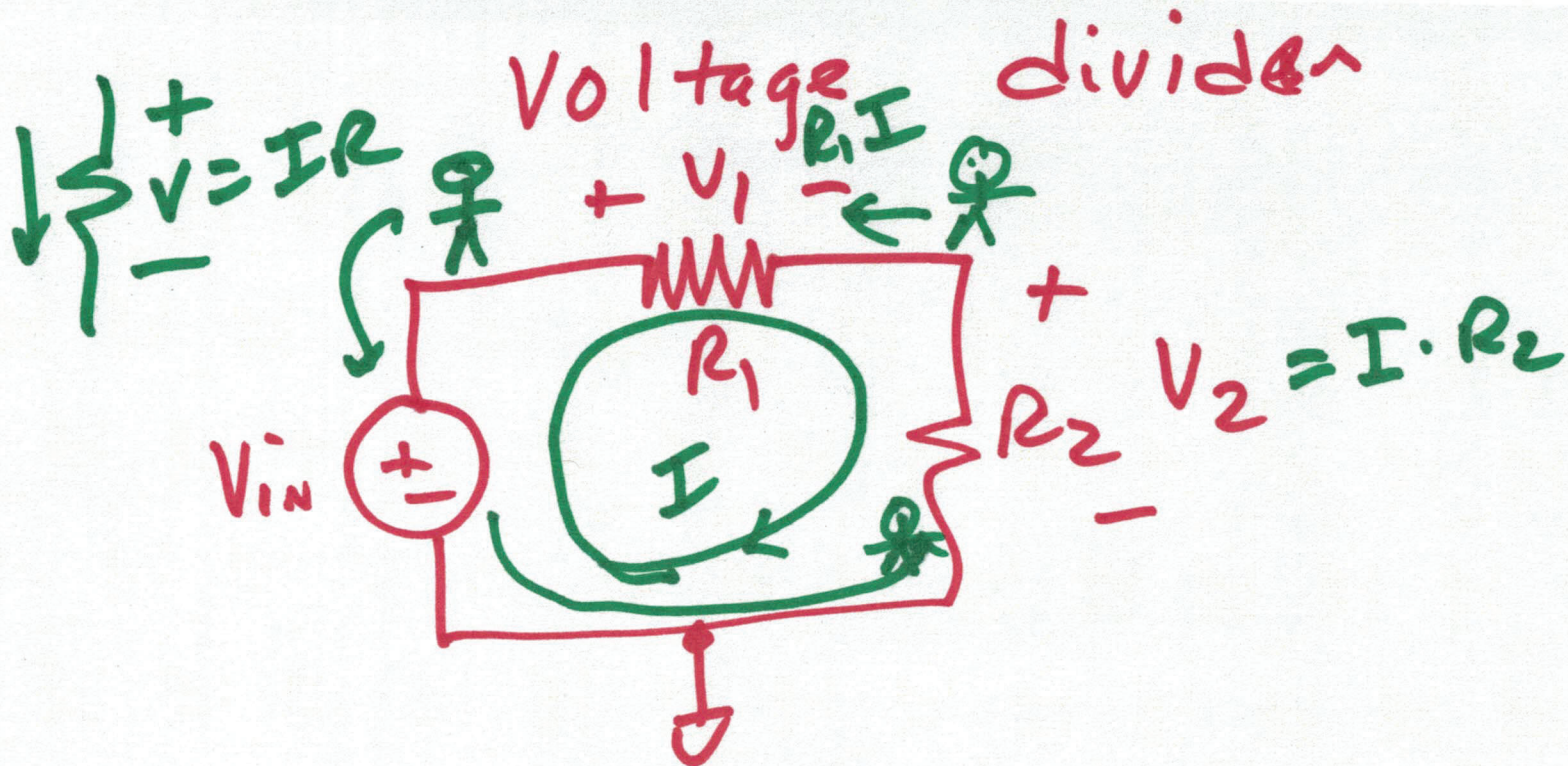

$$-V_{in} + I \cdot R_2 + I \cdot R_1 = 0$$

$$I = \frac{V_{in}}{R_1 + R_2}$$

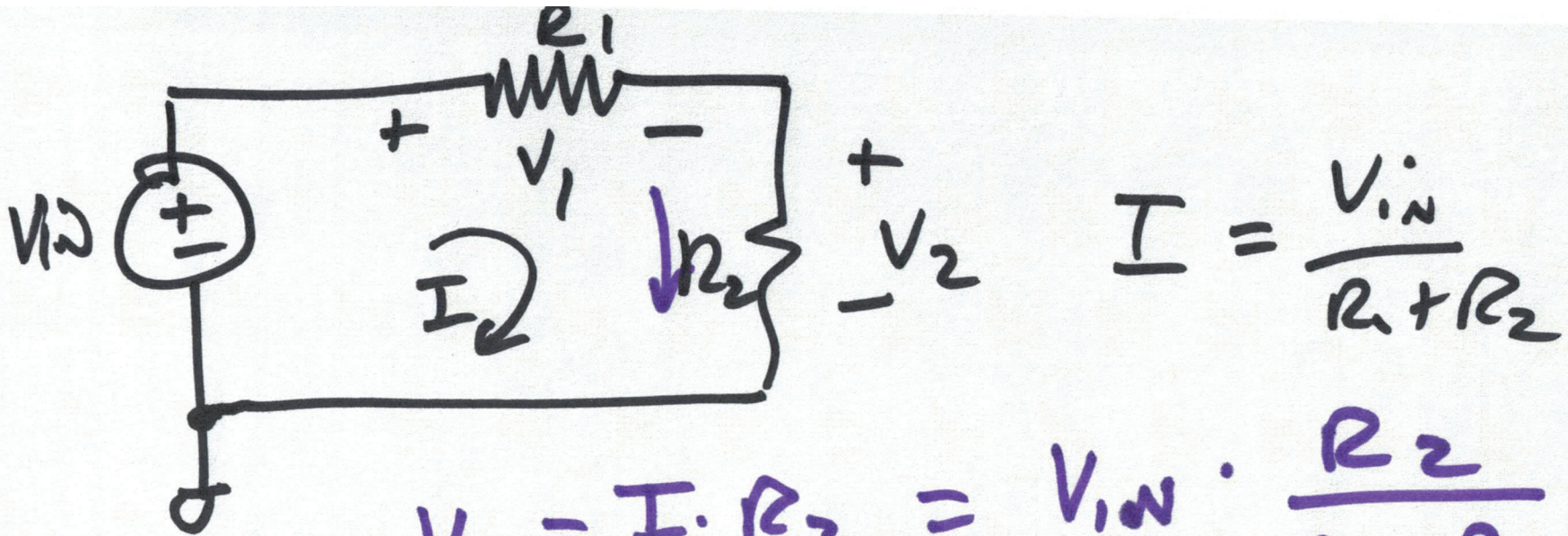


$$V_2 = I \cdot R_2 = V_{IN} \cdot \frac{R_2}{R_1 + R_2}$$

Voltage divider

$$V_2 = V_{IN} \cdot \frac{R_2}{R_1 + R_2}$$

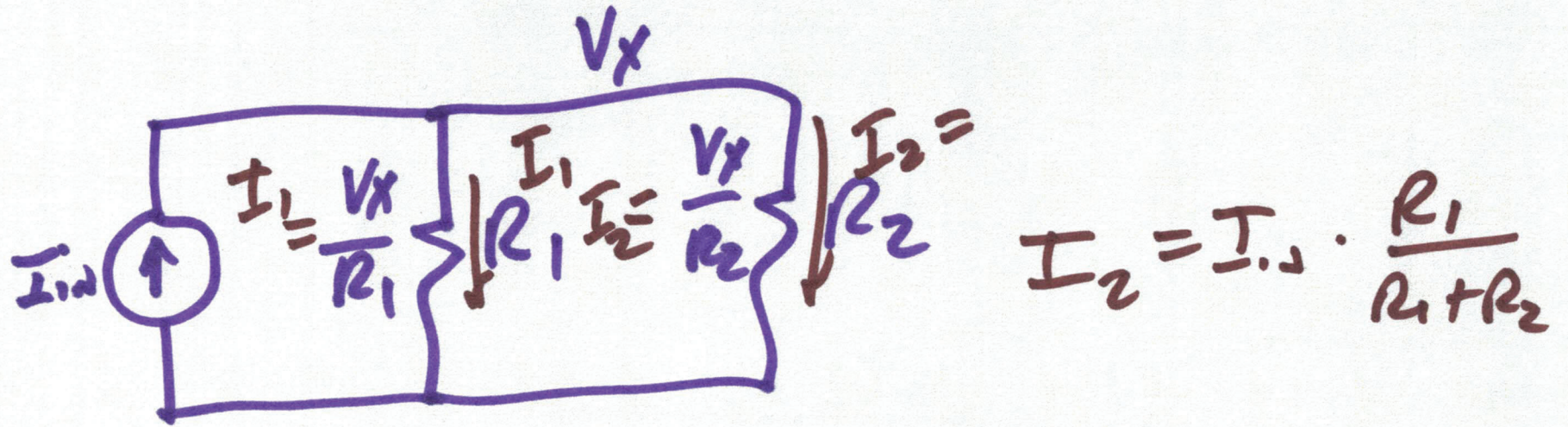
$$V_1 = V_{IN} \cdot \frac{R_1}{R_1 + R_2}$$



$$I_{in} = \frac{V_x}{R_1} + \frac{V_x}{R_2}$$


$$I_1 = I_{in} \cdot \frac{R_2}{R_1 + R_2} \quad V_x = \frac{I_{in}}{\frac{1}{R_1} + \frac{1}{R_2}}$$


CURRENT divider

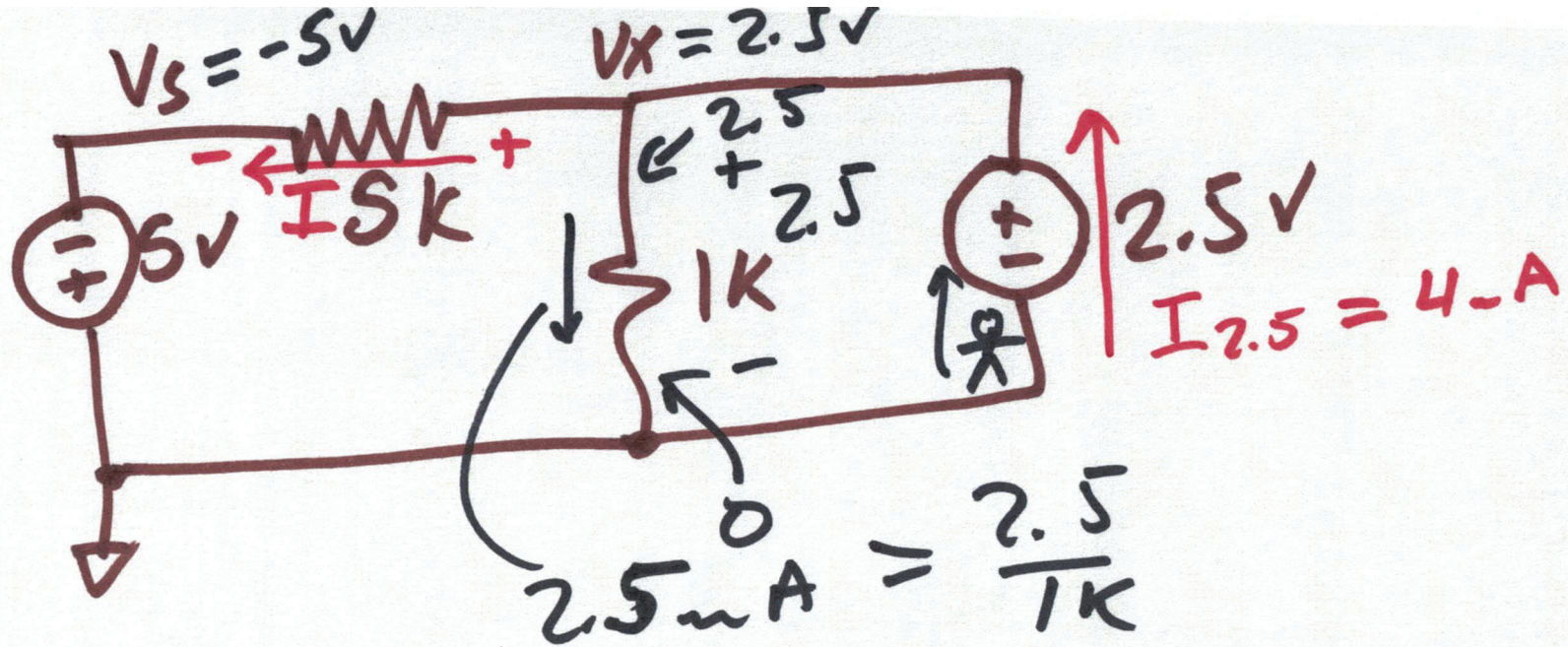


$$I = \frac{2.5 - (-5)}{5k} = \frac{7.5}{5k} = 1.5\mu A$$

$1.5\mu A$ $5k$ $4A$ $5k$

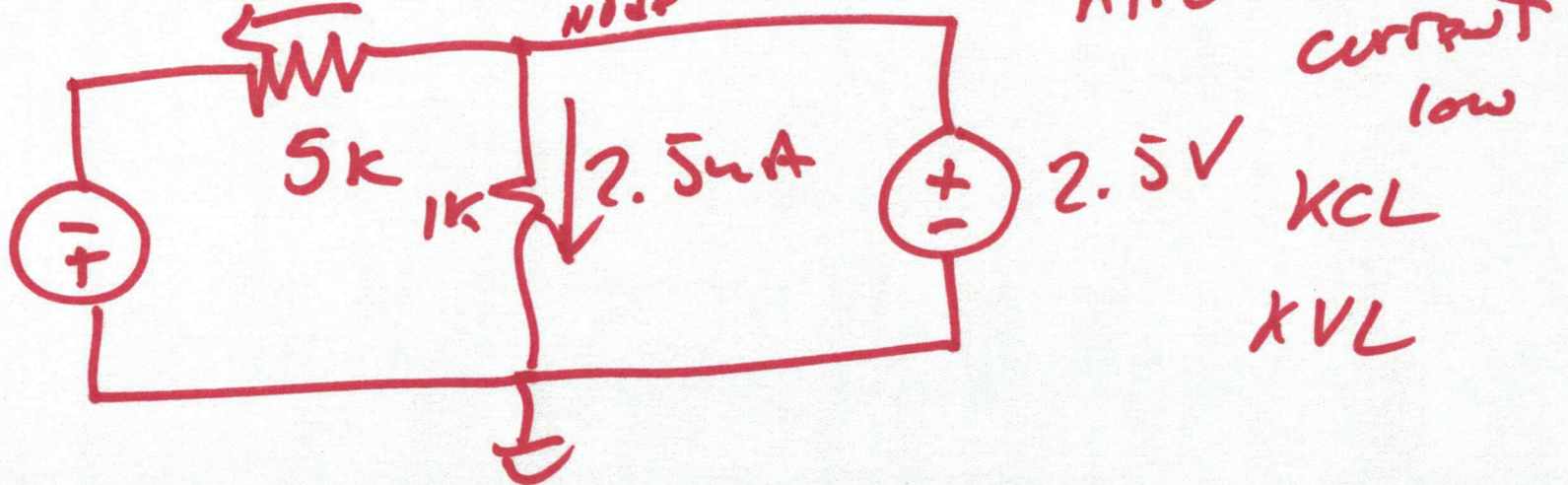

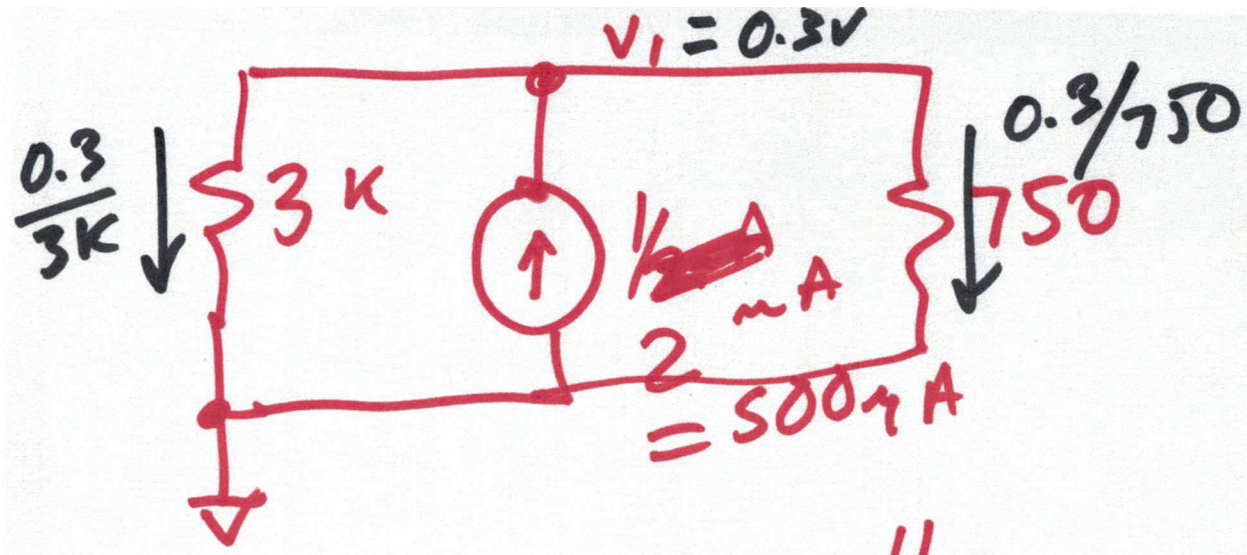

$750 \parallel 3k$

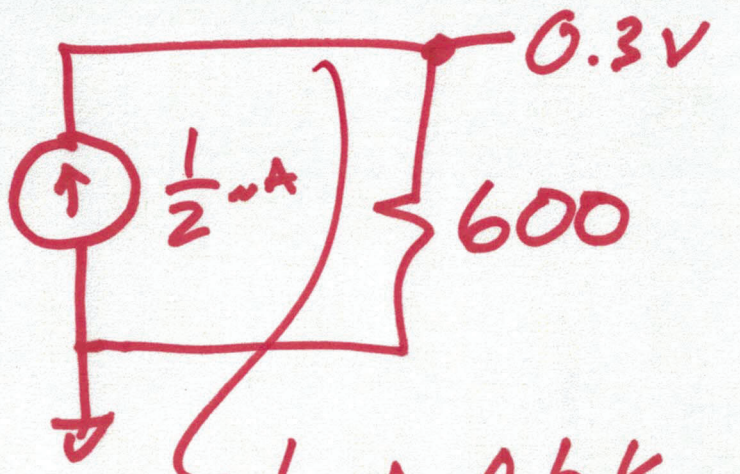

$\frac{1}{2} \mu A \cdot 0.6k$

$= 0.3V$


$$5 \overline{) 150} \\ \underline{750} \\ 500 \\ \underline{250}$$

$$\frac{750 \cdot 3000}{750 + 3000} = \frac{750 \cdot 750 \cdot 4}{750 \cdot 5}$$

$$= 150 \cdot 4$$

$$600$$

2)

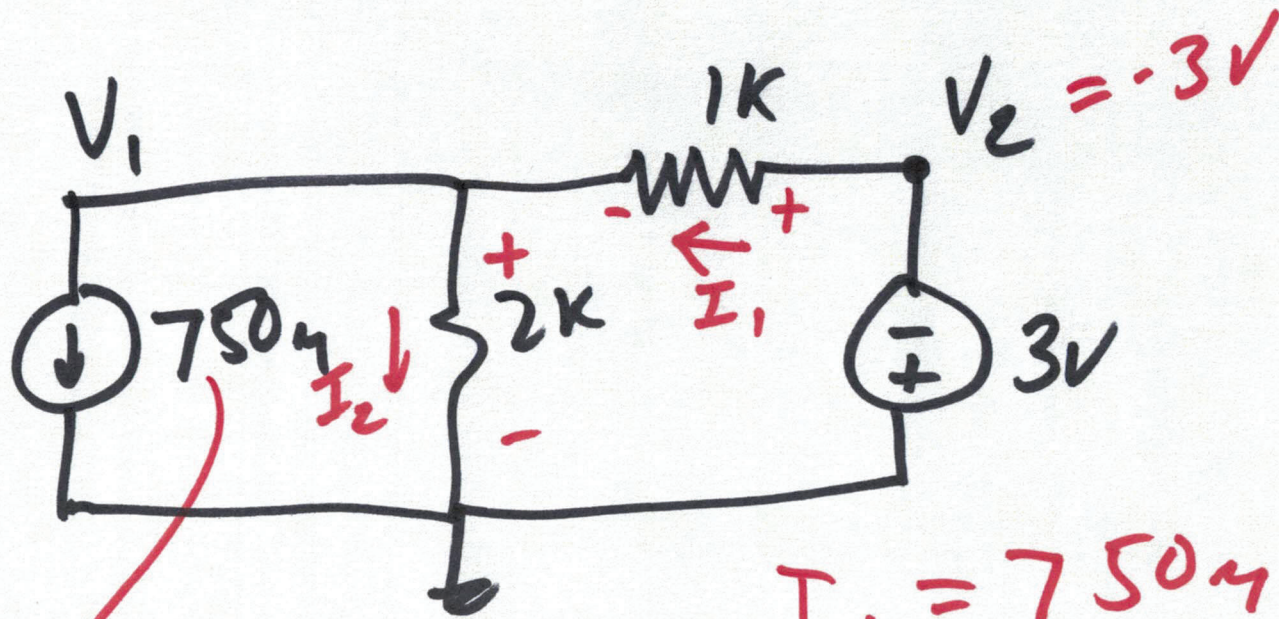

$$I_1 = 750\mu + I_2 \quad \text{KCL}$$

$$-3V - I_1 \cdot 1k - I_2 \cdot 2k = 0$$

750 μ A KVL

$$= 0.75\mu\text{A}$$

$$= 0.00075\text{A}$$

13)