


EE 220




Circuits I


September 11, 2023

$$1\text{A} + \frac{V_x}{3\text{k}} + \frac{V_x}{3\text{k}} = 0$$

Lecture 4 $V = IR$

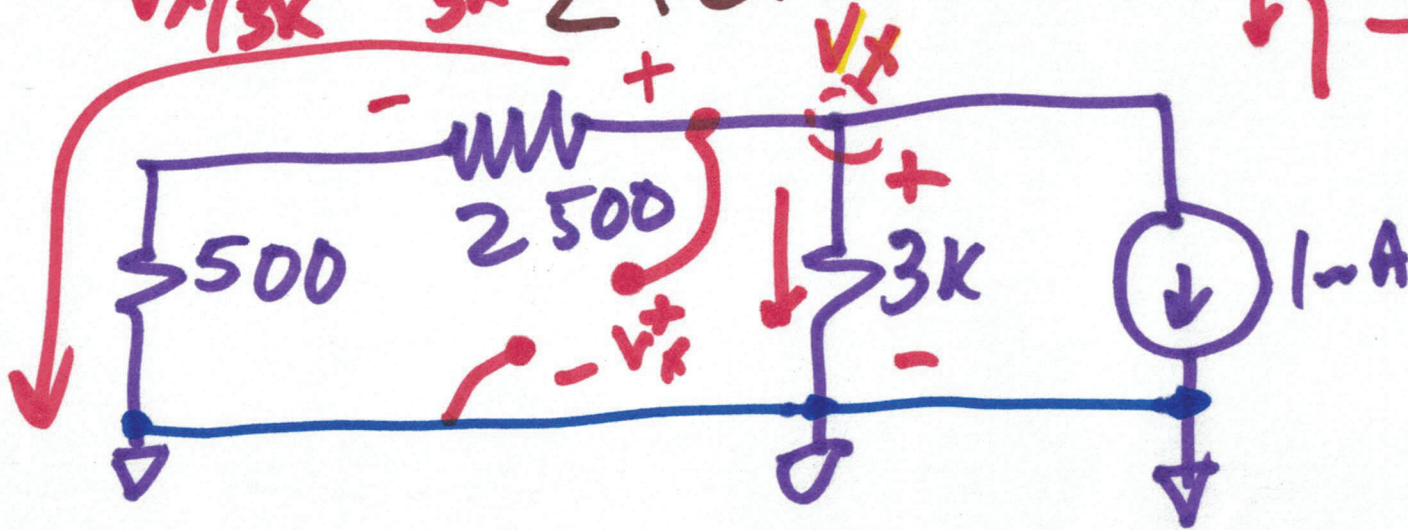

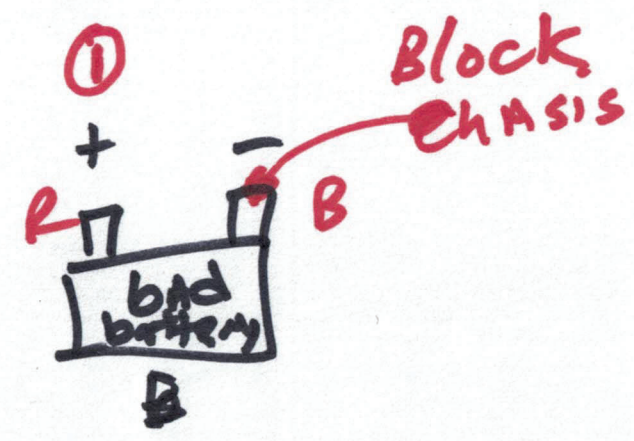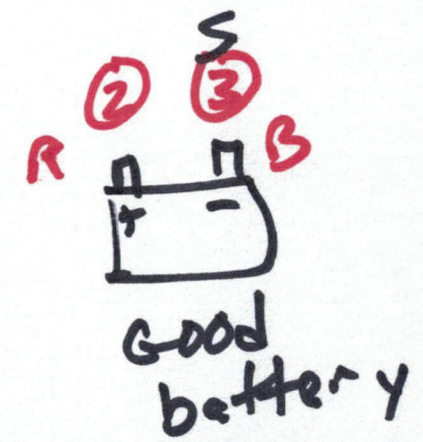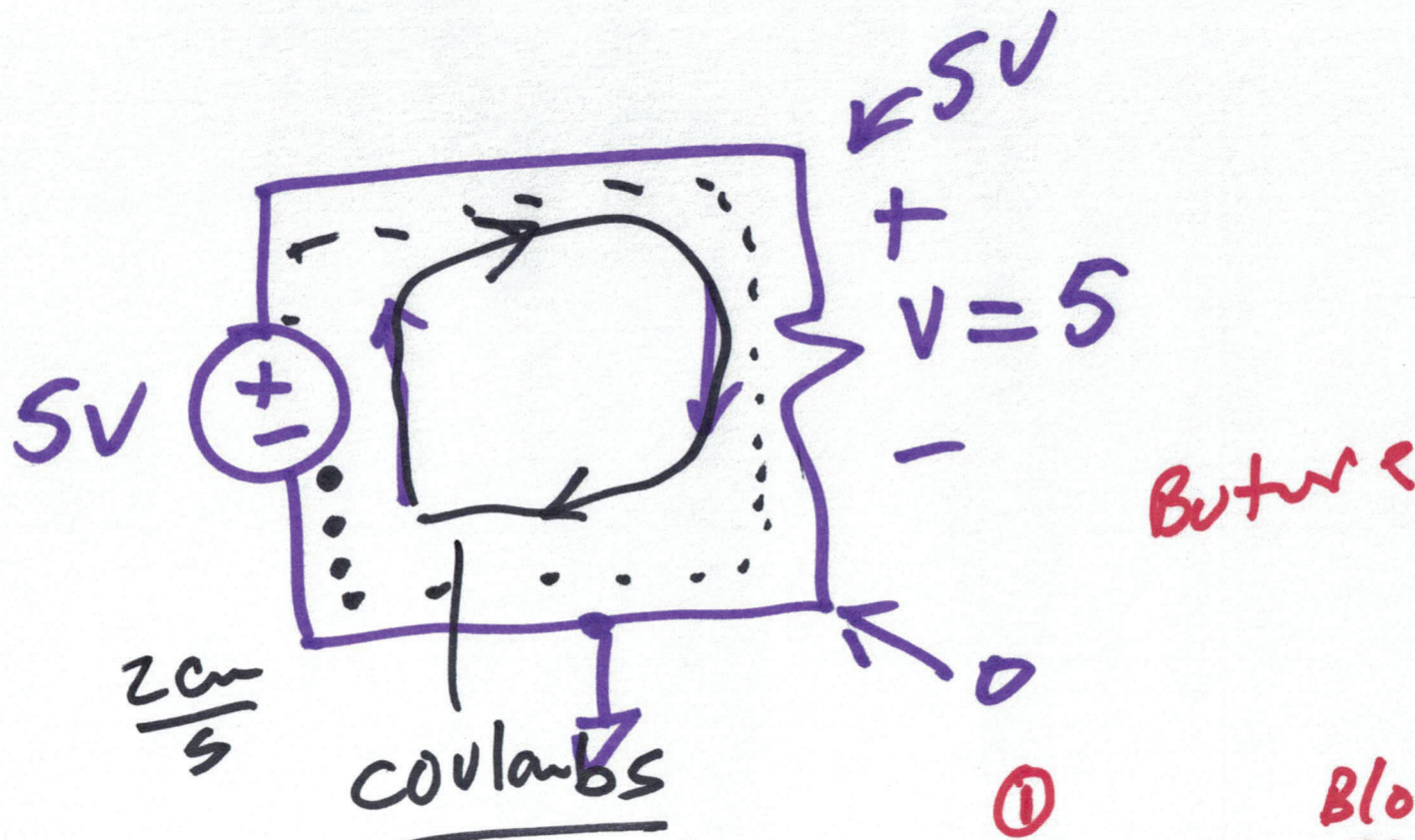

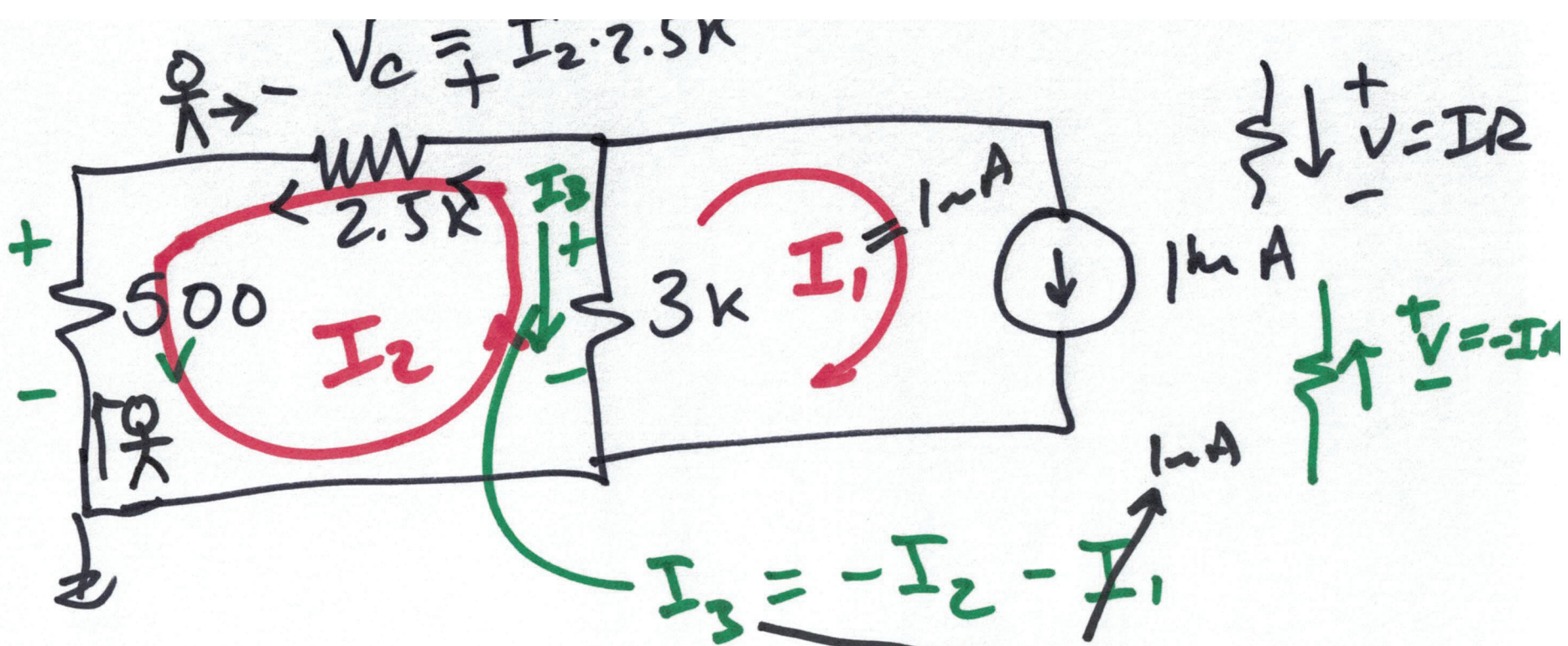


$$+500I_2 + 2.5kI_2 - 3kI_3 = 0$$

$$500I_2 + 2.5kI_2 - 3k(-I_2 - 1\mu A) = 0$$


$$3000I_2 + 3000I_2 + 3V = 0$$
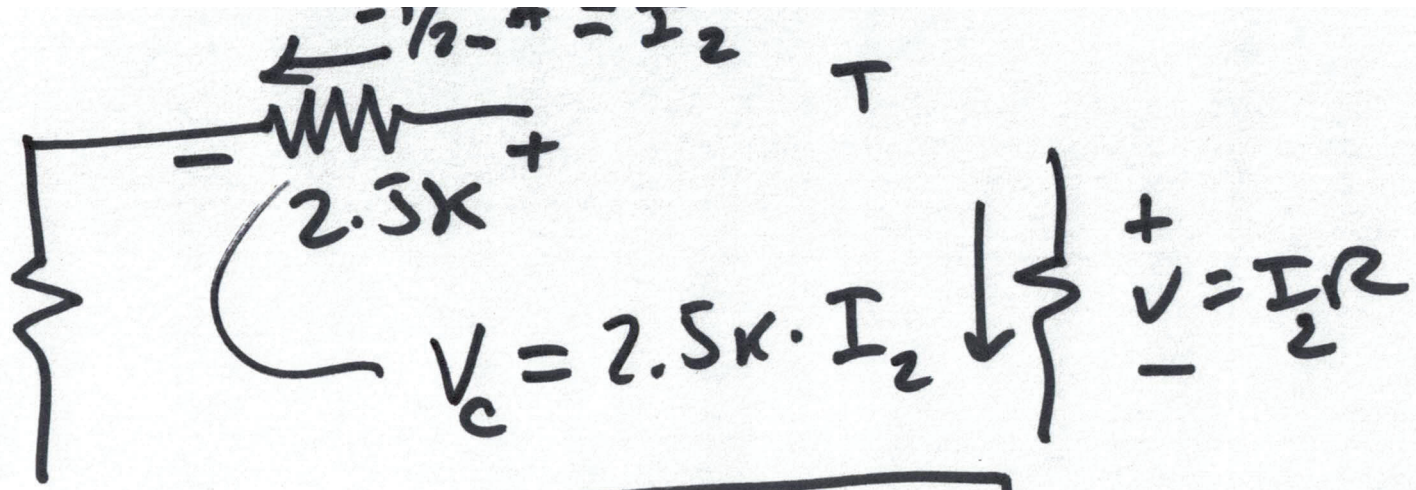
$$I_2 = \frac{-3}{6000} = -\frac{1}{2} \mu A$$



$$V_c = -1.25V$$
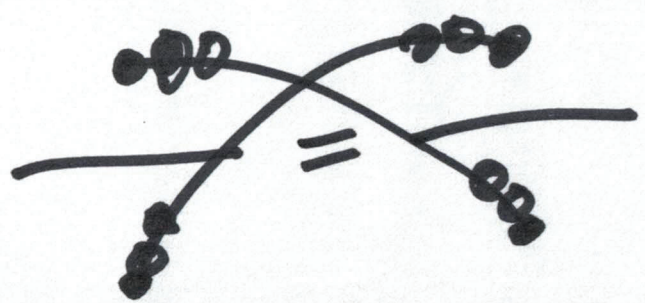
$$\frac{5ABX}{(X+5)C} = \frac{C \cdot (A+1)}{D \cdot (X+3)}, \quad D = \frac{(X+5)C \cdot C \cdot (A+1)}{5ABX(X+3)}$$



4)

Superposition


$\dots = 10^{-3} = \frac{1}{K} = \frac{1}{10^3}$

Look one source at a time

Voltage sources \rightarrow wire (short)

KVL

Current \rightarrow OPEN

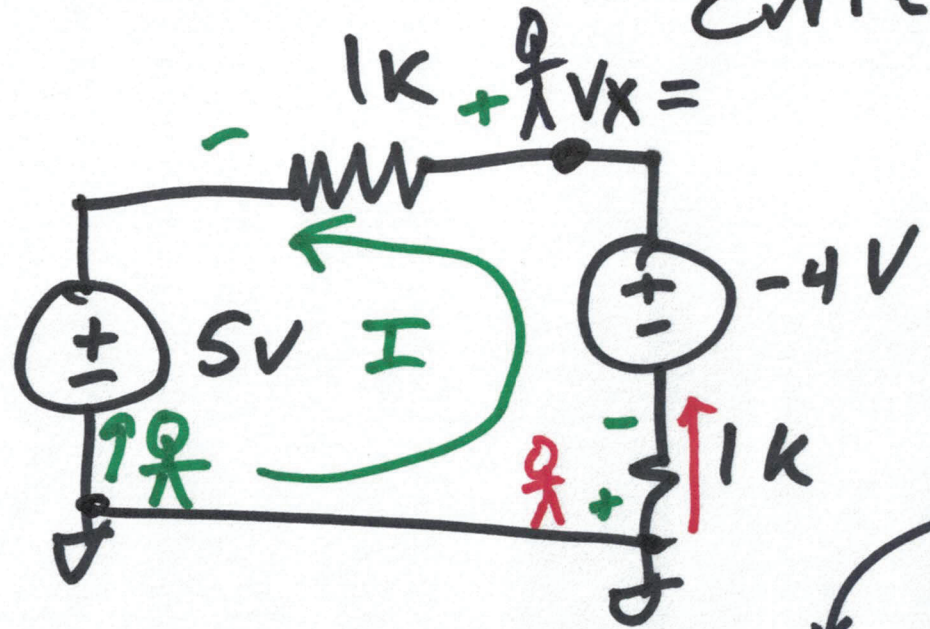

$+5V + 1kI - (-4) + 1k \cdot I = 0$

$\frac{2kI}{1} = \frac{-9}{1}$


$I = -4.5 \text{ mA}$

$-I 1k + (-4V) = V_x$

$\frac{1}{2} V = 4.5V - 4 = V_x$

5)


1st

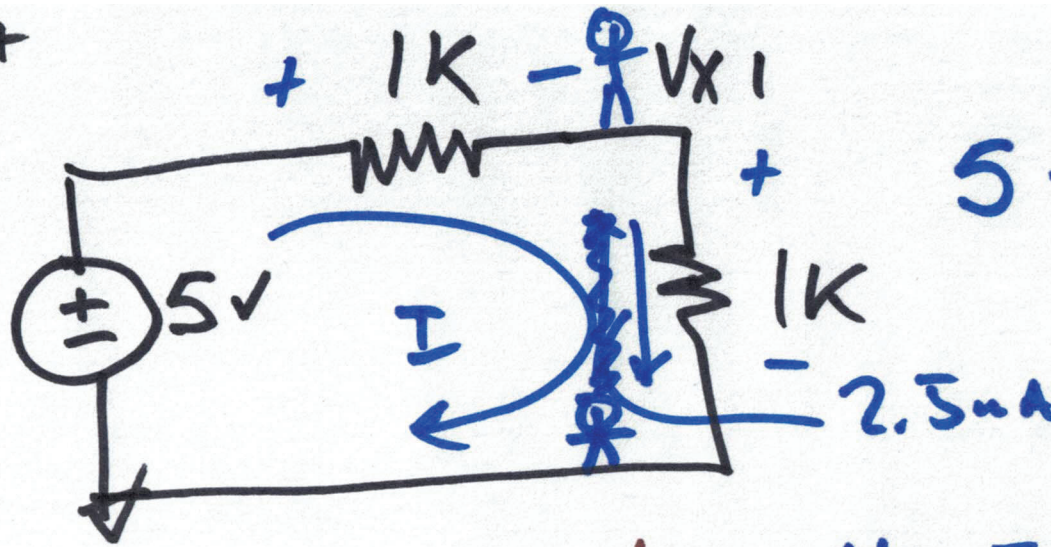

$$5 - 1kI - 1kI = 0$$

$$I = 2.5 \mu A$$

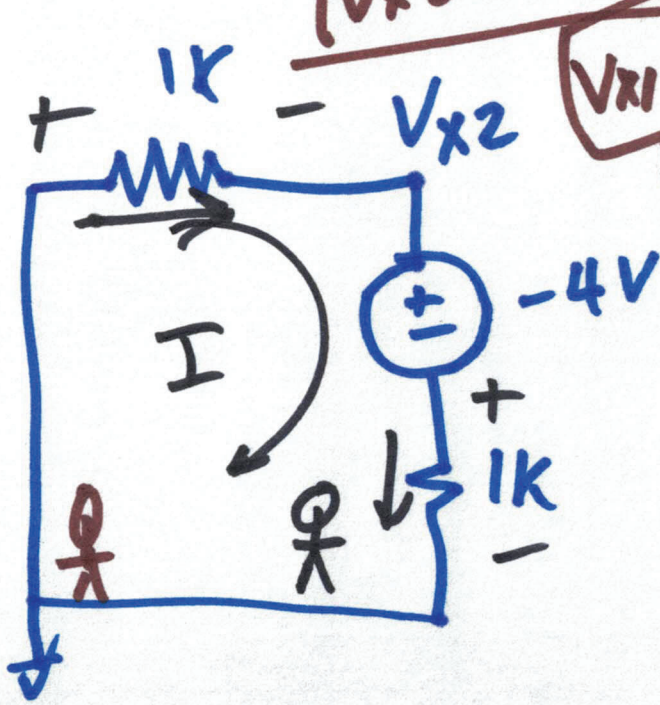$-1k \cdot 2.5 \mu A = V_{x2}$
 $V_{x2} = -2V$
 $V_{x1} = +1k \cdot 2.5 \mu A$
 $V_{x1} = 2.5V$



$+1k \cdot I + (-4V) + 1kI = 0$
 $2kI = 4$
 $I = \frac{4}{2k} = 2 \mu A$

$$I = \frac{4}{2k} = 2 \mu A$$

$$V_x = V_{x1} + V_{x2} = -2 + 2.5$$

$$V_x = \frac{1}{2}V$$

6)