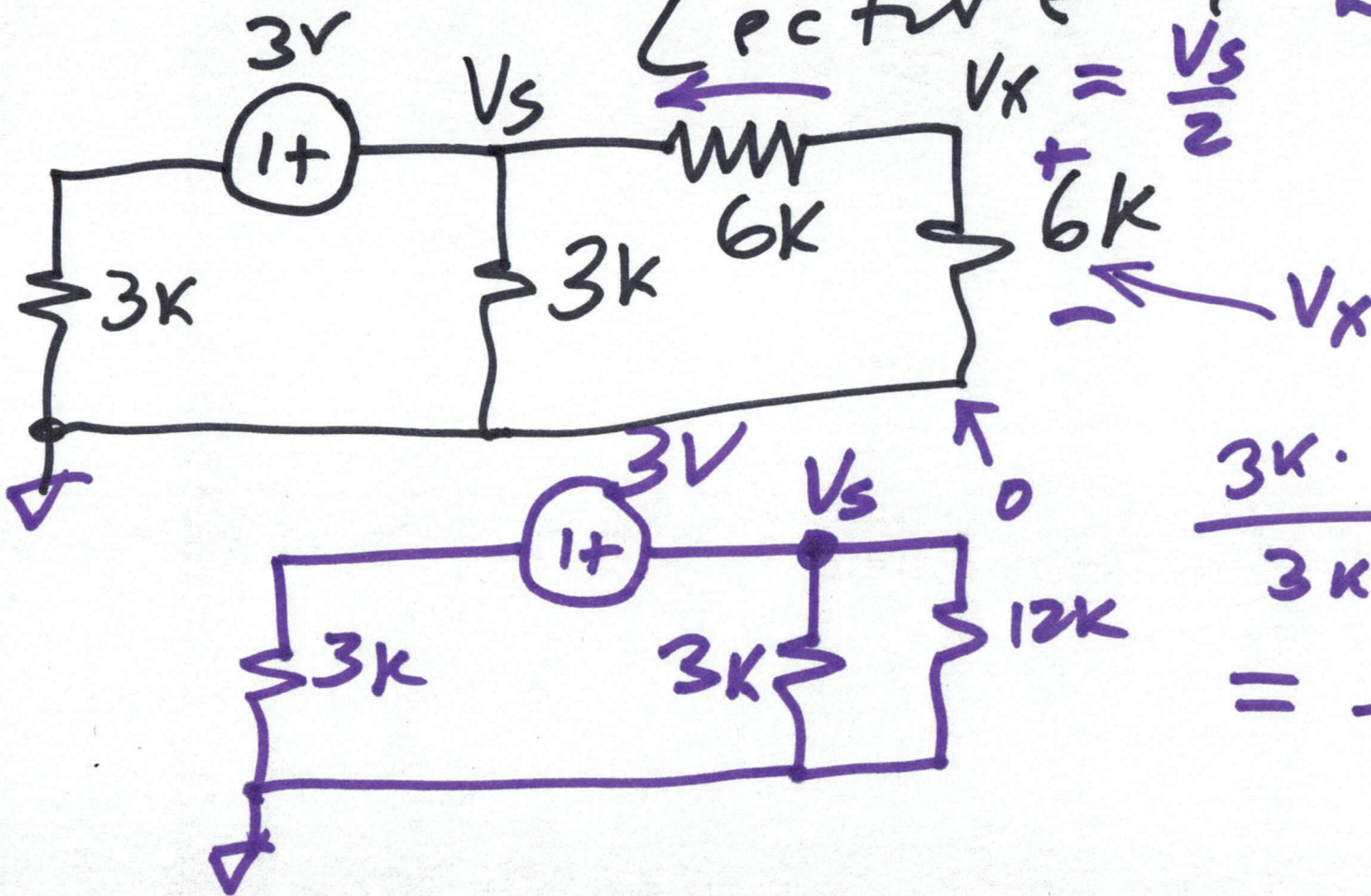


EE 220 Circuits I

Sept. 20, 2023


Lecture 7



$$V_x = \frac{V_s}{2}$$

$$\frac{3k \cdot 12k}{3k + 12k} = \frac{36k \cdot k}{15k}$$

1)

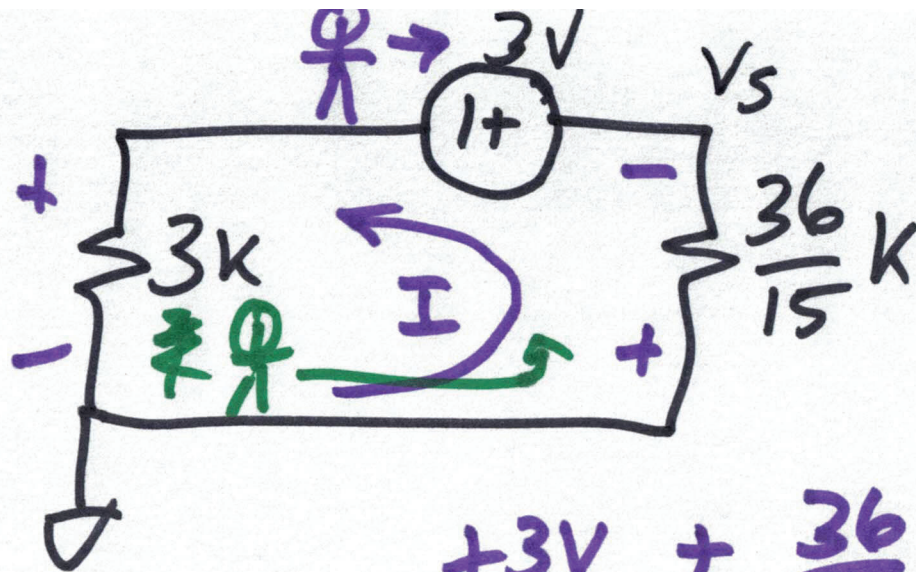

$$-\frac{36}{15} \text{ k} \cdot \frac{3}{81} \text{ mA} = V_s$$

$$-9.9 \cdot \frac{3}{81} = \frac{12}{9} \text{ V}$$

$$+3\text{V} + \frac{36}{15} \text{ k} \cdot I + 3 \text{ k} I = 0$$

$$V_s = \frac{12}{9} \text{ V} = \frac{4}{3} \text{ V}$$


$$-3 = \frac{36}{15} \text{ k} I + \frac{45}{15} \text{ k} \cdot I$$

$$-3 = \frac{81 \text{ k}}{15} \cdot I$$

$$I = \frac{-45}{81 \text{ k}}$$

$$I = -\frac{45}{81} \text{ mA}$$

$$V_s = \frac{4}{3} \text{ V}$$

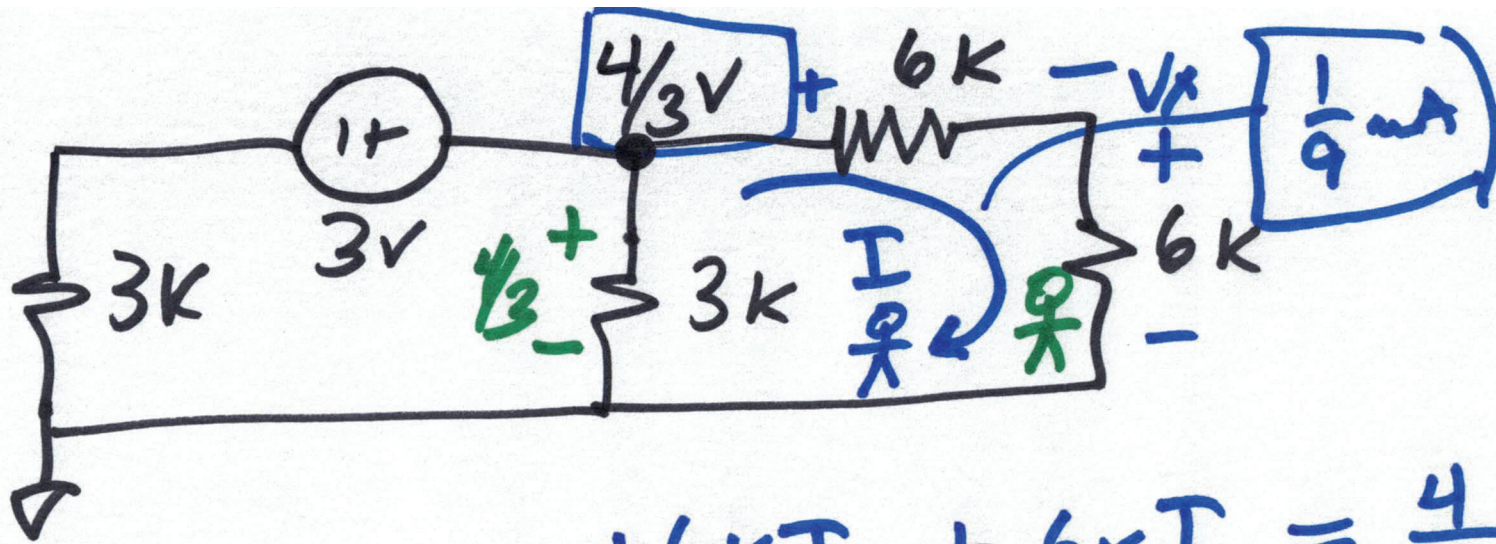

$$+6kI + 6kI = \frac{4}{3}V$$


$$+6kI + 6kI - \frac{4}{3}V = 0$$

$$V_x = \frac{1}{9} \text{ mA} \cdot 6k = 12kR \cdot I = \frac{4}{3}V$$

$$= \frac{6}{9}V = \frac{2}{3}V = V_x \quad I = \frac{4}{3 \cdot 12} \text{ mA}$$

$$= \frac{4}{3 \cdot 3 \cdot 4} \text{ mA}$$

$$I = \frac{1}{9} \text{ mA}$$

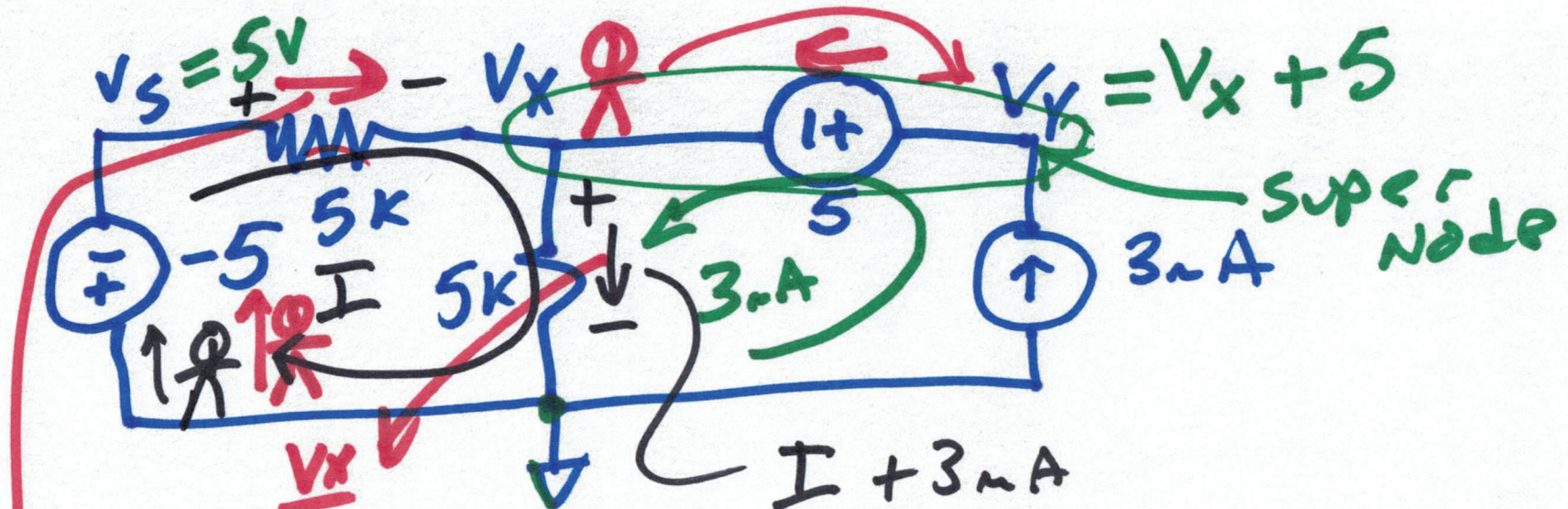


$$-(-5) - 5kI - 5k(I + 3mA) = 0$$

$$-(-5) - 5kI = Vx$$


$$-(-5) - 5kI + 5 = Vy$$

$$\frac{5 - Vx}{5k}$$


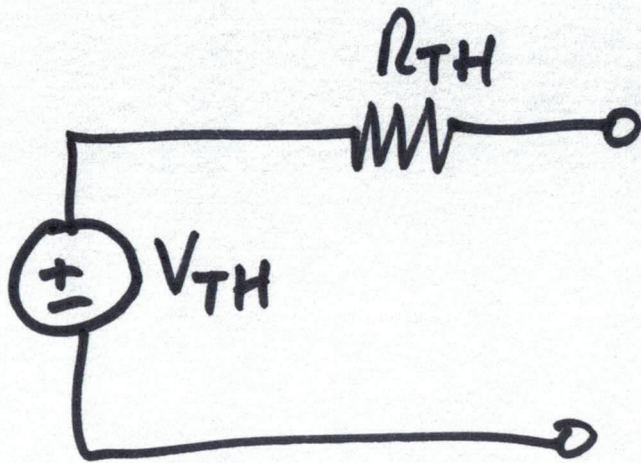



THEVENIN'S

Source transformation equivalent
Circuit

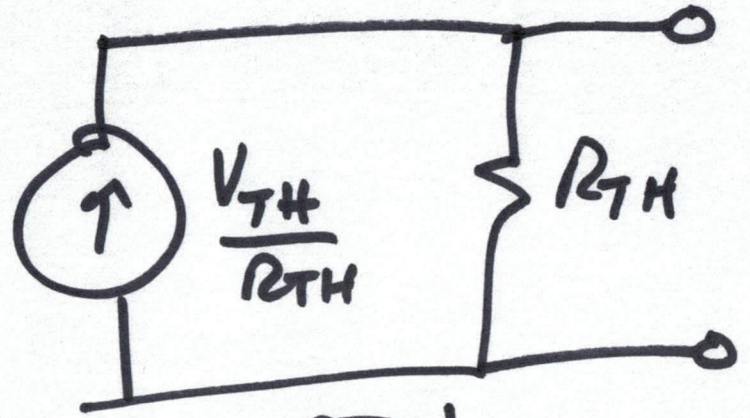

NORTON

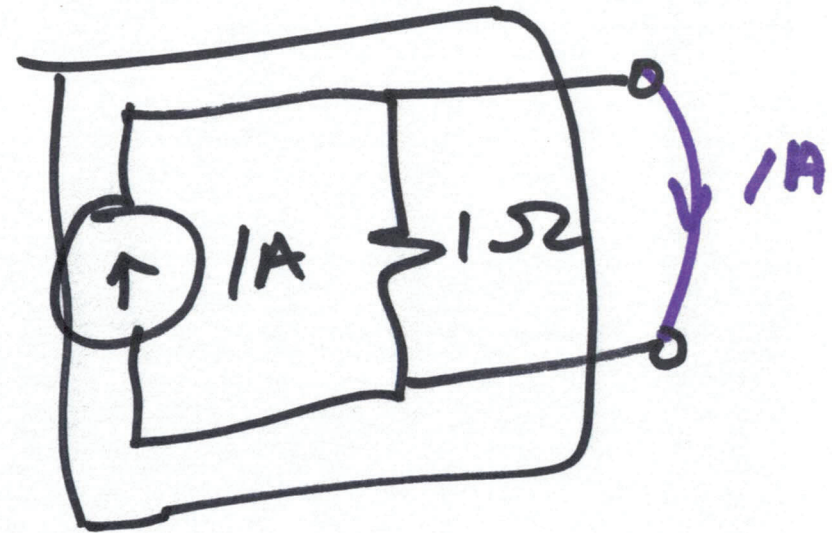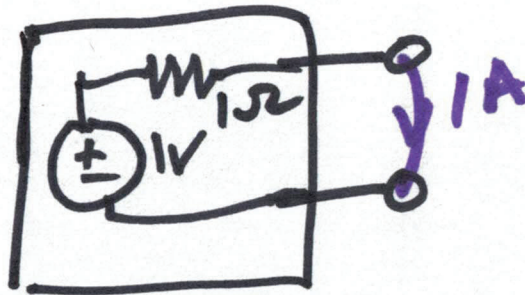


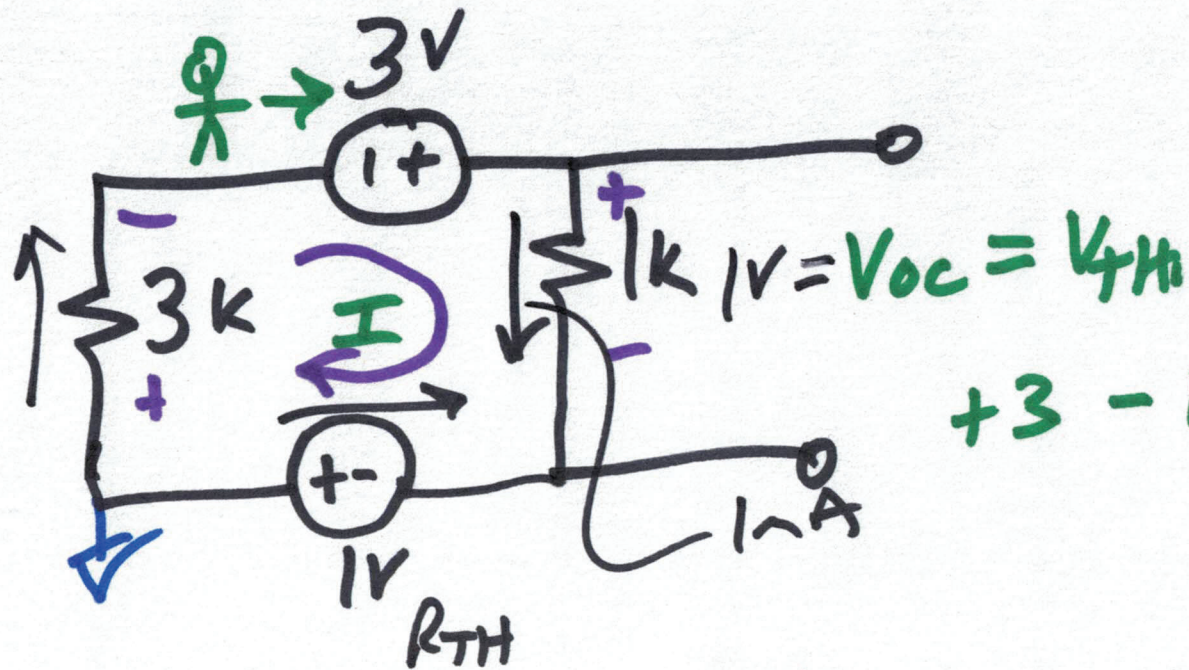



$$\frac{1k \cdot 3k}{1k + 3k} = 750$$

$$+3 - 1kI + 1 - 3kI = 0$$

$$4 = 4kI$$


$$I = 1\mu A$$

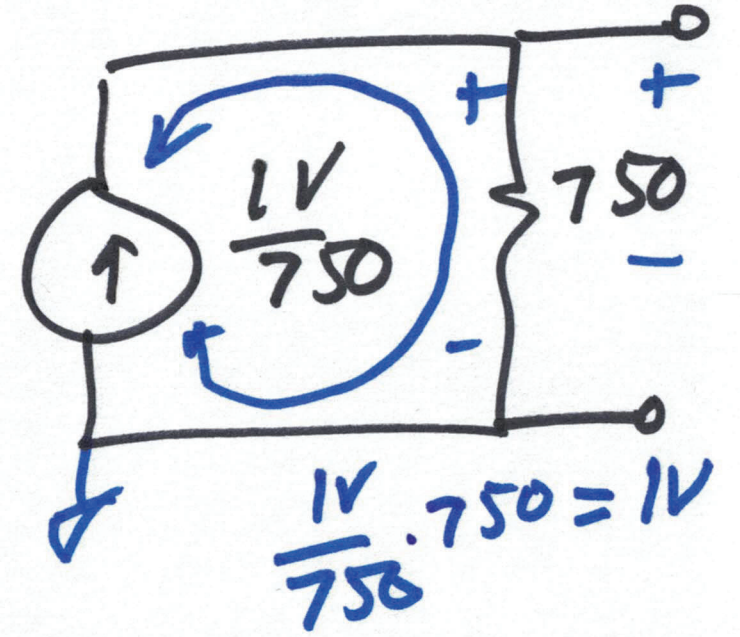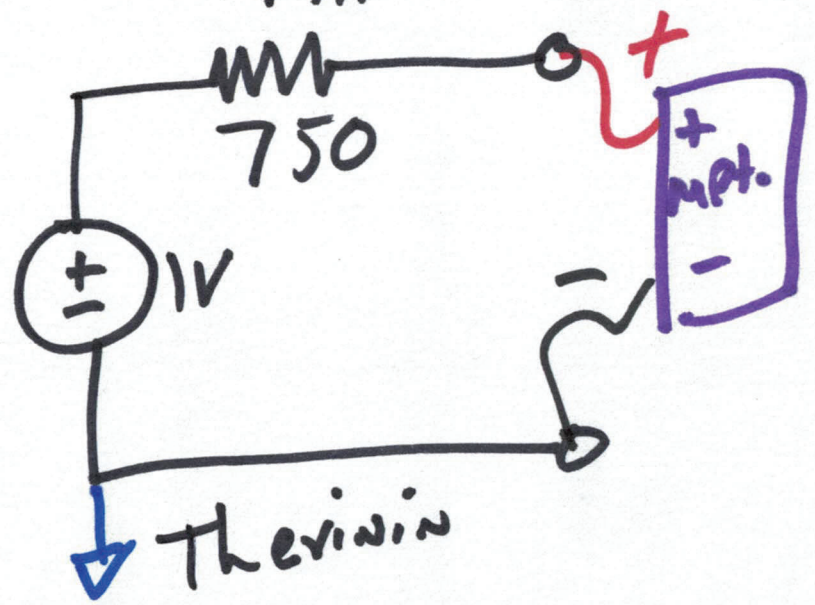

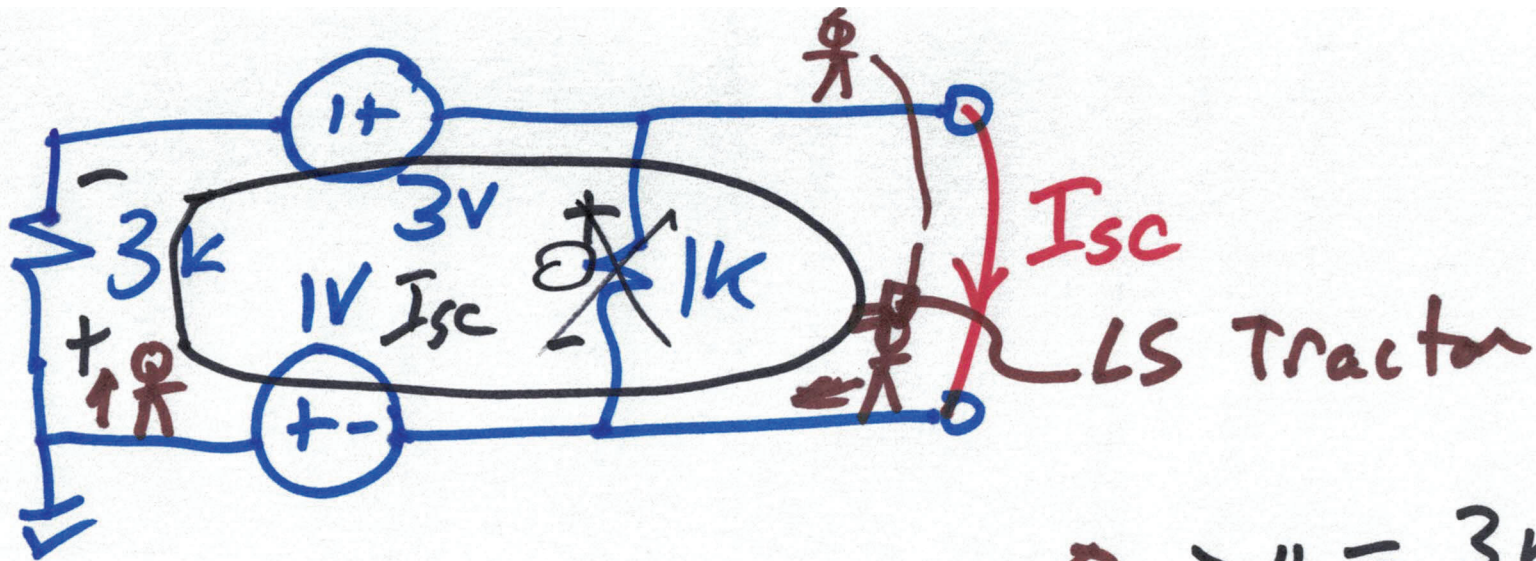



$$-3kI_{sc} + 3 + 1 = 0 \rightarrow 4 = 3kI_{sc}$$

$$I_{sc} = \frac{4}{3} \text{ mA}$$

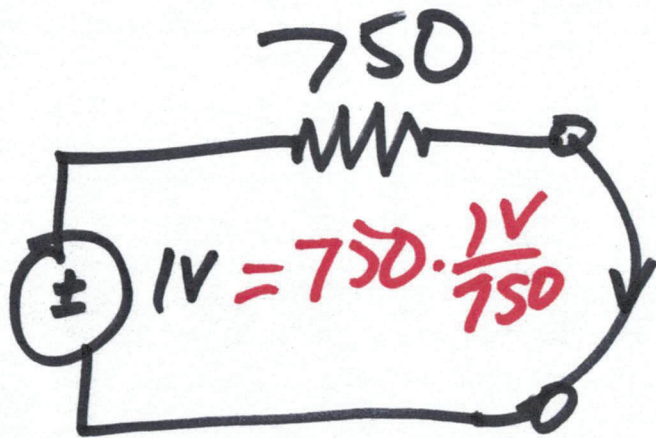
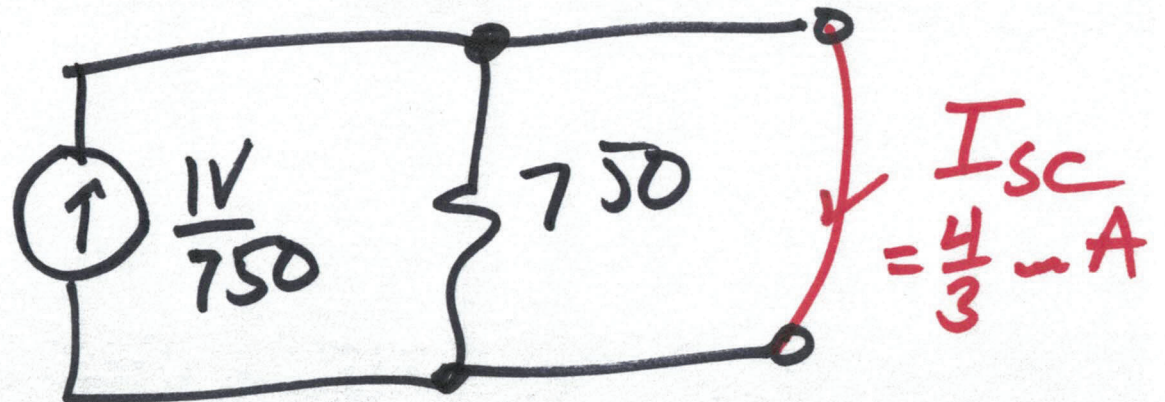
$$I_{sc} = \frac{1}{750} = \frac{1}{\frac{3}{4}k} = \frac{4}{3} \text{ mA}$$





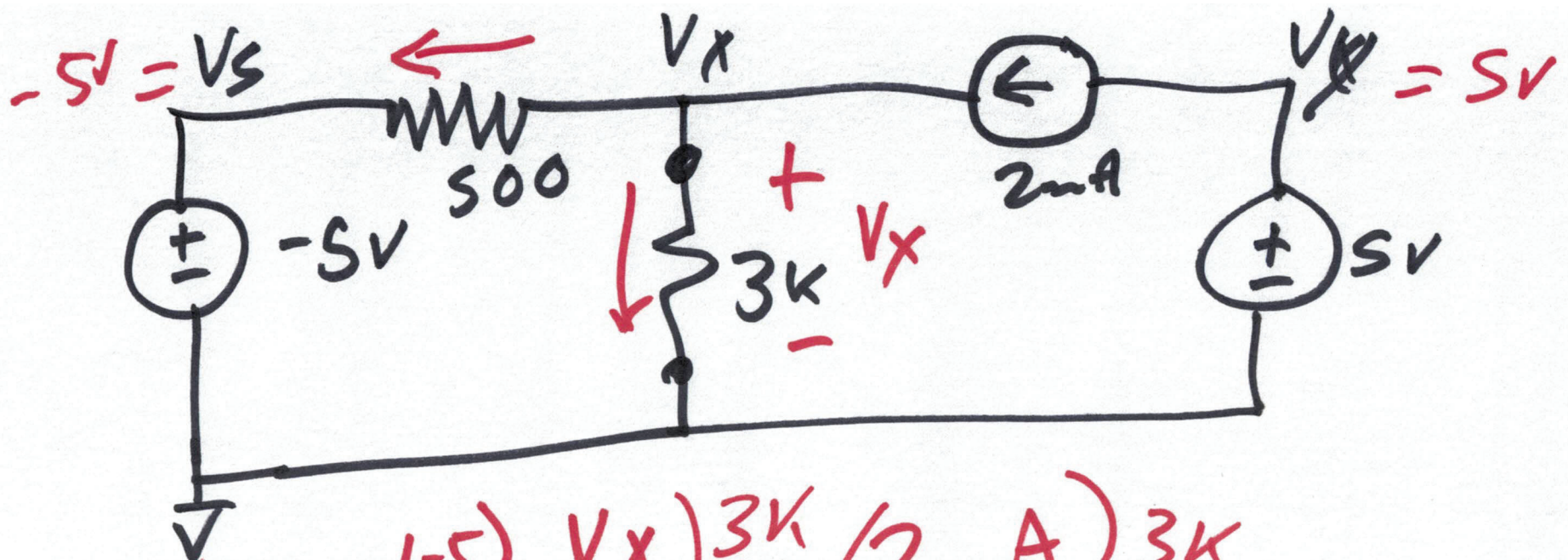

$$\left(\frac{V_x - (-5)}{500} + \frac{V_x}{3k} \right) 3k = (2 \text{ mA}) 3k$$

$$6V_x + 30 + V_x = 6V$$

$$V_x = -\frac{24}{7} \text{ V}$$

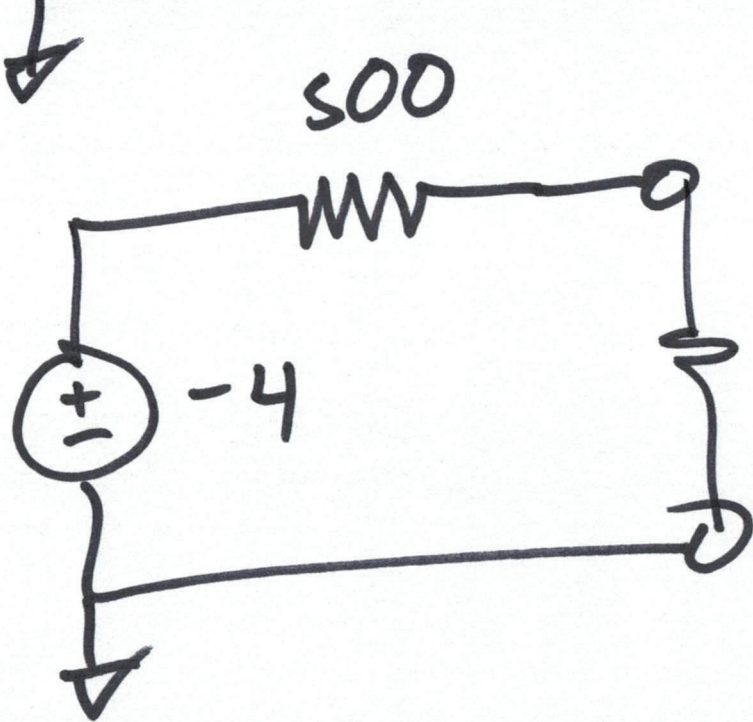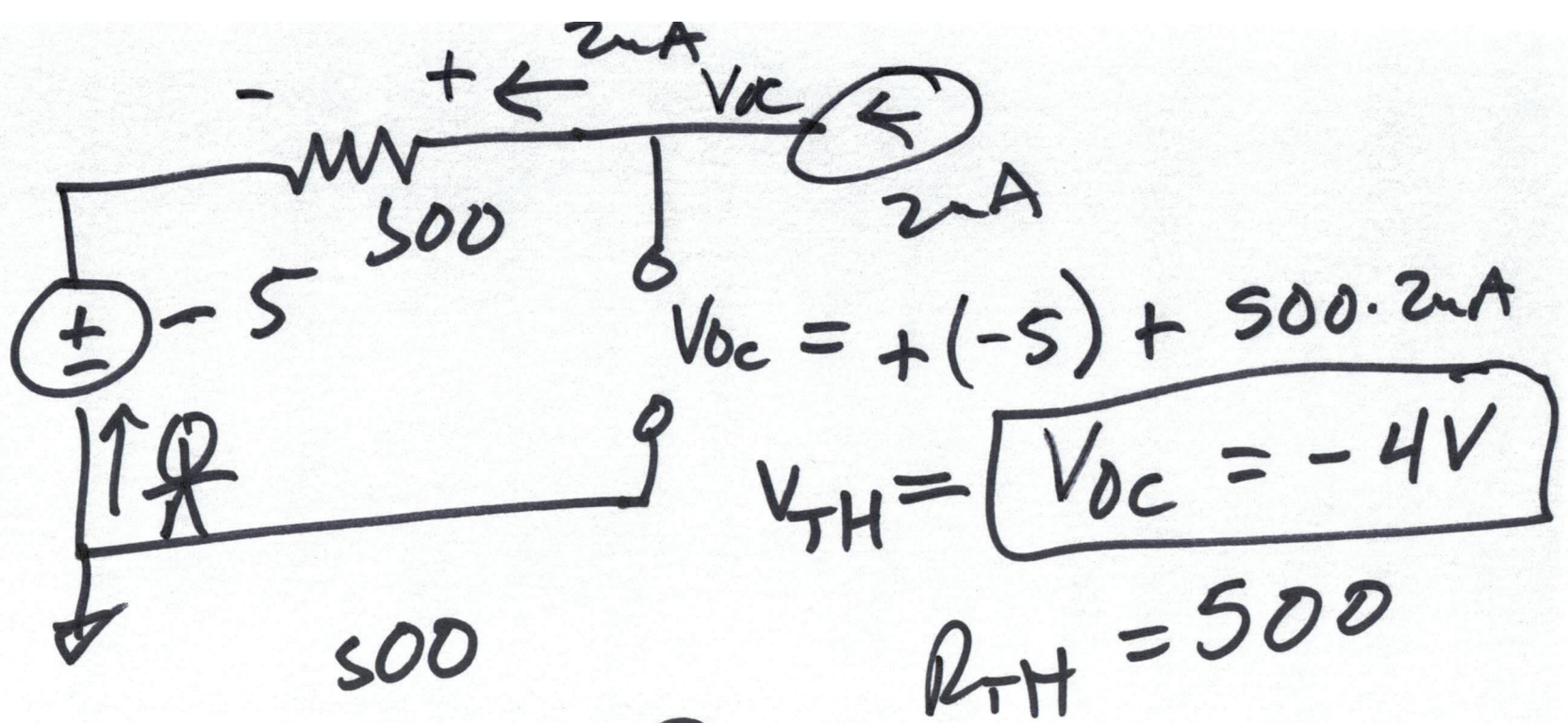

$$\begin{aligned}
 &3k \rightarrow -4 \cdot \frac{3k}{3k + 500} \\
 &= \frac{-4 \cdot 6 \cdot 500}{7 \cdot 500} \\
 &= -\frac{24}{7} V
 \end{aligned}$$