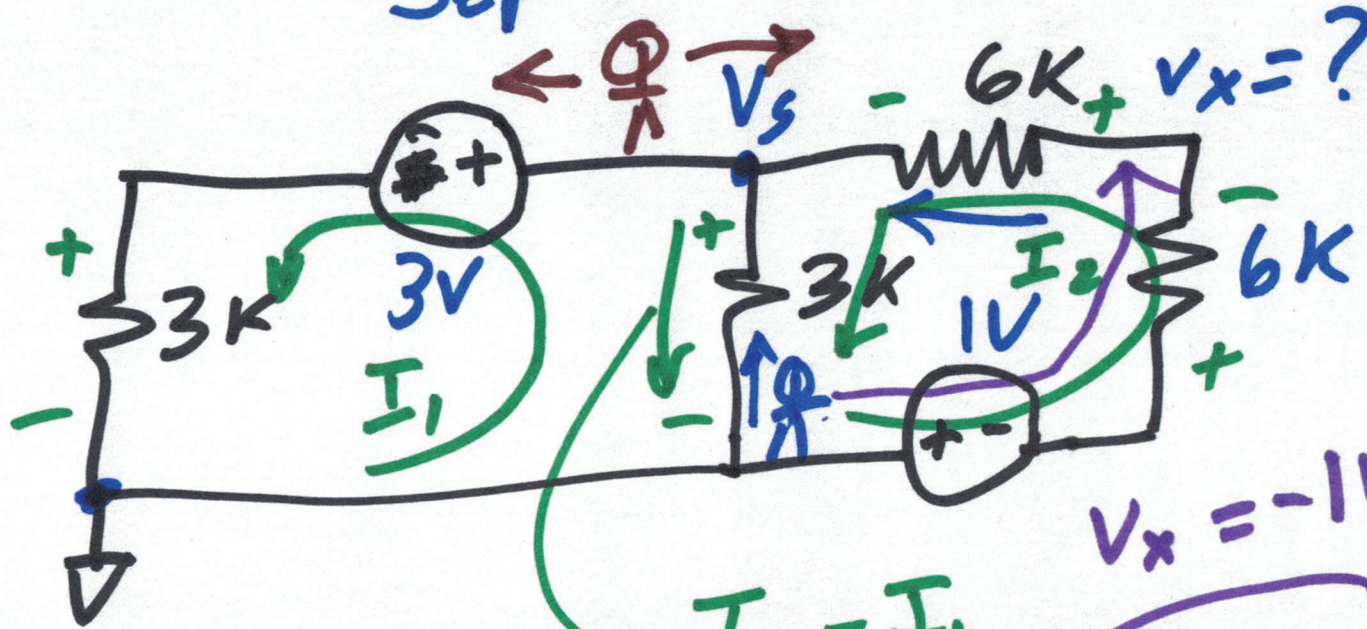


EE 220 Circuits I

Lecture 8

Sept. 25, 2023



V_s $6k$ $V_x = ?$

$$V_x = -1V - 6k \left(\frac{-5}{27} \right)$$

$$-3 - 3kI_1 + 3k(I_2 - I_1) = 0$$

$$+6kI_2 + 6kI_2 + 1V + 3k(I_2 - I_1) = 0$$

$$-\frac{27}{27} + \frac{30}{27} = \frac{3}{27} = \frac{1}{9}V$$

$$3 = -3kI_1 + 3kI_2 - 3kI_1$$

$$1 \mu A = -I_1 + I_2 - I_1$$

$$I_2 = 2I_1 + 1 \mu A$$

$$\rightarrow 12kI_2 + 1 + 3kI_2 - 3kI_1 = 0$$

$$\rightarrow 15kI_2 + 1 - 3kI_1 = 0$$

$$15k(2I_1 + 1 \mu A) + 1 - 3kI_1 = 0$$

$$30kI_1 + 15 + 1 - 3kI_1 = 0$$

$$27kI_1 = -16$$



$$I_2 = 2\left(\frac{-16}{27k}\right) + 1 \mu A$$

$$= \frac{-32}{27k} + 1 \mu A$$

$$I_1 = \frac{-16}{27k}$$

$$-1 \mu A + \frac{5}{27} \mu A + 1 \mu A$$

$$I_2 = \frac{-5}{27} \mu A$$

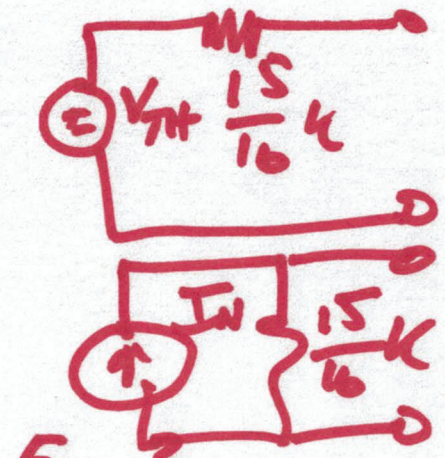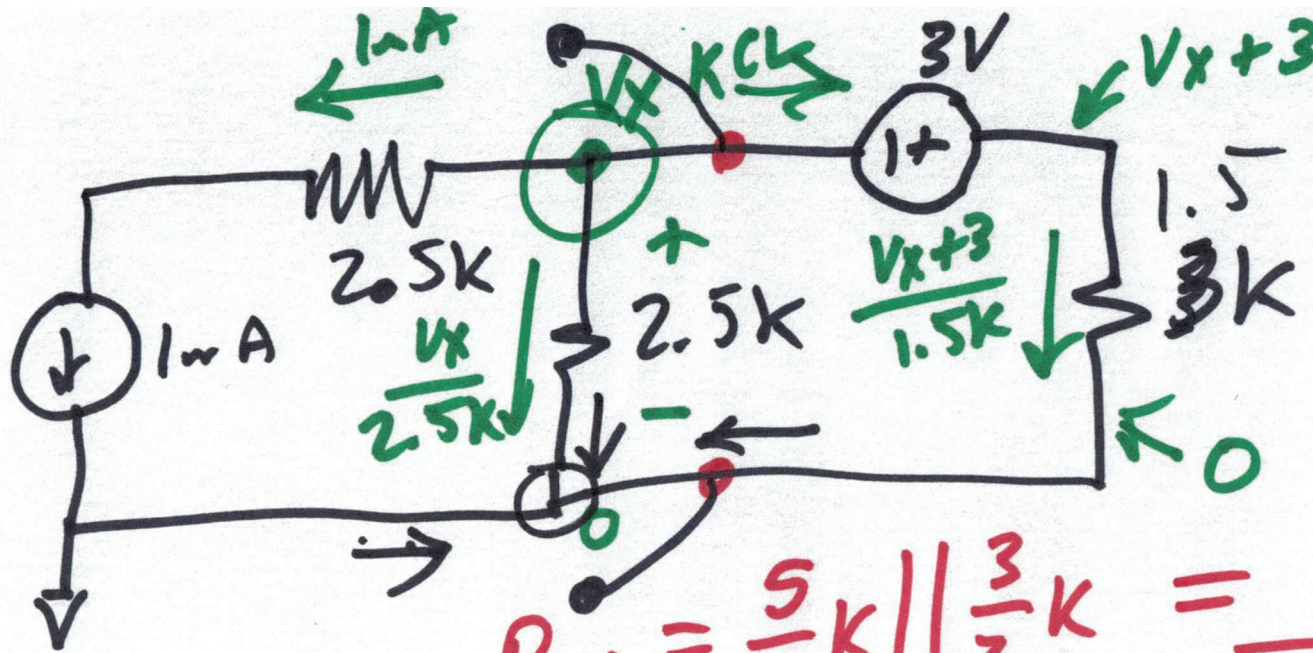

$$R_{TH} = \frac{5}{2} k \parallel \frac{3}{2} k = \frac{5 \cdot 3}{2+3} k$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad \left\{ \begin{matrix} R_1 \\ R_2 \end{matrix} \right\} \frac{R_1 R_2}{R_1 + R_2} + \frac{3}{2}$$

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{15}{2(8)}$$

$$R_{TH} = \frac{15}{16} k$$

$$2.5k \left(1\mu A + \frac{V_x}{2.5k} + \frac{V_x + 3}{1.5k} \right) = 0$$

$$2.5V + V_x + \frac{5}{3}(V_x + 3) = 0$$

$$\frac{2.5k}{1.5k}(V_x + 3) + 2.5V + \frac{3V_x}{3} + \frac{5V_x}{3} + 5 = 0$$


$$\frac{500.5}{500.3}(V_x + 3)$$

$$\frac{8}{3}V_x = -7.5$$


$$V_x = \frac{-22.5}{8}$$

$$V_{TH} = \frac{-22.5}{8}$$
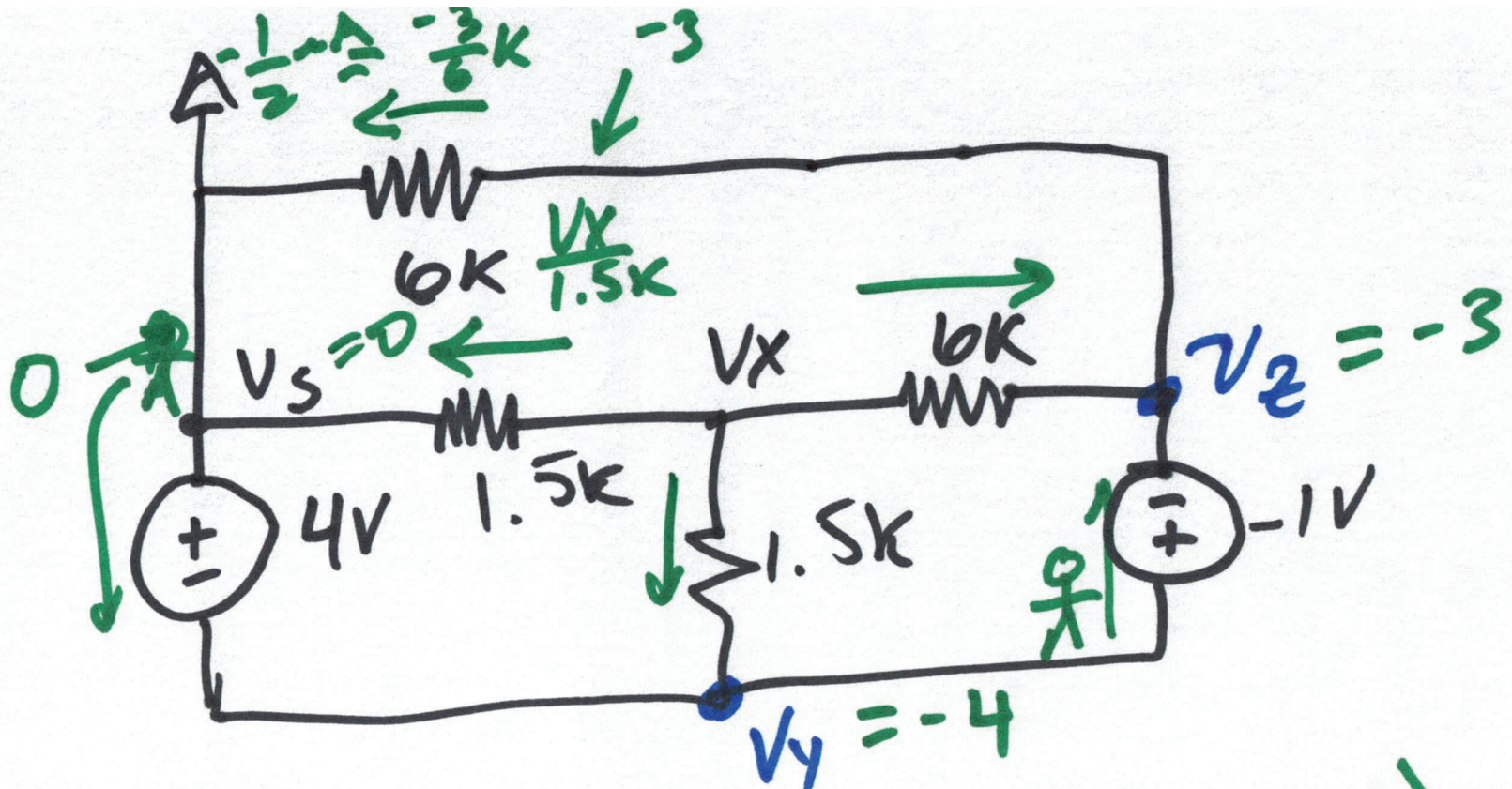
$$I_N = \frac{-22.5}{8} \div \frac{15}{16}k$$
$$= -\frac{55}{16} \mu A$$



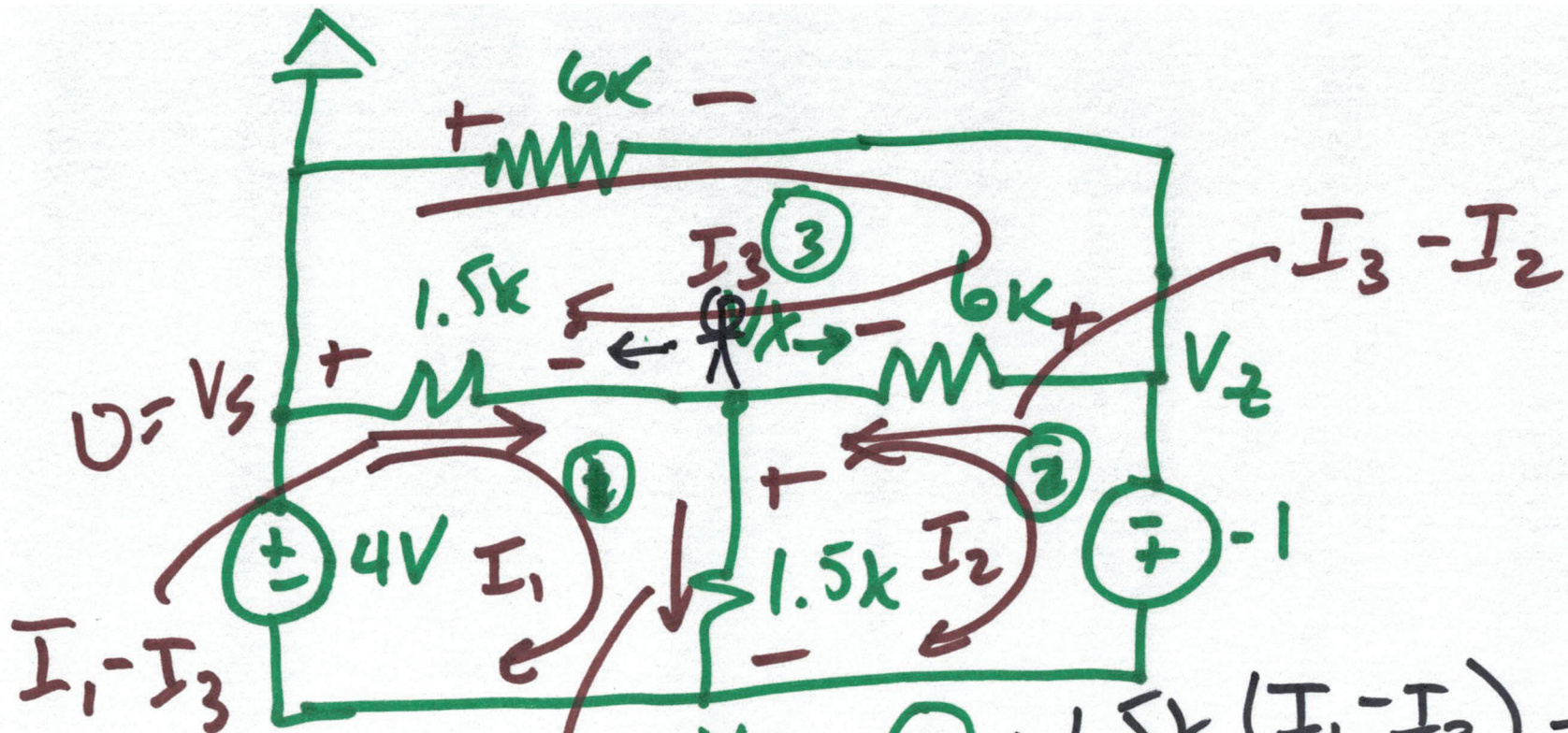
$$\frac{V_x - 0}{1.5k} + \frac{V_x - (-4)}{1.5k} + \frac{V_x - (-3)}{6k} = 0$$




$$+1.5k(I_1 - I_3) - 6kI_3 - 6k(I_3 - I_2) = 0$$

$$6k(I_3 - I_2) + (-1) + 1.5k(I_1 - I_3) - 4 + 1.5k(I_1 - I_2) = 0$$

①

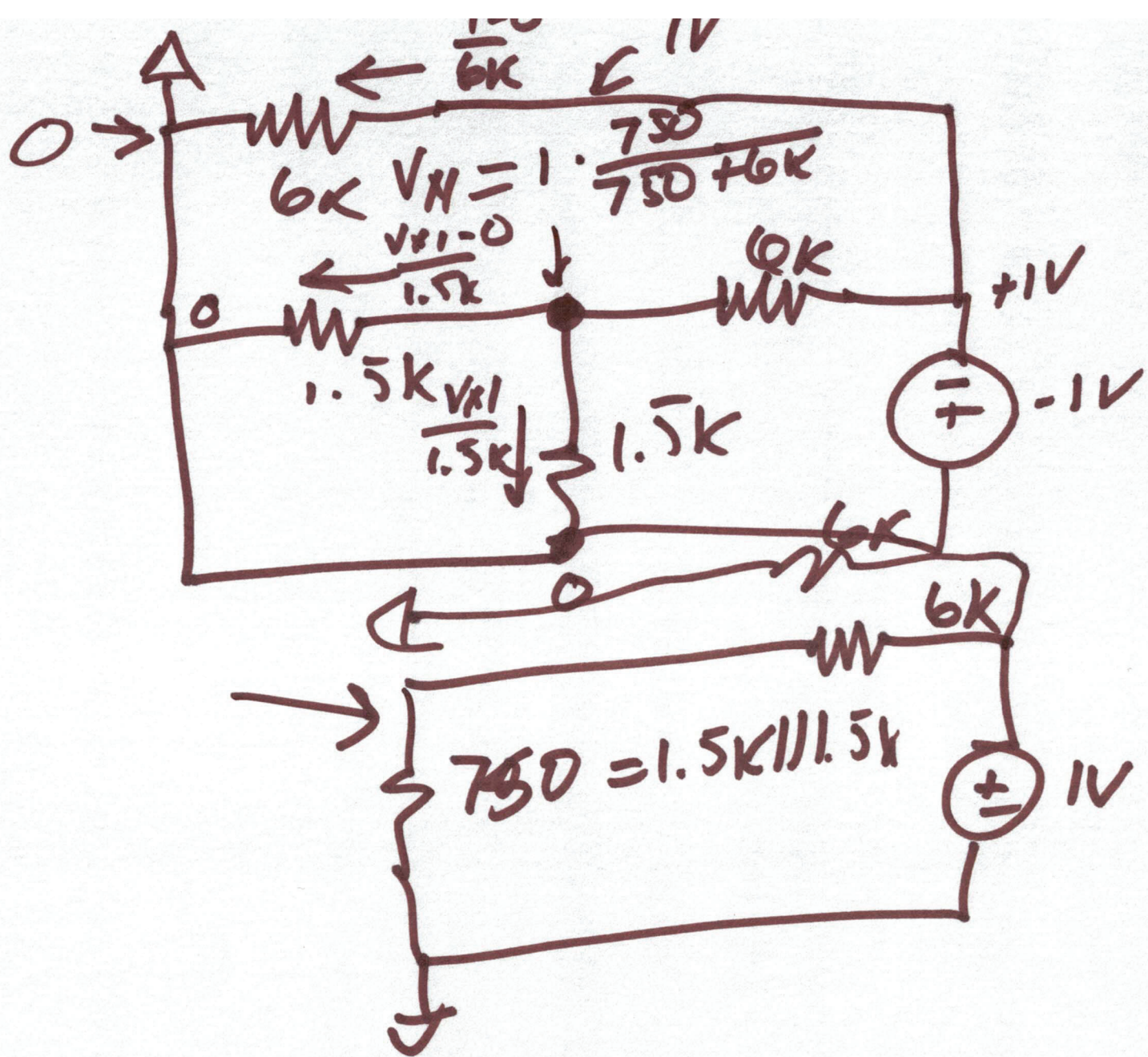

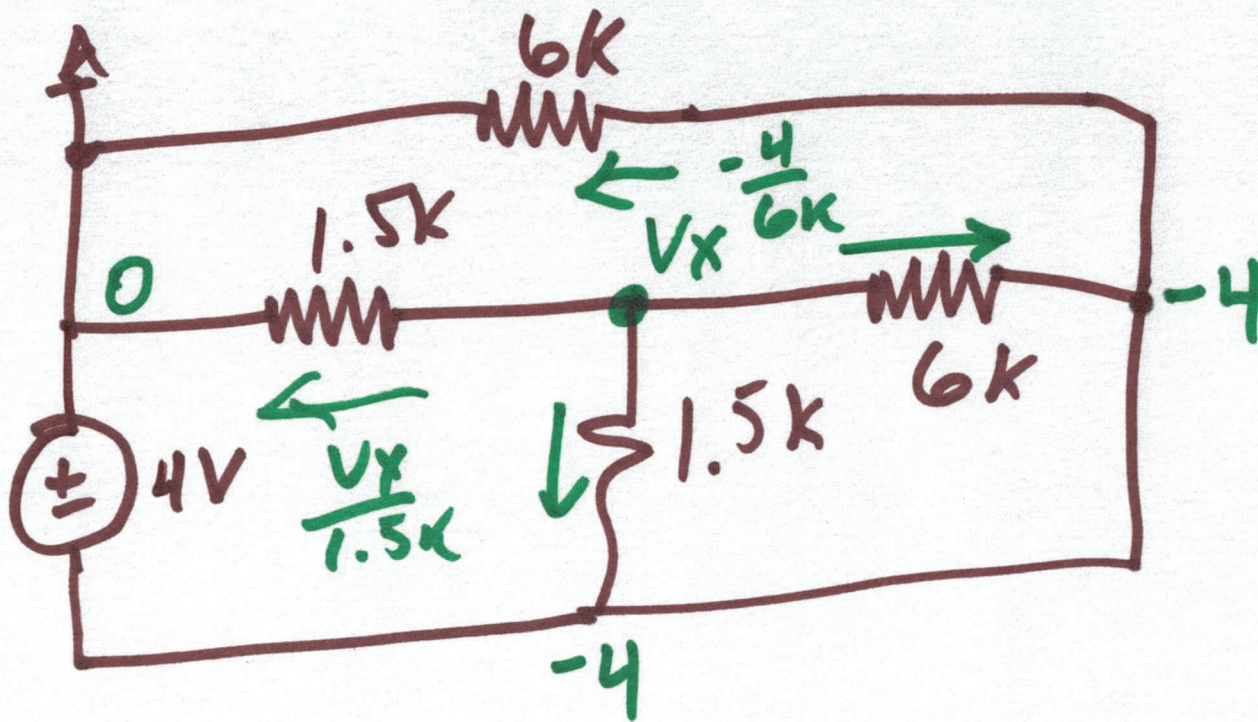

$$\frac{V_x}{1.5k} + \frac{V_x + 4}{1.5k} + \frac{V_x - (-4)}{6k} = 0$$

8)