

Quiz #9 EE 220 Fall 2023 Name: \_\_\_\_\_

Closed book and closed notes.

Show your work for credit!

1. Find the voltages  $V_s$  and  $V_t$ . As always, show your work for credit. (5 points)

