

Closed book and notes.

Show your work for credit and place boxes around your answers.

1. What are V_1 , V_2 , V_3 , and V_4 in the following circuits? (1 point) Next, determine the currents that flow in the directions indicated. (4 points)

