

Quiz #15 EE 220 Spring 2017

Name: _____

Closed book and notes.

Show your work for credit!

1. What is wrong with the following LTspice schematic? Note that this schematic was copied from one of the questions on the CMOSedu Google Group. (2 points, no partial credit)

